

Chapter 5

CHAPTER 5


CMOS Circuit and Logic Design



Chapter 5

Outline

- 5.1 Static Logic Circuit
- 5.2 Dynamic Logic Circuit
- 5.3 CMOS Differential Logic
- 5.4 Pass - Transistor Logic Families
- 5.5 Input / Output Circuits
- 5.6 Clock Drivers and Clock Distribution

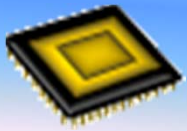

Chapter 5

❑ The demand for high-performance CMOS VLSI circuit :

- High operation speed
- High packing density
- Low power dissipation

❑ Logic Structure

- Static logic : No floating output nodes
- Dynamic logic : a lower bound on the speed of the clock
- Transmission gate logic : MOS action as a switch
- Asynchronous logic : no global clock




Chapter 5

5.1 Static Logic Circuit

5.1.1 Static Logic Circuit

(A) CMOS Basics

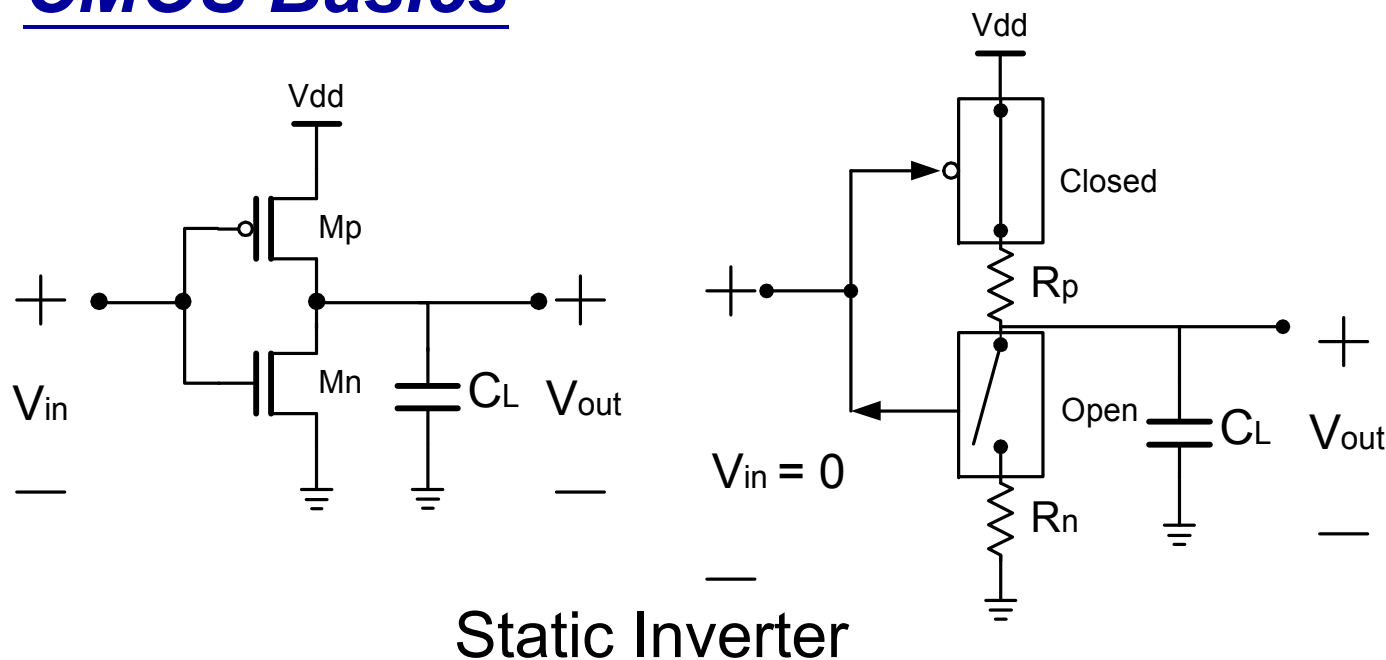

Active pull down device : **NMOS**

Active pull up device : **PMOS**



Chapter 5


- ❑ The output of CMOS must make a **full voltage swing** between VDD and GND . This is important to guarantee the **zero static power dissipation** and **increase the noise margin** .
- ❑ CMOS is a **ratio less logic** , so that makes the circuit design simpler , Functionally , it is always correct without taking into account the ratio between pull-up and pull-down device .
- ❑ Only transition **power dissipation**
- ❑ Output **rise and fall transition time** can be made **the same** by account the ration between pull-up and pull-down device .



Chapter 5


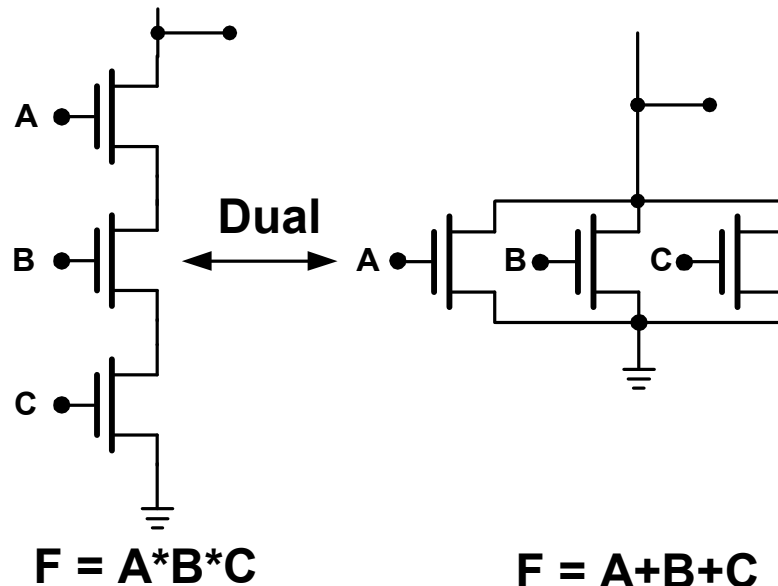
(B) Combination Logic

NMOS Logic Formation and Naturally Dual Network




(b) Rule 2 :

Parallel - connected
NMOSFETs

  


(c) Rule 3 :

Series - connected
Logic Blocks

 

(d) Rule 4 :

Parallel - connected
Logic Blocks

 


Chapter 5

- Conversion of Dual

AND \Leftrightarrow OR


SERIAL \Leftrightarrow PARALLEL

- NMOS Network ^{V.S.} \Leftrightarrow PMOS Network

 

Chapter 5


(C) NAND Gate and NOR Gate

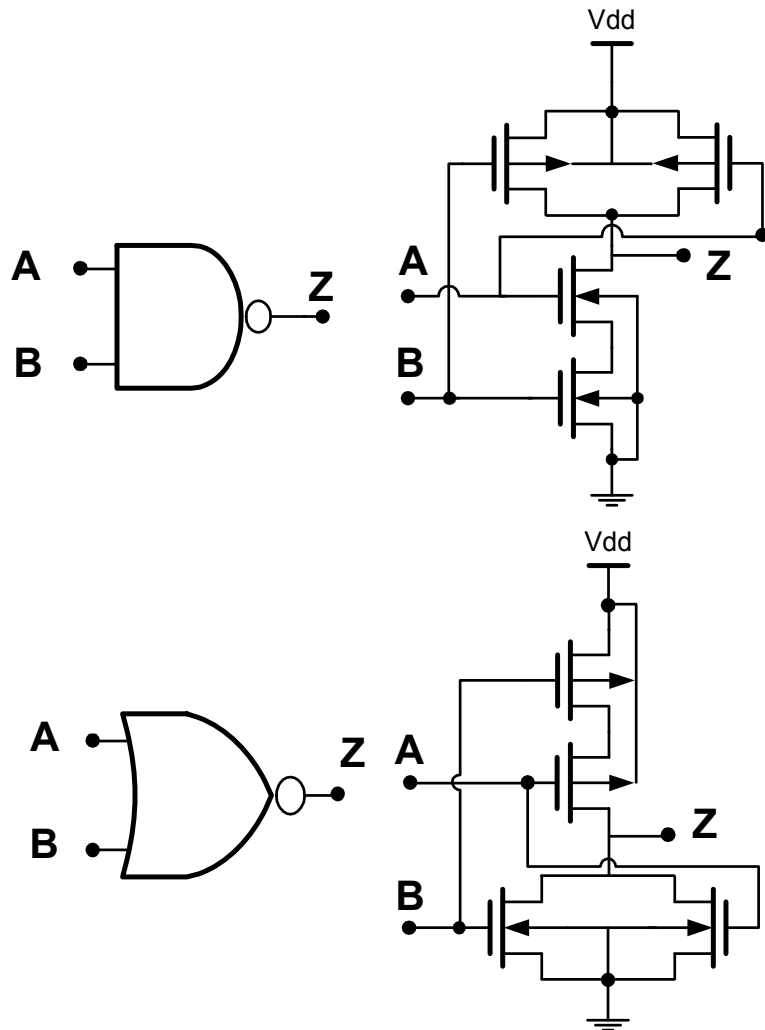


- PMOS substrate connected to the highest supply voltage V_{DD}
- NMOS substrate connected to the lowest supply voltage GND




Chapter 5

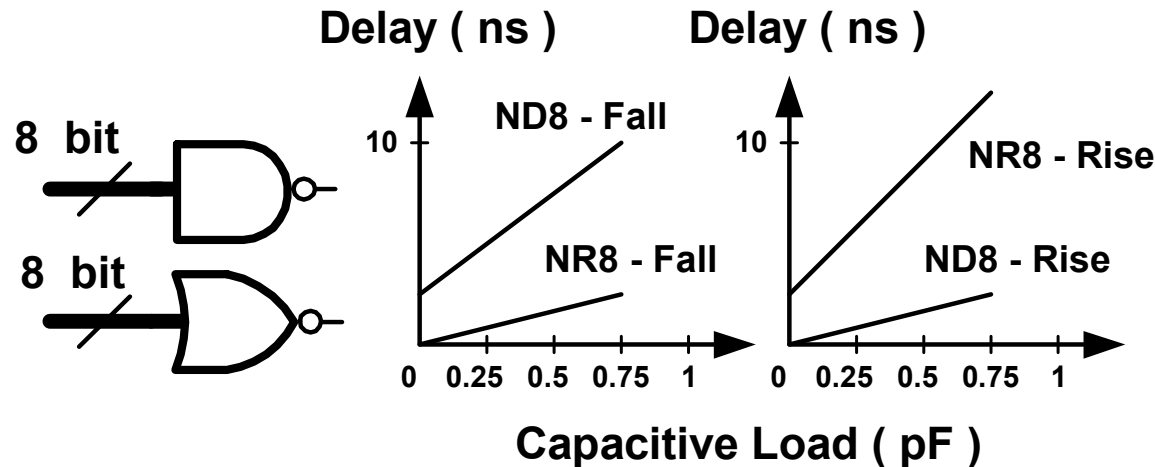


- Gate delay of logic gates
- A function of capacitive load , and logic gate types .

 

 

Chapter 5

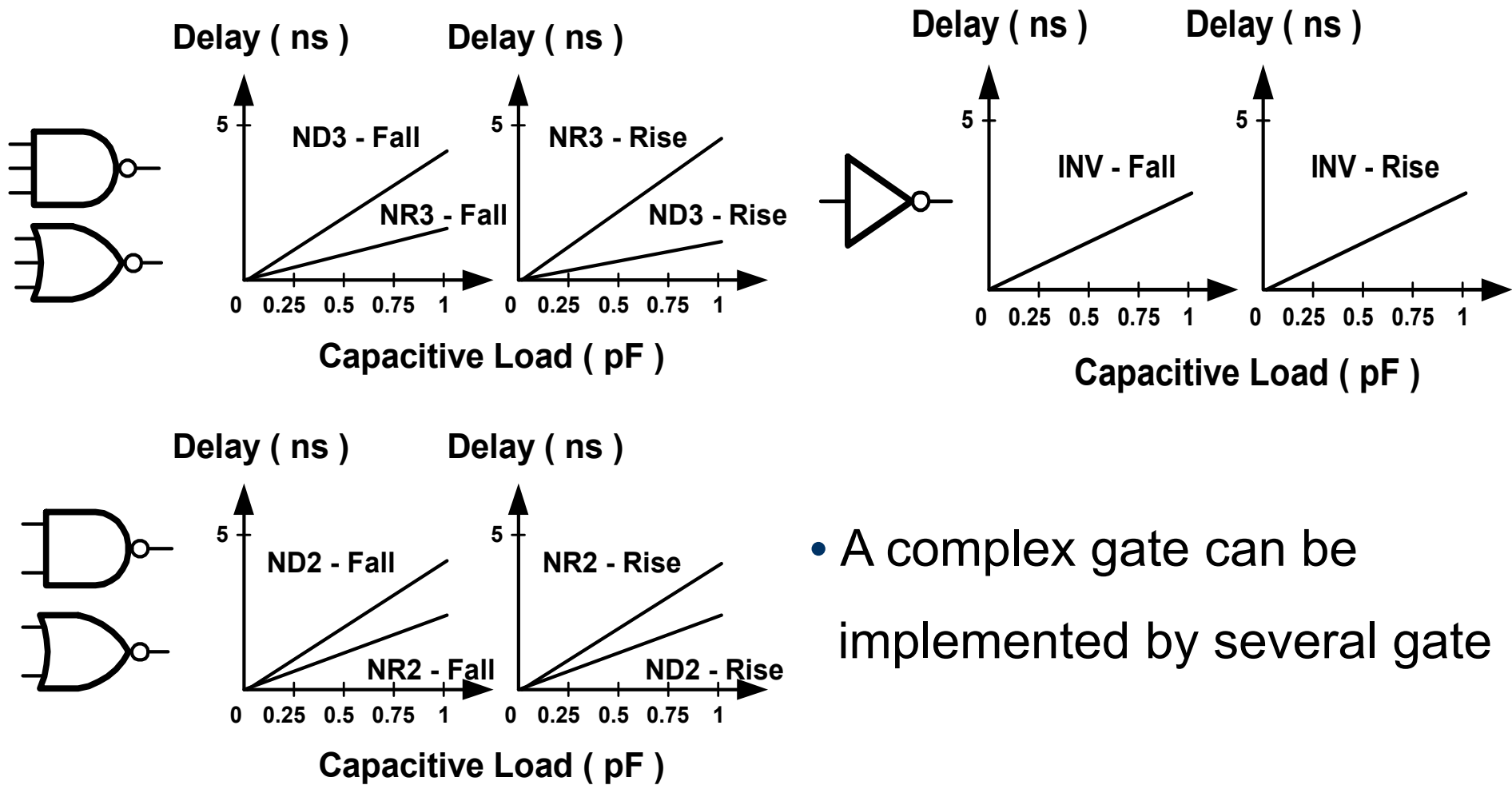


- A complex gate can be implemented by several gate



Chapter 5

EXAMPLE

- As an example of a simple logic decision consider the implement of an 8-input AND gate driving 1pF load (for instance , a row decoder in a RAM or ROM) , we may use the following :
 - Approach 1 – An 8-input NAND and an inverter
 - Approach 2 – Two 4-input NAND and 2-input NOR
 - Approach 3 – Four 2-input NAND two 2-input NOR , a 2-input NAND and an inverter ◦

 



Chapter 5



- Comparison of approaches to designing an 8-input AND gate

APPROACH	DELAY STAGE 1	DELAY STAGE 2	DELAY STAGE 3	DELAY STAGE 4	TOTAL DELAY (SPICE) ns
1	3.37	2.82			6.2
ND8->	ND8	INV			6.5
INV	Falling	Rising			
2	4.36	0.88			5.24
ND4->	ND4	ND2			5.26
NR2	Falling	Rising			
3	0.31	0.4	0.31	2.17	3.19
ND2->	ND2	NR2	ND2	INV	3.46
NR2->	Falling	Rising	Falling	Rising	
ND2->					
INV					





Chapter 5

(D) Complex Combination Logic Gate

  

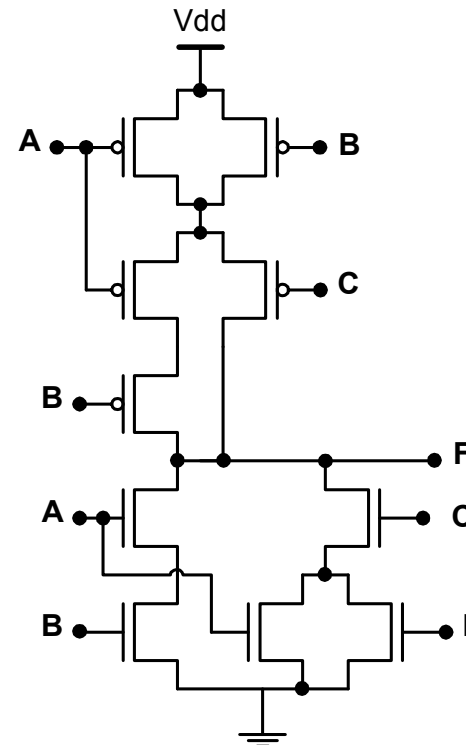 CMOS Circuit for $F = \overline{ABC + AD}$




AOI CMOS Circuit for $F = \overline{AB + AC + BC}$




Chapter 5


(E) Symbol Layout

 


(a)

 

(b)

 

(c)

 


(d)


A sequence of steps to create the physical layout of an inverter





Chapter 5

- Symbolic Layout for CMOS inverter

 

 


Chapter 5

  


- Large inverter can be created by paralleling inverters



Chapter 5

 

(e)

 


(f)



Chapter 5


- Symbolic layouts for the CMOS NAND gate

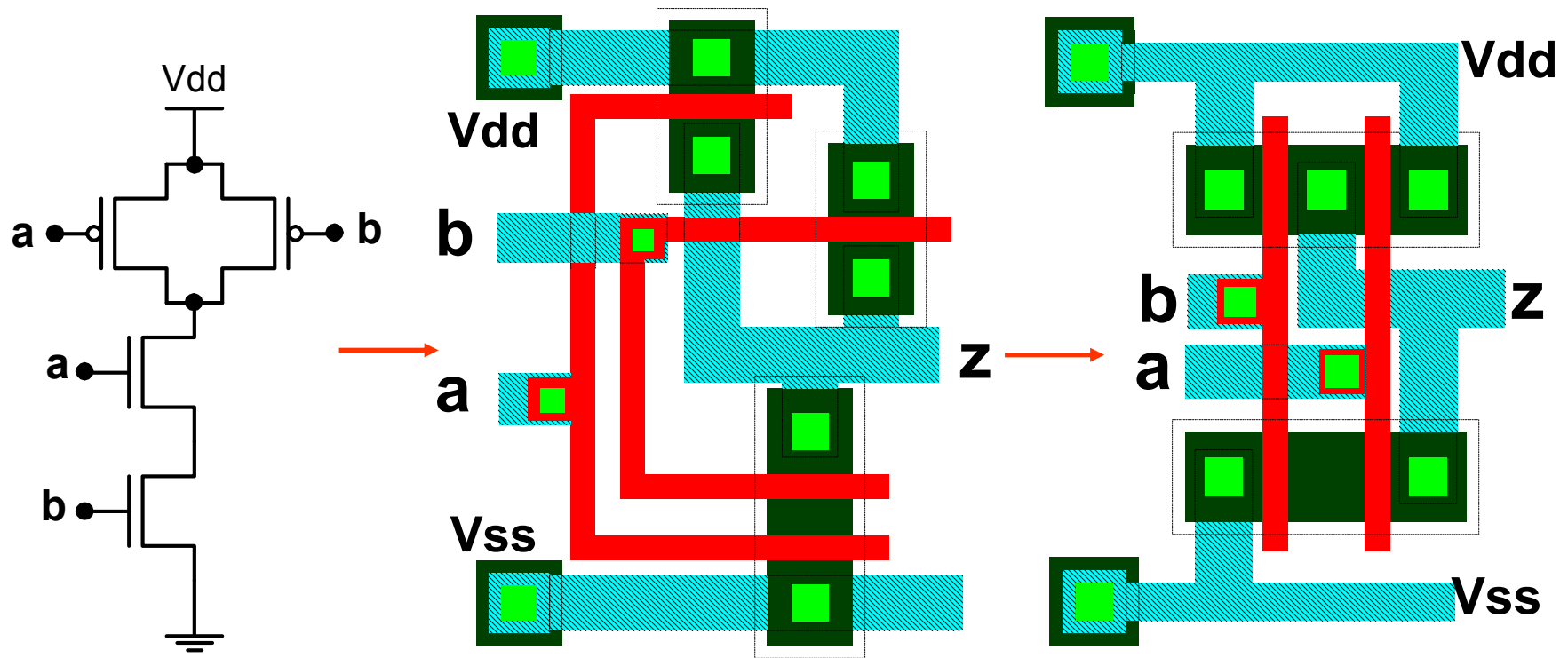



Chapter 5

- Symbolic layouts for the CMOS NOR gate


 




Chapter 5

(F) Complex Logic Gate Layout

- The PMOS and NMOS connection can be represented as an P-graph and N-graph .
- Each edge of the graph represents a MOS .

  




Chapter 5

- Euler path : A sequence of edges in the graph .
- The gate in the Euler path may share a common source-drain connection and may be connected together with no breaks .
- The algorithm are as follows
 1. Find all Euler paths that cover the graph .
 2. Find a p- and n- Euler path that have identical labeling (a labeling is an ordering of gate labels on each vertex) .
 3. If the paths in step 2 are not found , then break the gate in the minimum numbers of places to achieve step 2 by separate Euler paths .



Chapter 5

Example :

 





Chapter 5


5.1.2 NMOS Logic

Enhancement Mode

 

(a) Enhancement Load

 


 

Chapter 5

5.1.3 Pseudo NMOS Logic

(a) Pseudo-NMOS NAND2 circuit

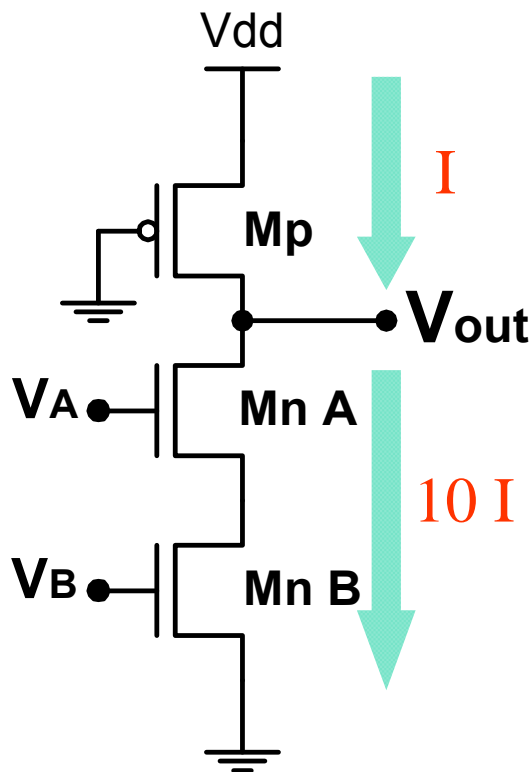


- ☐ Less Area
- ☐ Low cap Load (only NMOS)
- ☐ Speed is compatible (or slower) than static CMOS
- ☐ RATIO LOGIC : pull up current is always flow even the output logic value is " 0 " .
- ☐ DC power dissipation



Chapter 5

(b) Pseudo-NMOS Logic Array

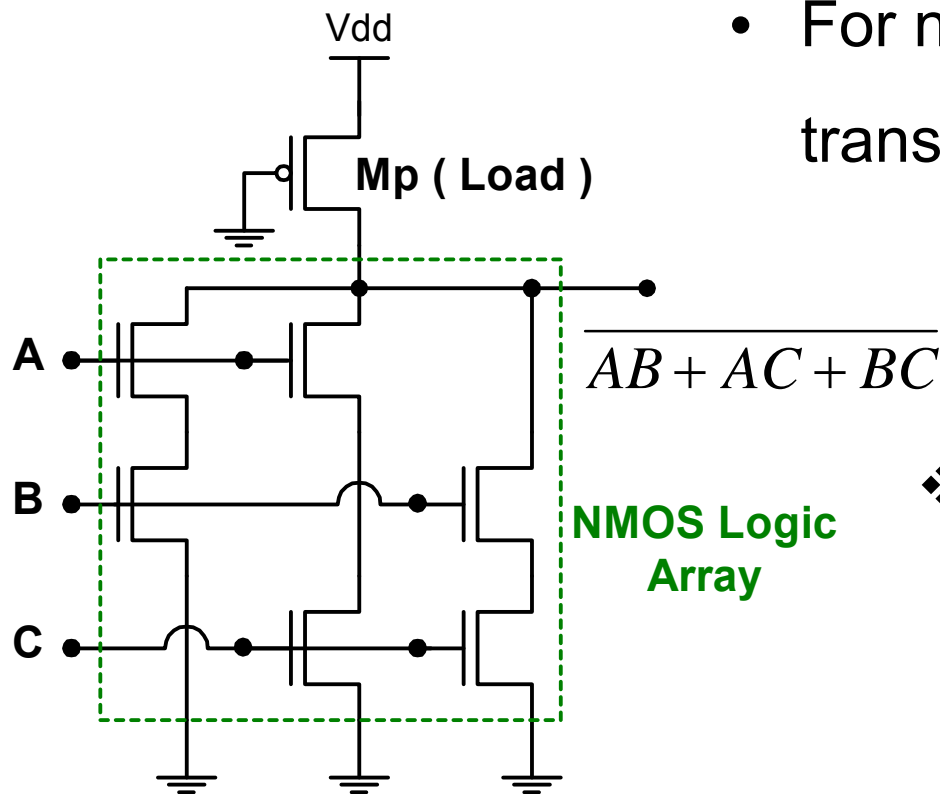

- For n-input gate , need n+1 MOS transistor

❖ Design Pseudo-NMOS logic must consider :

$$\frac{\mu_p \times \frac{W_p}{L_p}}{\mu_n \times \frac{W_n}{L_n * n}} = \frac{1}{10}$$

串聯個數




Chapter 5

5.2 Dynamic Logic Circuit

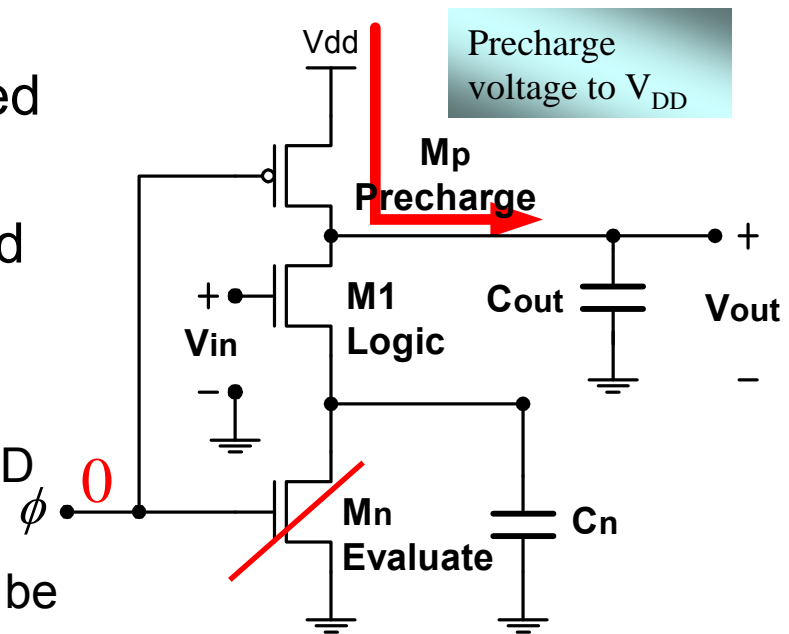(A) Basic Concept :

- As mentioned previously , the static logics have a pull-up and pull-down network . However they are activated at different times .
- The pull-up network can be replaced by a precharge PMOS M_P .
- **Advantages :**
 - i. No direct current path from V_{DD} to GND
→ No DC power dissipation .
 - ii. Speed is enhanced . (transistors can be made wider and input never cause the output pull-up .)



Basic Dynamic NMOS inverter

❖ **Note :** input must be made glitch free .




Chapter 5

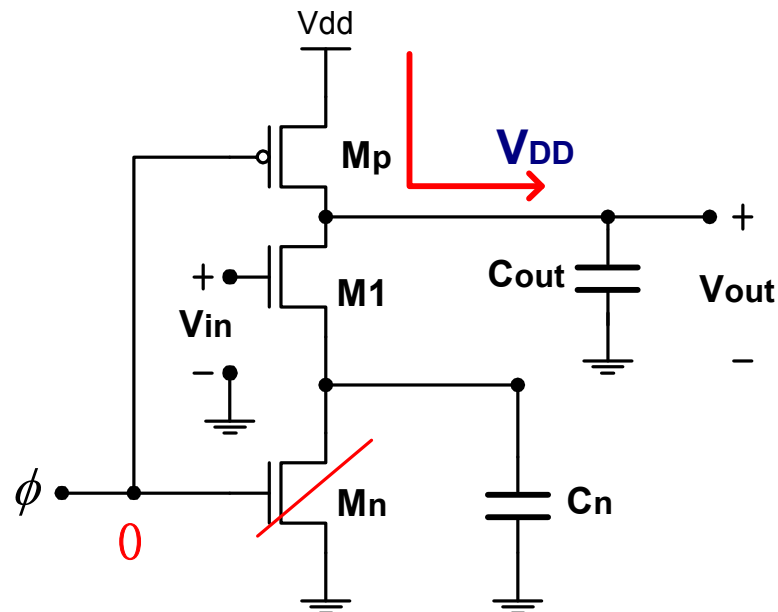(B) Logic operations :


Two phase of operations controlled by clock ϕ

$\phi = 0$: precharge
 $V_{out} = V_{DD}$



PRECHARGE

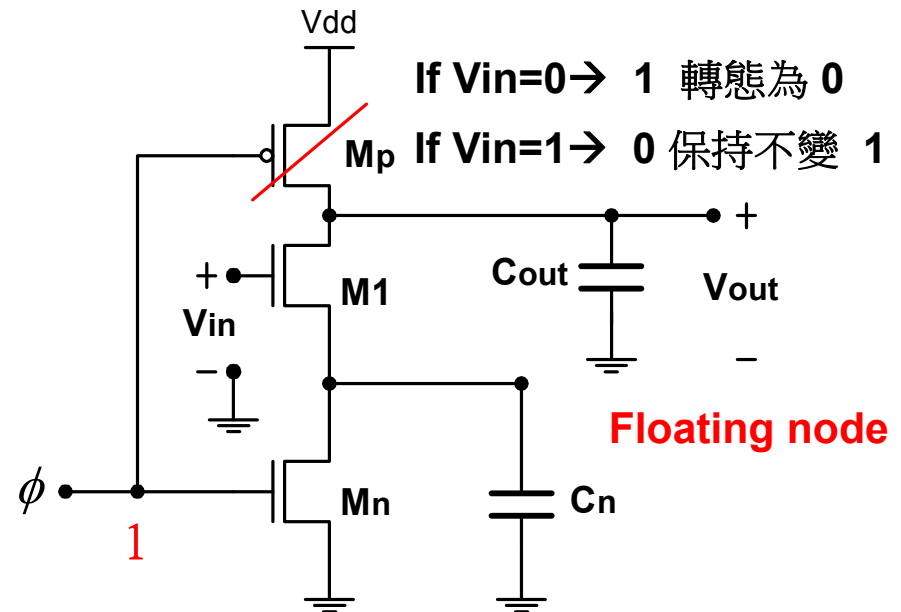
$\phi = 1$: Evaluate
 V_{out} : conditional discharge




EVALUATE
(Conditional Discharge)



Chapter 5

 


PRECHARGE

 

EVALUATE


(Conditional Discharge)

 



Chapter 5

(C) N-Rich Dynamic Logic :

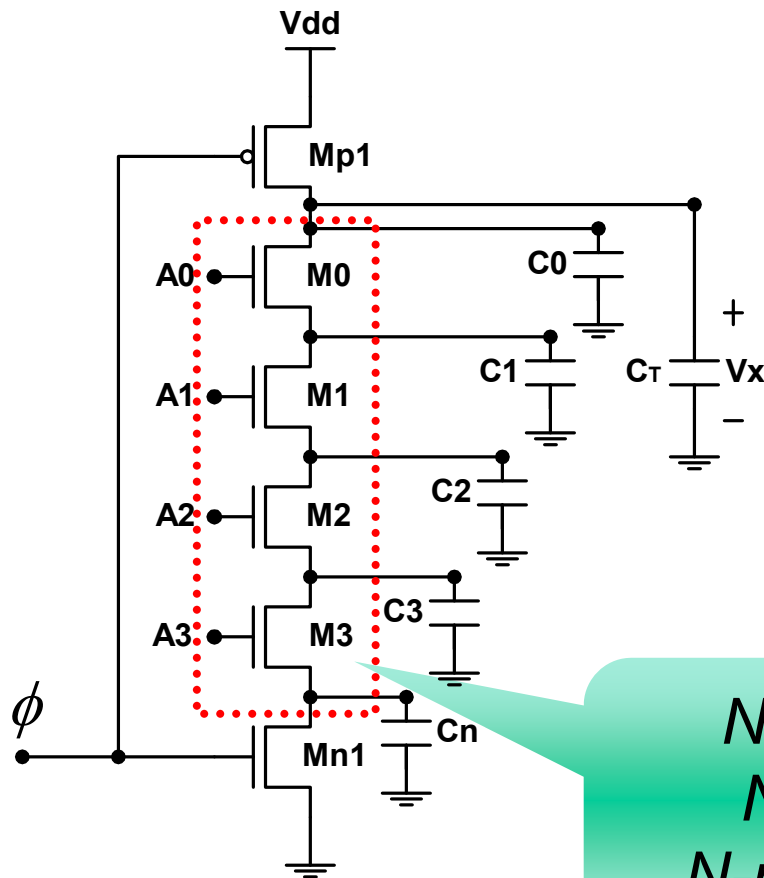


- C_T precharged to V_{DD} during $\phi = 0$ (precharge)
- N-channel logic block stacked with a clocked NMOS may discharge the output to GND during $\phi = 1$ (evaluation)

*N-block
N-tree
N-network*



Chapter 5

(D) P-Rich Dynamic Logic :

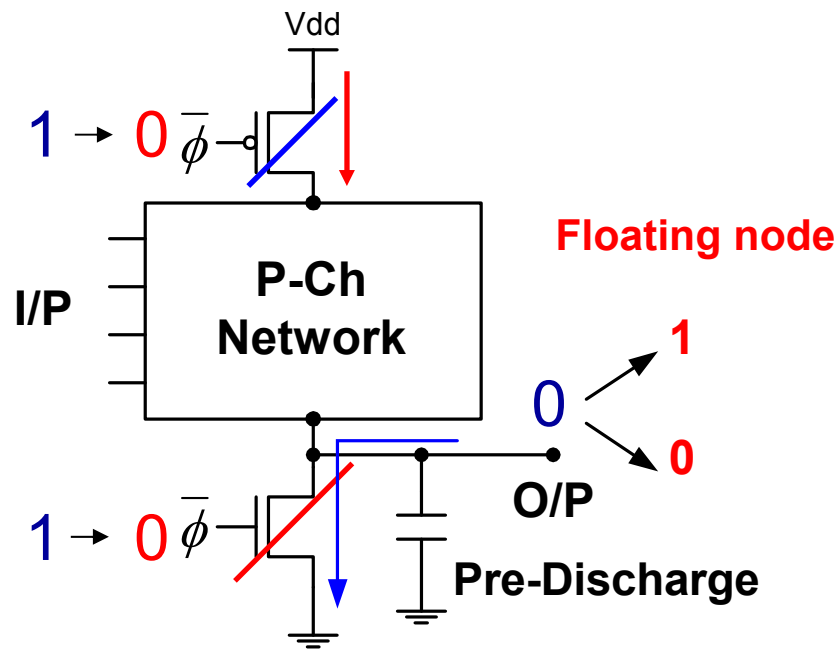





$\phi = 0 (\bar{\phi} = 1)$: Pre-Discharge
O/P precharge to GND .

$\phi = 1 (\bar{\phi} = 0)$: Evaluation
P-Ch network may precharge
the O/P to V_{DD} .



Chapter 5

Example : $\phi = 0 (\bar{\phi} = 1)$ **Precharge**
 $\phi = 1 (\bar{\phi} = 0)$ **Evaluation**

    




Chapter 5

5.2.1 Clock static CMOS Logic

* Static holding , dynamic shifting

(A) Pseudo 1-phase (or 2-phase) Logic

☀ Shift Register

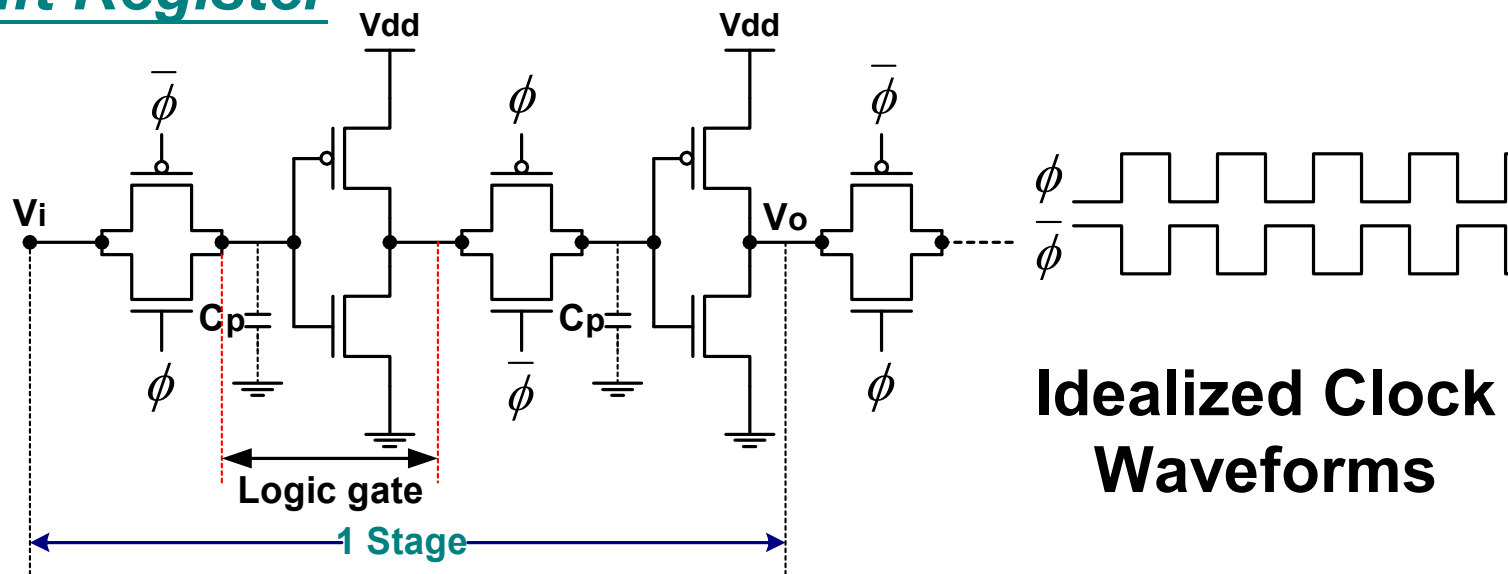


- Data is held in the input capacitance C_p of the inverter (or static logic gate) temporarily , Not Static Holding .
- Not race free if clock skew exists .
- Simpler structure than the fully static shift register .




Chapter 5

Latch Concept

Positive-Polarity Latch

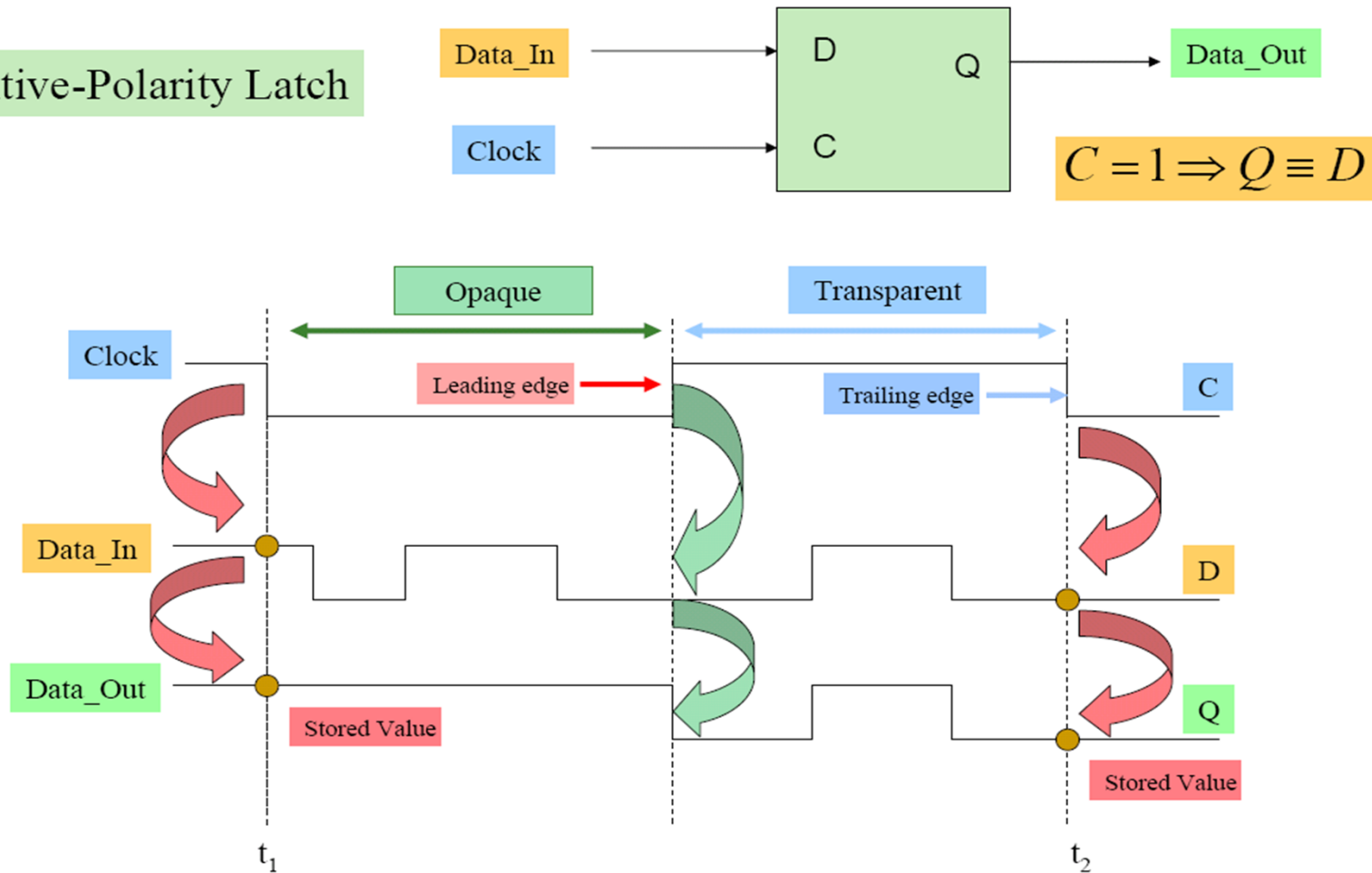


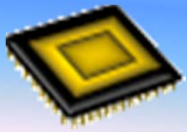


Chapter 5

Latch—Bistable latch

➤ The cross-coupling of two inverters

- bistable circuit
- 0 or 1

 
 






Chapter 5


Latch VS. FlipFlop

- ❑ Latch stores data when clock is low

  


- ❑ Register stores data when clock rises

  

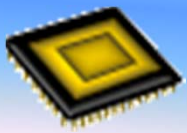

Chapter 5

✧ Basic Transmission Gates Latch

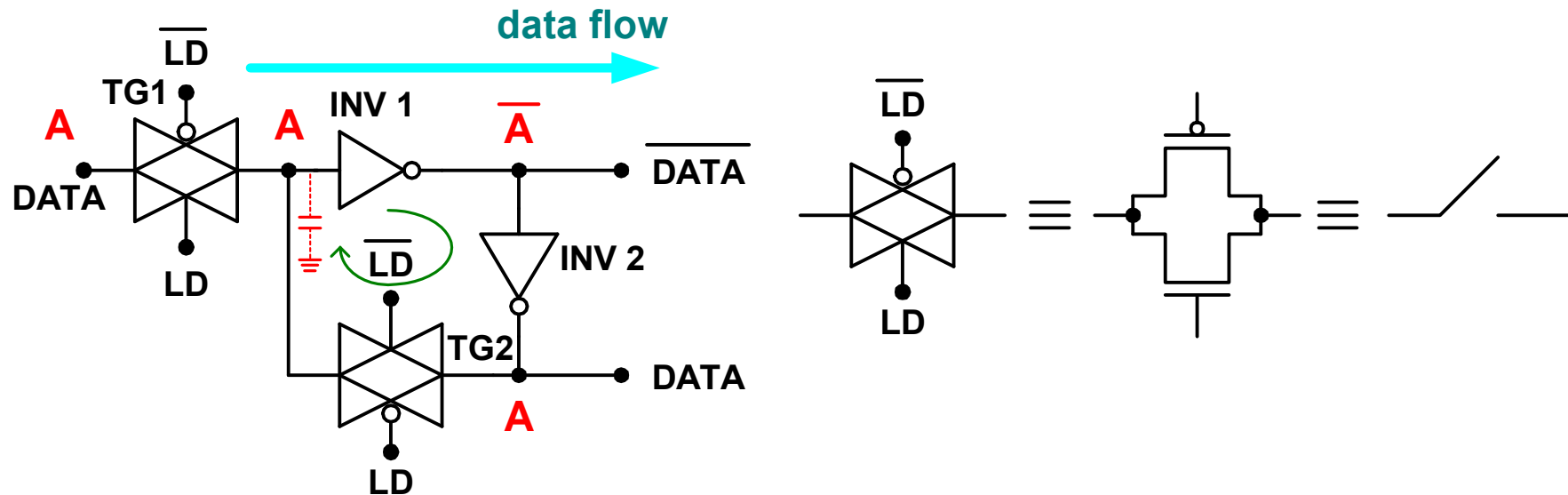



- TG2 is in the feedback loop
- Load signal $LD=1$, TG1 allows data enter the latch , TG2 is open .
 $LD=0$, TG1 is open , TG2 provides feedback .



Chapter 5


★ Master - Slave D type Flip Flop

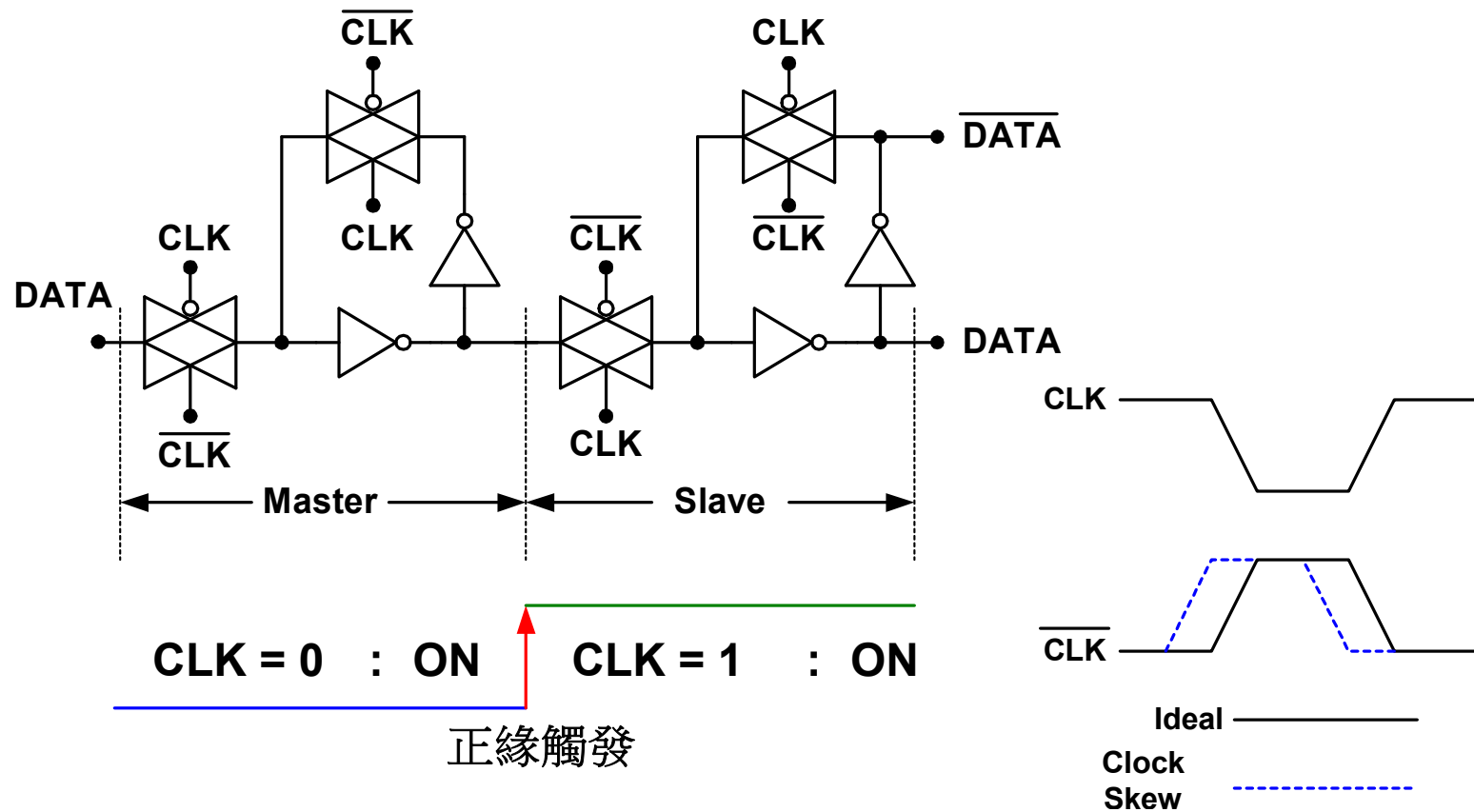

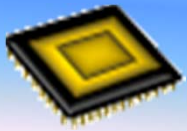

Chapter 5

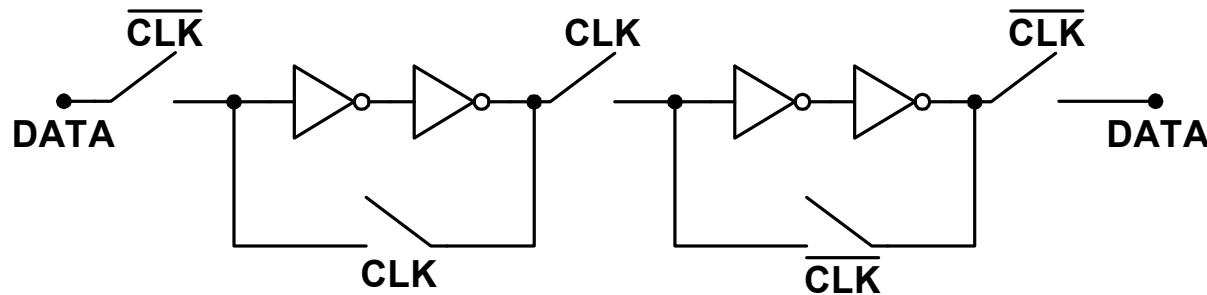- CLK=0 , DATA pass the master stage and previous data is latched by the slave stage .
- CLK=1 , DATA latched by the master stage and sent into the slave stage .
- Could race if CLK and $\overline{\text{CLK}}$ overlaps → Both master and slave are turned on .




→ Clock skew race problem



Chapter 5

✦ Master - Slave D type Flip Flop Improved Version

- Improve latch stability

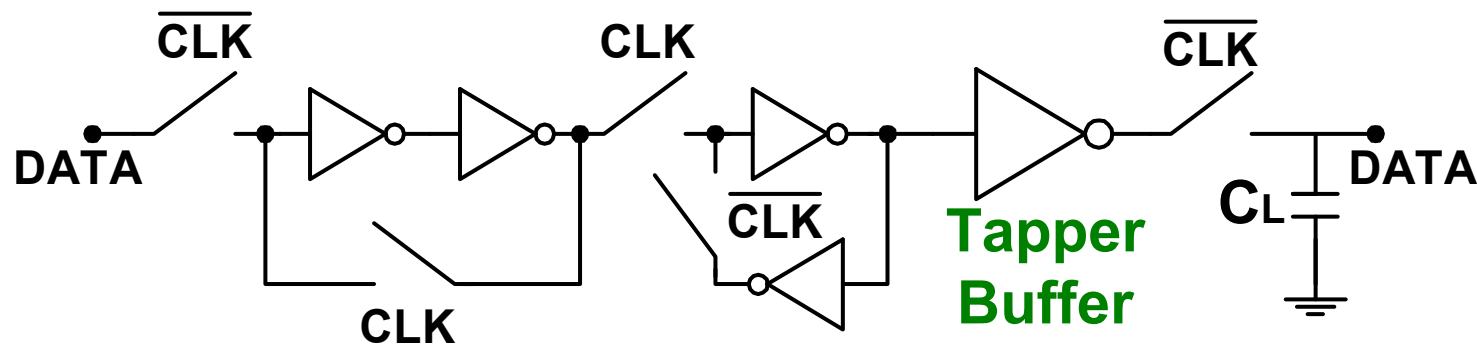

* Clock skew → race




The diagram illustrates a 4-bit ripple-carry adder implemented using four 4-bit multiplexers. The inputs are two 4-bit numbers, A and B , and a carry-in C_{in} . The outputs are the 4-bit sum S and the carry-out C_{out} .

- Multiplexer 1 (Leftmost):** Selects between A and B based on the carry-in C_{in} . Its output is the first bit of the sum S_0 .
- Multiplexer 2:** Selects between A and B based on the carry-in C_{in} . Its output is the first bit of the sum S_1 .
- Multiplexer 3:** Selects between A and B based on the carry-in C_{in} . Its output is the first bit of the sum S_2 .
- Multiplexer 4 (Rightmost):** Selects between A and B based on the carry-in C_{in} . Its output is the first bit of the sum S_3 .

The carry propagation is implemented using a chain of logic gates:


- The carry-in C_{in} is connected to the C_{in} input of the first multiplexer.
- The carry-out of the first multiplexer is connected to the C_{in} input of the second multiplexer.
- The carry-out of the second multiplexer is connected to the C_{in} input of the third multiplexer.
- The carry-out of the third multiplexer is connected to the C_{in} input of the fourth multiplexer.
- The carry-out of the fourth multiplexer is the final carry-out C_{out} .

- VLSI 5-40

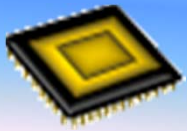

Chapter 5

✧ Toggle Flip-Flop

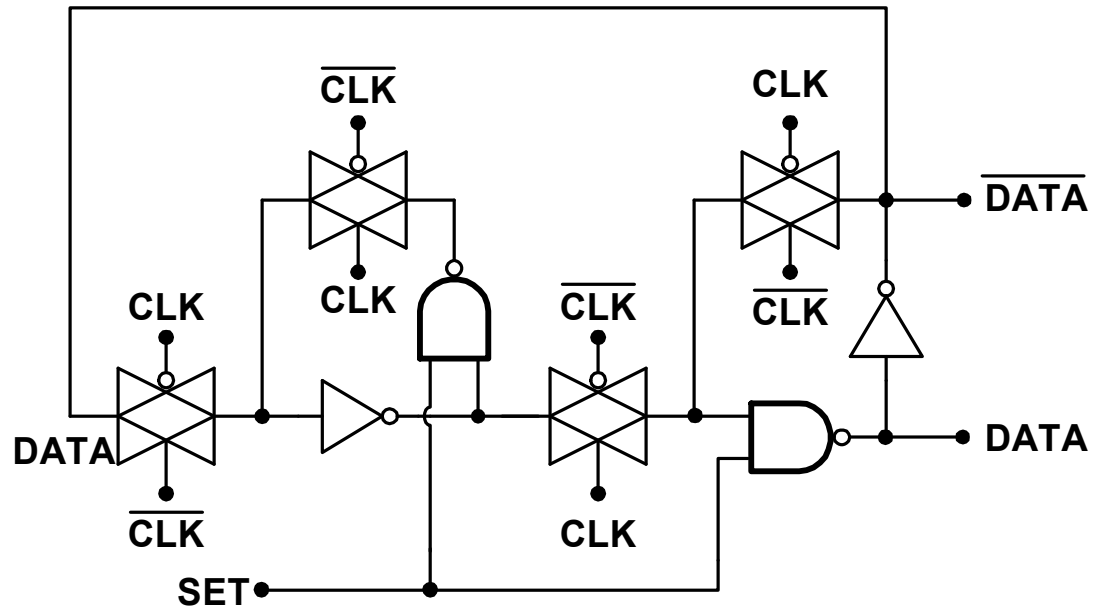

- $DATA(t) = \overline{DATA}(t-1)$
- Operation is controlled by CLK and \overline{CLK}
- SET allows an initial state set
SET=0 : Set data $DATA=1$, $\overline{DATA} = 0$




Chapter 5

✧ JK Master-Slave Flip-Flop

- JK F/F is obtained by combining the input with feedback

$$Q(t+1) = J\bar{Q} + \bar{K}Q$$

J	K	$Q(t+1)$
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}

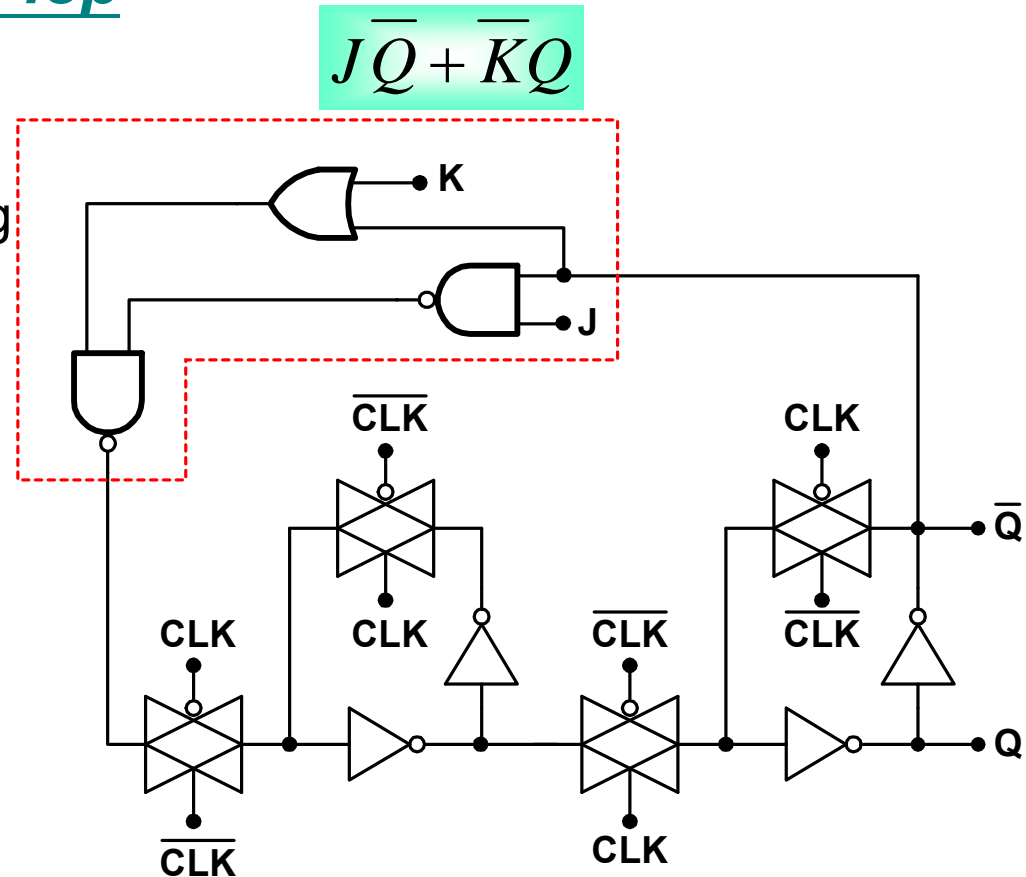





Chapter 5

(B) C²-MOS (Clocked CMOS) Logic


Version 1 :

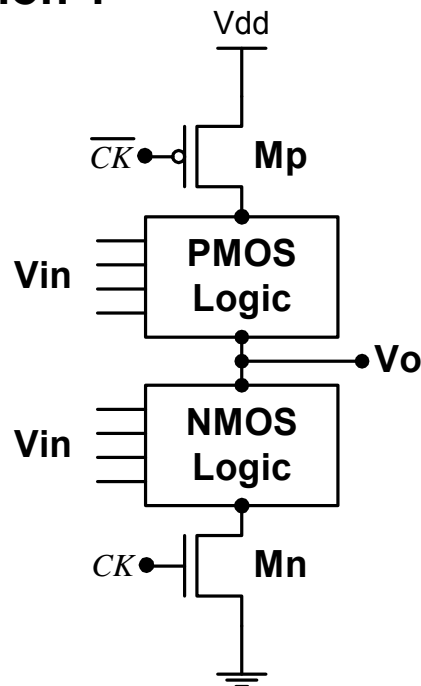

Version 2 :



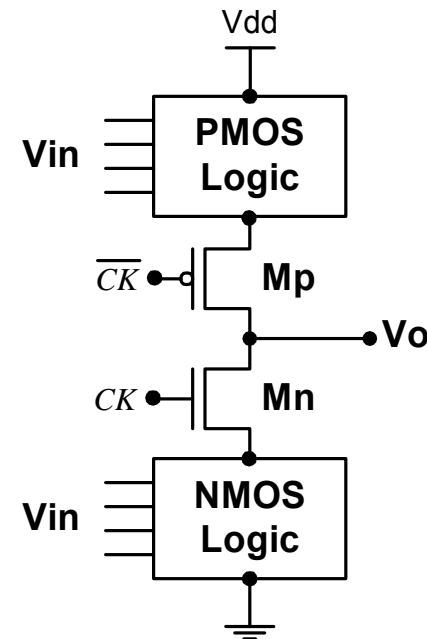


- CK=1 : Active ; CK=0 : Disable
- Mp , Mn Switching or isolating devices
- Suitable for FF construct

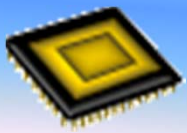

Chapter 5

✧ C²-MOS Inverter (Latch)

  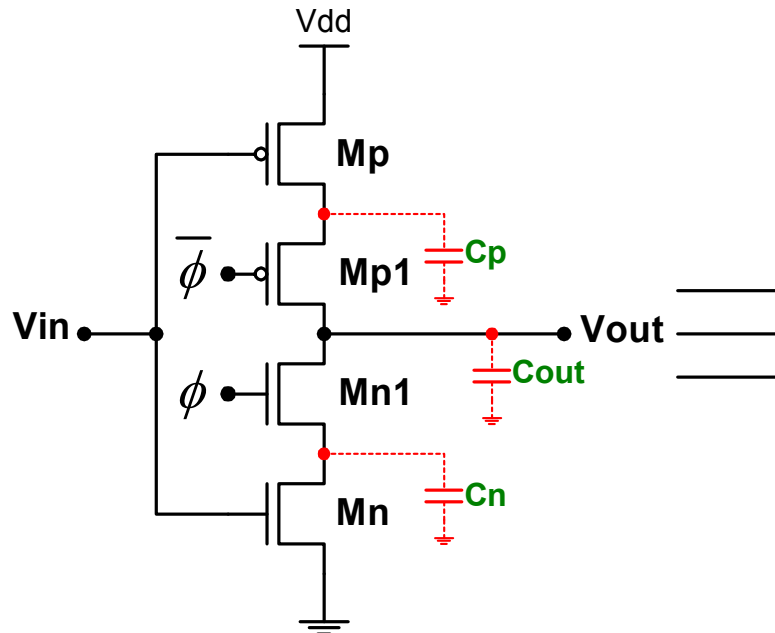

- C²-MOS Latch has better clock skew race immunity than transmission gate latch
- (Homework : shown by SPICE)




Chapter 5


☀ Charge Redistribution Problem (1/2)

Version 1 :


Active

 

Disable

 

Disable with V_{in} changing

 

Charge
Redistribution




Chapter 5


★ Charge Redistribution Problem (2/2)

Version 2 :


Active

 

Disable

 

Disable with V_{in} changing

 


No Charge Redistribution

- Version 1 has the charge redistribution problem due to incomplete output isolation
- For safety design , Version 2 is recommended



Chapter 5

✧ D-type F/F

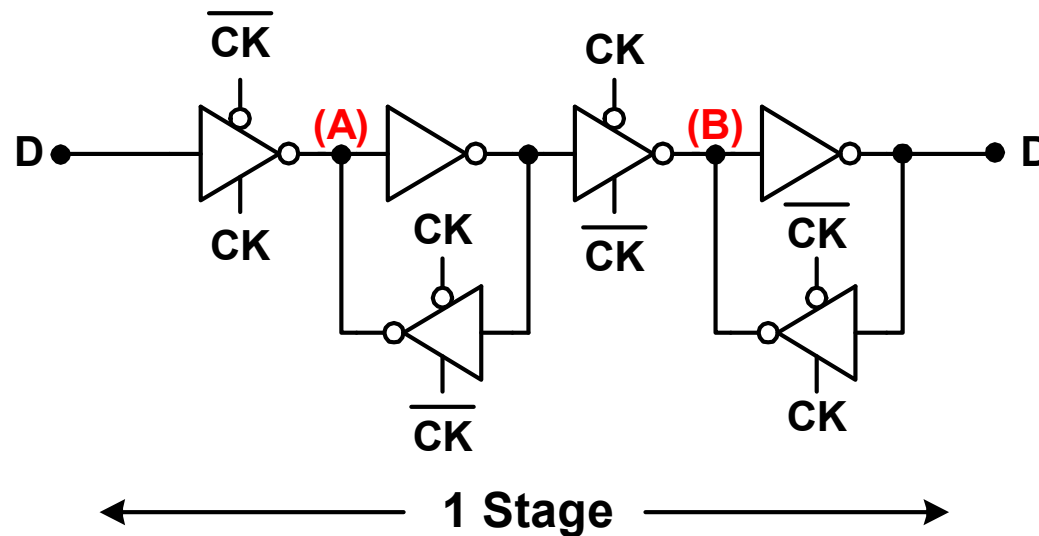

- Node (A) and (B) are sensitive nodes . If charge redistribution occurs at these two nodes before latch forms
➔ Error generation.





Chapter 5

5.2.2 Problems of Dynamic CMOS Logic

- Because of precharging at the output node, dynamic CMOS techniques are common to the following Limitations

(A) Charge Redistribution : (Charge Sharing)

- The O/P signal of dynamic CMOS logic rely on the capacitance storage
- As Input signals variation charge redistribution between output capacitance C_0 and parasitic capacitance C_p . V_{out} lose it's value

  



Chapter 5

(B) Leakage Current and Noise Margin


- Due to leakage of storage node , power supply variation
- Input may be altered from ideal 0 and V_{DD}
 - ➔ NMOS logic section input may driven to weak inversion
 - ➔ Leakage
- Serious problem in low frequency operation
 - ➔ Dynamic ckt requires a lower bound on the speed of operation frequency



Chapter 5

(C) Internal Delay Problem (Internal Race)

1. During CK=0 (Precharge)
N1 and N2 are charged to V_{DD}
 2. During CK=1 (Evaluation)
Internal delay in gate1 will cause N1 from 1 \rightarrow 0
 - The delay time can cause an incorrect discharge of N2
 - ∴ During CK=1 and while N1 is “1”, there is a direct path from N2 to GND
 - Precharged information in N2 is loss by this internal delay of gate1
- ❖ Solved by using :
- Domino Logic
 - N-P pair
 - Zipper CMOS Logic
 - 4-phase dynamic logic

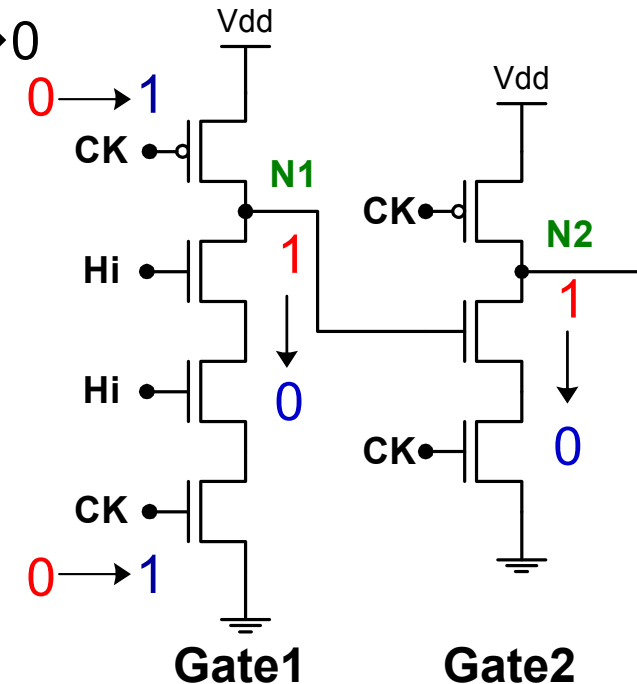





Chapter 5

5.2.3 CMOS Domino Circuit [Bell lab] (1/3)

Ref : R.H. Krambeck , C.M. Lee , H.F. Stephen Law “ How speed Compact Circuits with CMOS ” IEEE JSSC , Vol. sc-17 , No.3
P.P.614 ~ 619 , 1982

- Basic Cell :

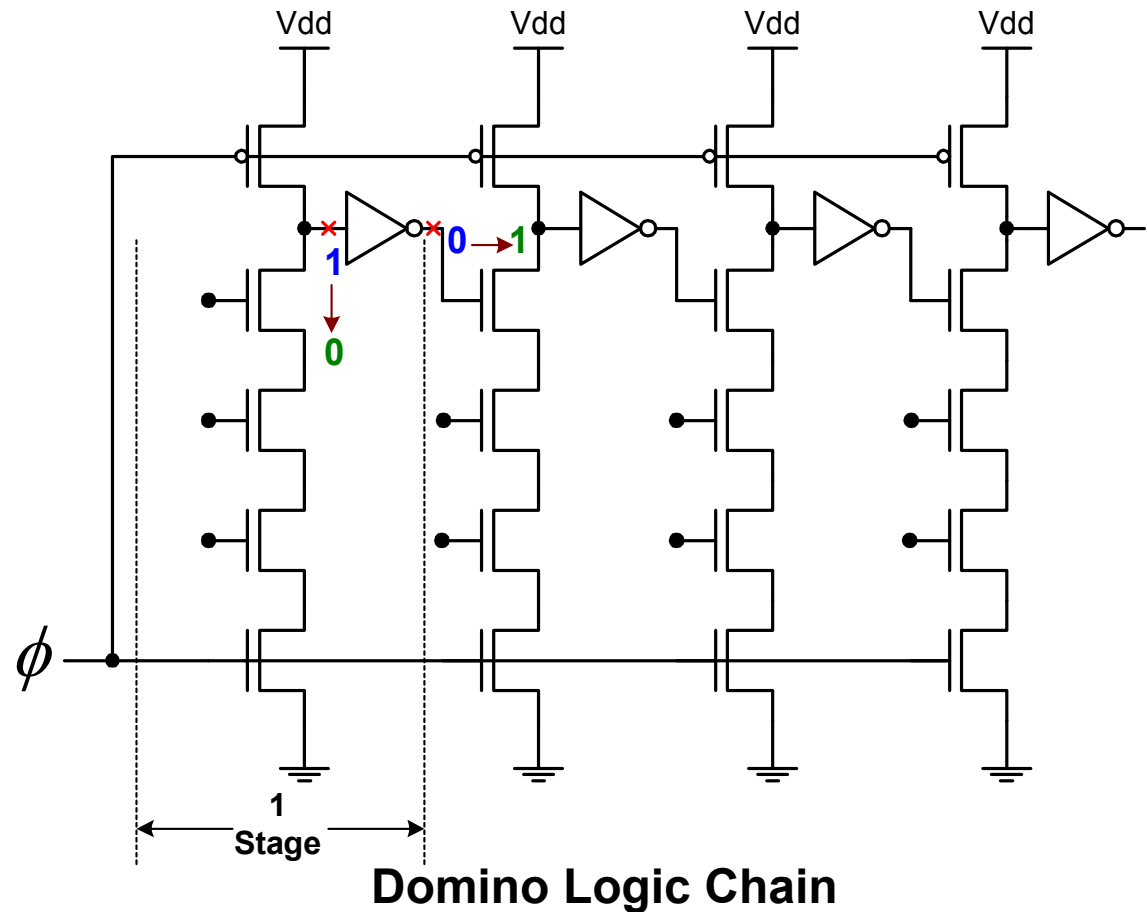 



Chapter 5

CMOS Domino Circuit [Bell lab] (2/3)

- Consist of a pair of a dynamic CMOS and a static inverter
- **$\psi=0$: Precharge**
 - Dynamic gate is charged to V_{DD} , so that the static inverter is discharge to GND
 - ➔ All N-rich nodes driven by domino circuit is low
 - ➔ All NMOS transistor are off
- **$\psi=1$: Evaluation**
 - Domino circuit output makes single transition from Low to High or keeps to Low
 - ➔ No glitches (internal race) and all gates can be switched from precharge to evaluation with same clock edge



Chapter 5


CMOS Domino Circuit [Bell lab] (3/3)

Advantages :

- 1. Faster than the corresponding static CMOS circuit
- 2. Low power dissipation
- 3. Full Pull-Down current is available
- 4. Small load cap
- 5. Use of single clock edge to activate the circuit
- 6. No internal race problem(glitch free operation)

Disadvantages :

- 1. Lack of inverted output→ Decrease logic flexibility and therefore requires more transistors for a given logic function
EX: No way to implement XOR gate
- 2. Charge redistribution problem

 


Chapter 5

5.2.4 Modified Domino Logic -N-P pair Dynamic Circuit (1/3)

Ref : IEEE JSSC , Vol. sc-19 , P.P. 263 , Apr. 1984

Principles :

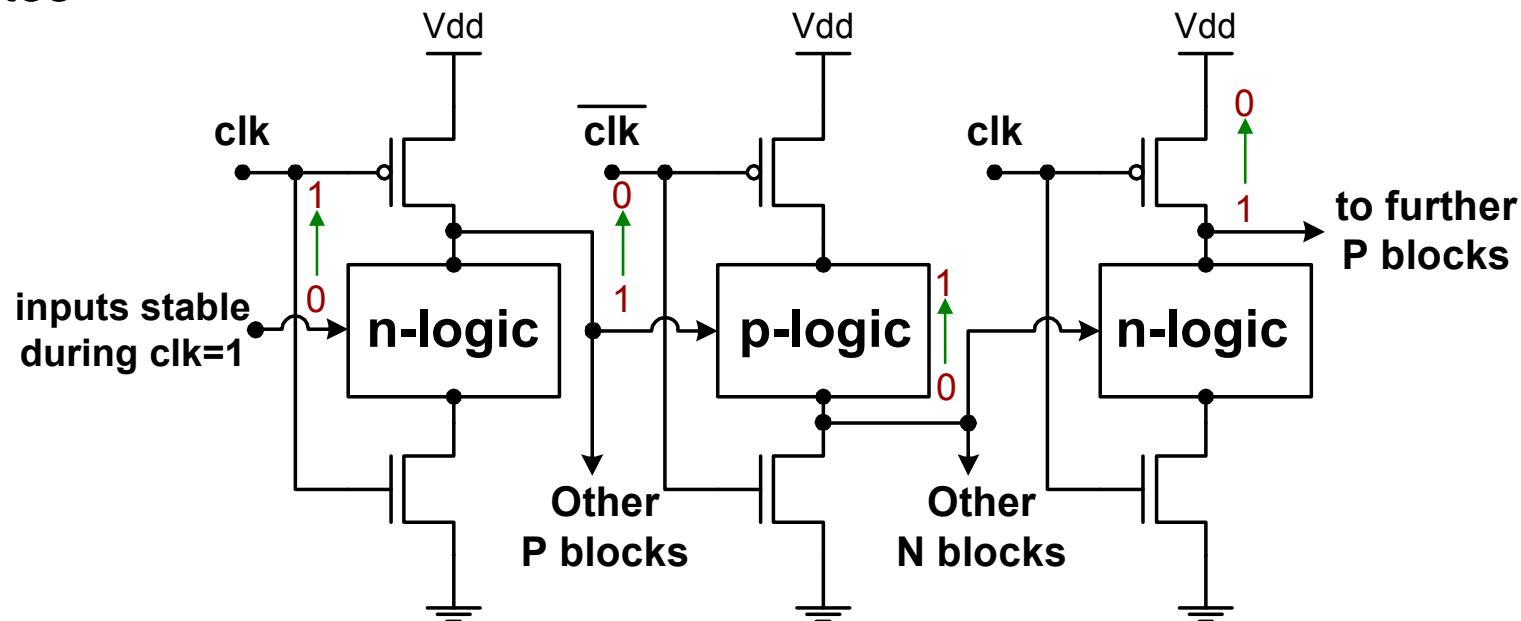1. Remove domino buffer (inverter)
2. **P-rich** gate can be directly drive an N-rich gate without glitch problem and vice versa → consist of alternating the two types of CMOS dynamic logic gates





The diagram illustrates a 3-stage pipeline with crossbar interconnects. Each stage consists of an **n-logic** block followed by a **p-logic** block. The pipeline is controlled by a clock signal **clk**. The input to the first **n-logic** block is labeled "inputs stable during clk=1". The output of the first **n-logic** block is connected to the input of the first **p-logic** block. The output of the first **p-logic** block is connected to the input of the second **n-logic** block. The output of the second **n-logic** block is connected to the input of the second **p-logic** block. The output of the second **p-logic** block is connected to the input of the third **n-logic** block. The output of the third **n-logic** block is labeled "to further P blocks". The circuit includes crossbar interconnects that allow for flexible routing between the logic blocks. The diagram also shows the connection to **Other N blocks** and **Other P blocks** and the power supply **Vdd**.



Chapter 5

Modified Domino Logic -N-P pair Dynamic Circuit (3/3)

■ Advantages :

- 1. Smaller area than fully static gates
- 2. Smaller parasitic cap.
- 3. Glitch free operation → No internal race problem
- 4. Inverted output is available

■ Disadvantages :

- 1. Still has the charge redistribution problem
- 2. Low operation speed in PMOS blocks

➤ How to Avoid Charge Redistribution Problem ?



Chapter 5


5.2.5 Modified Domino CMOS with Reduced Charge Redistribution

Ref :

- IEEE JSSC , Vol. sc-21 , P.P. 304 ~ 306 , Apr. 1986
- IEEE JSSC , Vol. sc-21 , P.P. 786 ~ 793 , Aug. 1986
- IEEE JSSC , Vol. sc-19 , P.P. 263 ~ 266 , Apr. 1984

(A) Internal Node Precharge

- Mp1 is used to precharge the internal node (2) to avoid charge redistribution between node (2) and (1)
- Charge redistribution can be more eliminated by
 - a. Carefully control of layout dependent capacitance
 - b. Increase output inverter size (i.e. increase C_x)
- Internal node precharge may slow down the discharge operation in the Evaluation phase

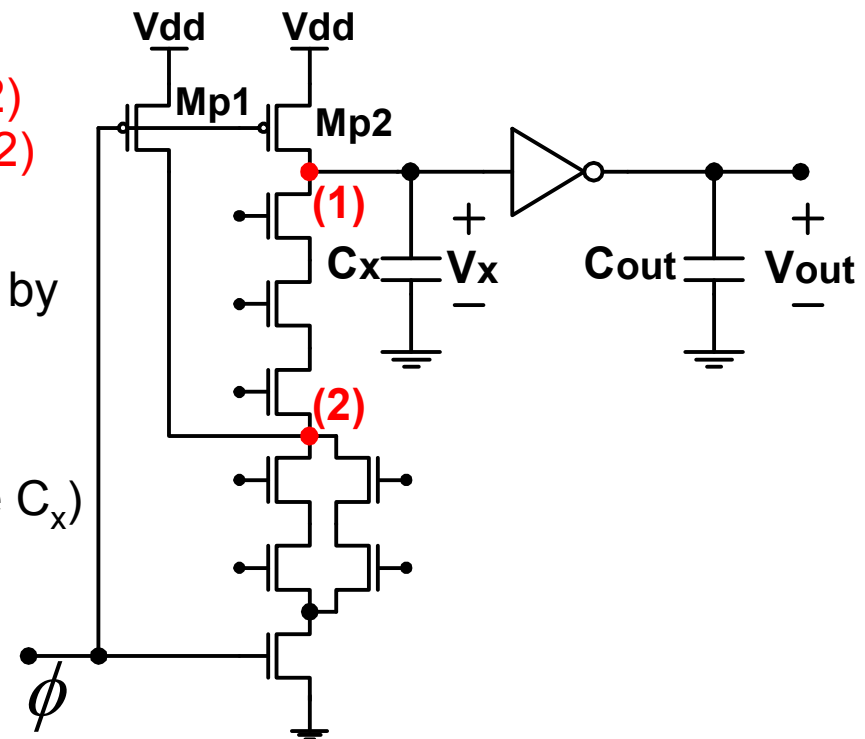




Chapter 5

(B) Static Domino gate

- Domino gate may be made static by adding a weak PMOS (small W/L ratio)
- ❑ Static capability to allow lower frequency operation or to avoid the risk of storing data on floating nodes
- ❑ Pull-up time could be slower than pull-down speed
- ❑ Can moderate the charge redistribution problem and improve noise margin
- ❑ W/L of the Mp must be low to keep a low DC power dissipation (EX : L=10um , W=2um)
- ❑ Clocked PMOS can be omitted
- ❑ Not Valid For High Speed Circuit

Charge Compensation Circuit

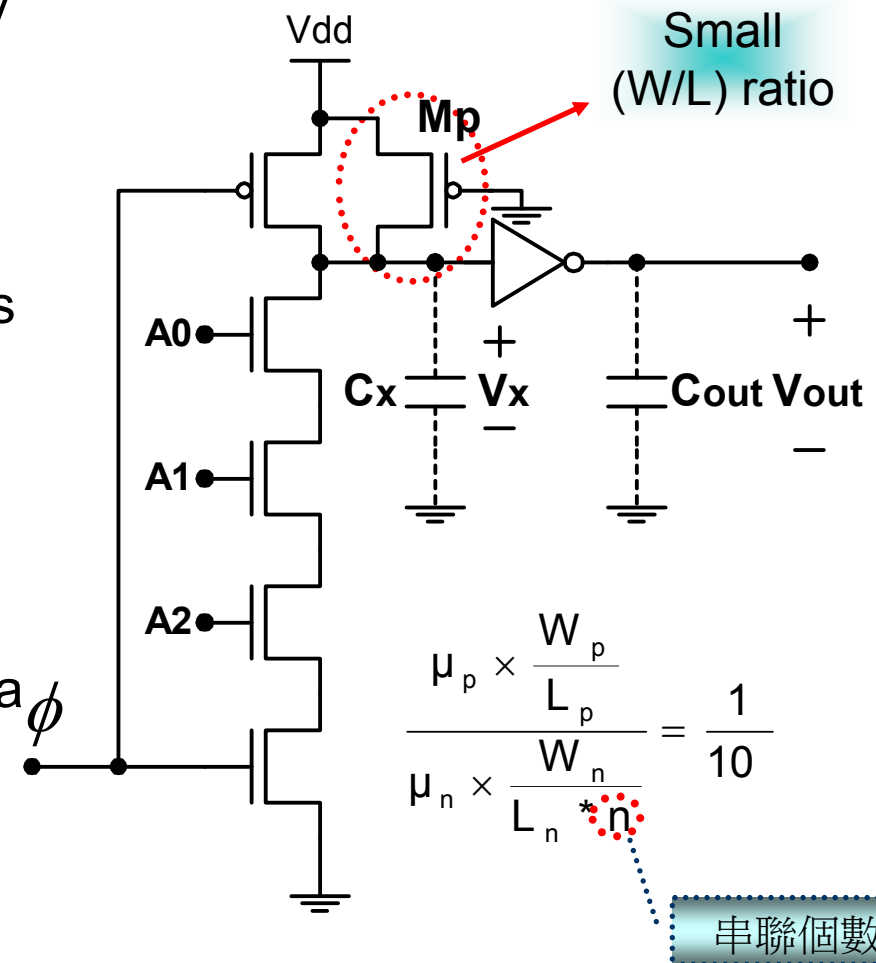




Chapter 5

(C) Feedback PMOS Charge Compensation Circuit

Alternate Charge Compensation Scheme

- Domino gate may be made latching by placing a weak PMOS feedback transistor
- The charge compensation scheme can effectively solve the charge redistribution problem, but the operating speed is decreased as compared to standard domino
- Standard domino with series NMOS higher than 5 is unable. Due to charge redistribution.

Solution : Zipper CMOS

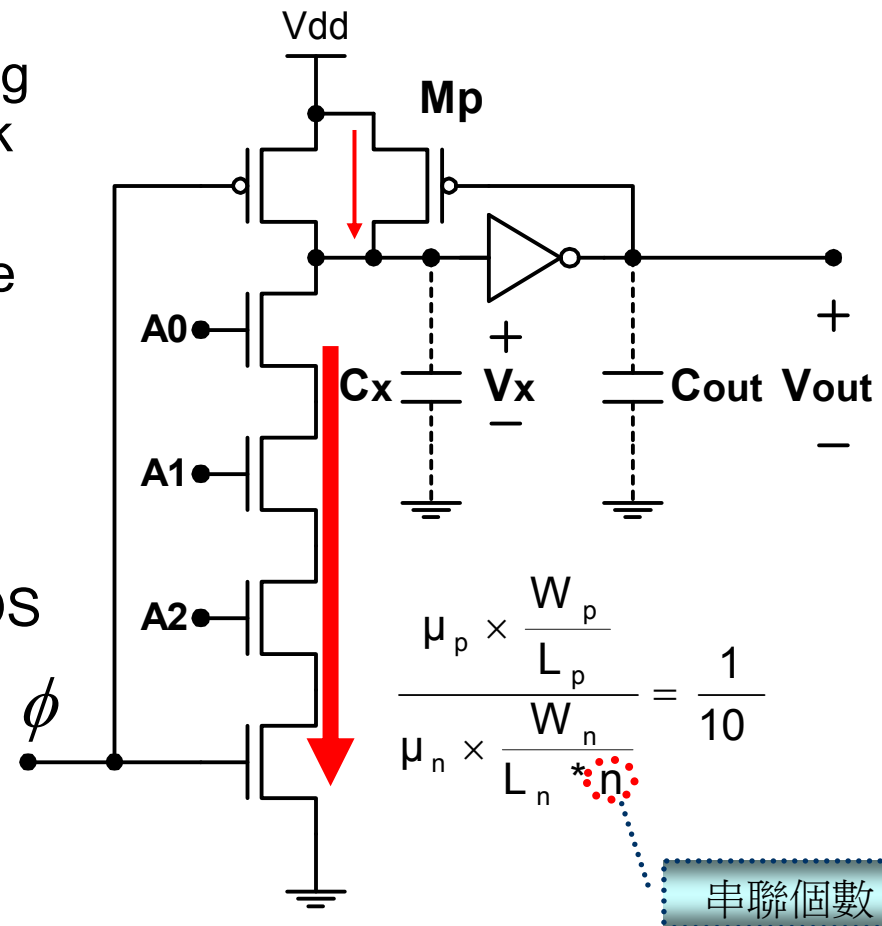



Chapter 5



5.2.6 Zipper CMOS (1/3)

- The gate connection is similar as the N-P pair domino structure
- The precharge PMOS in the N-block and the predischage NMOS in the P-block is controlled by a special Zipper clock ψ_{1X} , ψ_{2X} where the voltage swing of ψ_{1X} and ψ_{2X} are
$$\psi_{1X} = 0 \text{ V} \sim V_{DD} - |V_{TP}| ; \psi_{2X} = |V_{TN}| \sim V_{DD}$$
- In the Evaluation phase $\psi_1 = V_{DD} ; \psi_{1X} = V_{DD} - |V_{TP}| ; \psi_2 = 0 \text{ V} ; \psi_{2X} = |V_{TN}|$. The PMOS Mp1 controlled by ψ_{1X} is nearly turn-on while the Zipper clock $\psi_{1X} = V_{DD} - |V_{TP}|$, If the charge redistribution is occurred at node A , V_A is pulled-down , Mp1 is turned-on by $\psi_1 = (V_{DD} - |V_{TP}|)$ to precharge node A to V_{DD} → No charge redistribution



Chapter 5

Zipper CMOS (2/3)

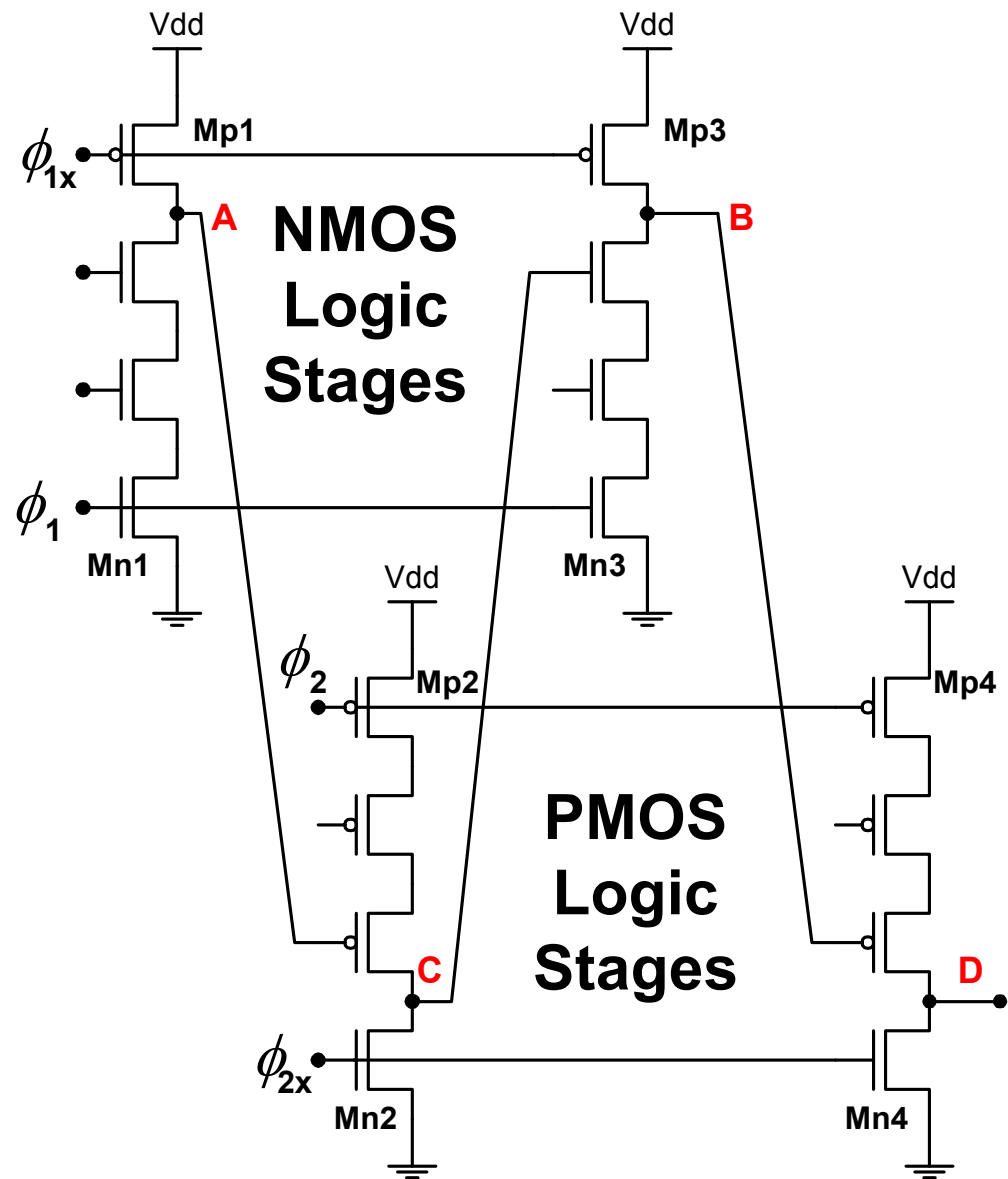 



Chapter 5

Zipper CMOS (3/3)

■ Advantages :

- 1. No charge redistribution problem
- 2. No internal race problem if carefully design
- 3. No DC power dissipation
- 4. The operating speed is compare to the standard domino

■ Disadvantages :

- Requires special clock generator for Zipper CMOS logic , and more clock line




Chapter 5

5.2.7 NORA – CMOS pipelined circuits


Ref : IEEE JSSC , Vol. sc-18 , P.P. 261 ~ 266 , June . 1983

- NO RAce circuit

(A) Basic Concept of Dynamic Latch

 


(a) General Structure

 

(b) Clocking

- Each section contains two units : logic unit and latch unit
- Latch unit as the pipeline – section control unit

 

Chapter 5

(B) NORA Circuit (1/3)


ψ - section :

$\psi=0$ Precharge ; Data out is hold

$\psi=1$ Evaluation ; Data out Valid


Configuration :

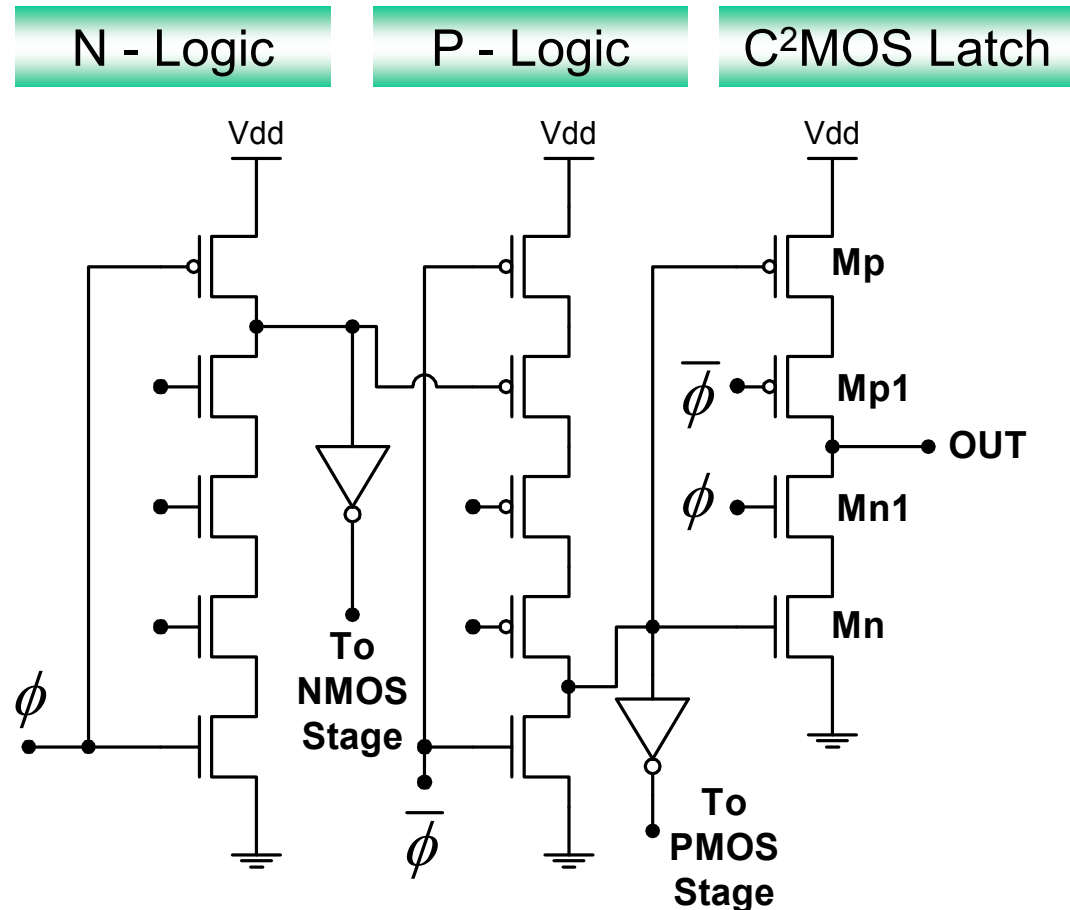1. Direct couple of N-P dynamic logic blocks
2. Indirect couple of same type logic
→ Domino logic
3. Data out must stored in C²MOS latch



(a) NORA ψ - section

\	Logic	Latch
$\phi = 0$	Precharge	OFF
$\phi = 1$	Evaluation	ON

 

Chapter 5

(B) NORA Circuit (2/3)

N - Logic

P - Logic


C²MOS Latch

$\bar{\psi}$ - section :

$\psi=1$ Precharge ; Data out is hold

$\psi=0$ Evaluation ; Data out Valid

\	Logic	Latch
$\phi = 1$	Precharge	OFF
$\phi = 0$	Evaluation	ON

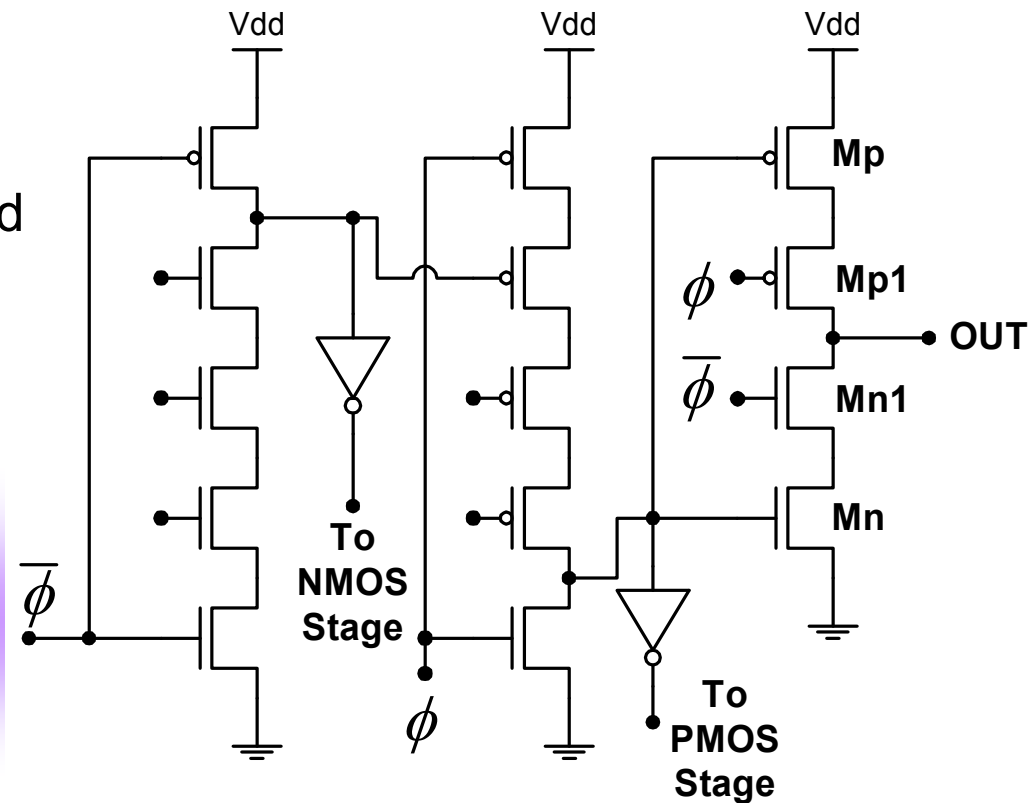


(b) NORA $\bar{\psi}$ - section



Chapter 5


(B) NORA Circuit (3/3)

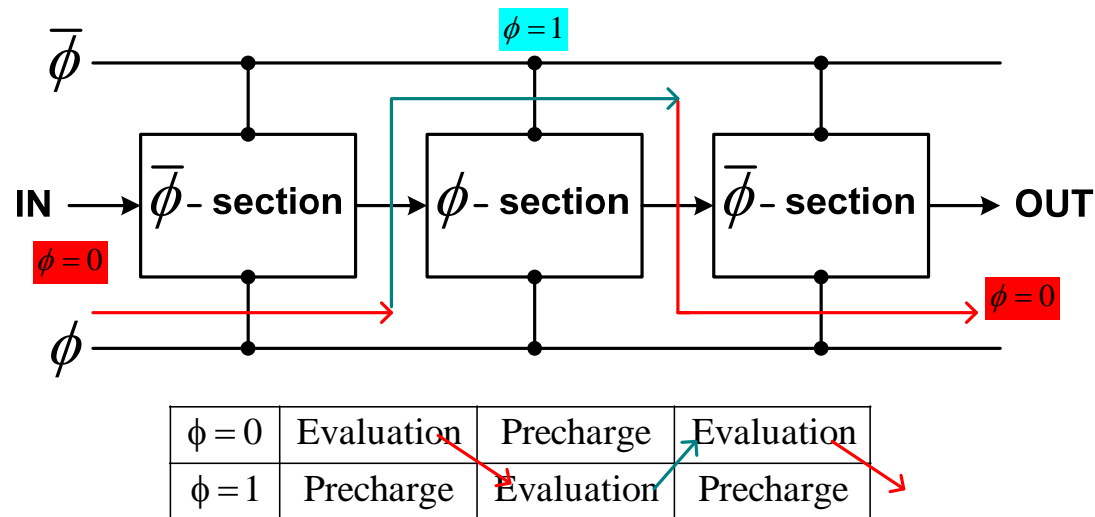

NORA Cascades

■ **Characteristic :**

- Inverted and noninverted signals are provided
- N-P (P-N) sequence can be of arbitrary depth
- Data flows and latched in this way from $\bar{\psi} \rightarrow \psi \rightarrow \bar{\psi}$ as a pipeline structure

 

Chapter 5

(C) NORA race free properties and logic composition rules

(—) Internal Delay Race free Property (1/2)

■ **Definition :**

- The capability of the dynamic block to keep its precharge signal during the delay time of the previous blocks to set up the internal inputs

■ **Properties :**

- a. During the precharge : " Precharge to cut-off the corresponding input MOS "
- b. During the Evaluation : " Internal inputs are Glitch-Free " (can make only are transition)




Chapter 5

(—) Internal Delay Race free Property (2/2)

■ **Composition Rules :**

- a. The number of static inversion gates between two N-P (P-N) dynamic block is EVEN or 0
- b. The number of static inversion gates between two N-N (P-P) dynamic block is ODD
- c. For mixing dynamic blocks with static CMOS , the static must be put between dynamic blocks and C²MOS latch . Static functions can be used after the C²MOS stage .

 

Chapter 5

(二) Clock Race Free (1/11)

■ **Definition :**

- NORA pipelined section keeps its output results in spite of clock skew (i.e. high – high or low – low overlaps) . The latch signal should not be altered by precharge signal or by input variations




Chapter 5

(二) Clock Race Free (2/11)

★ Case1 : Precharge Racefree (1/3)

 (The case that the precharge signal is altered by the input)



$\psi=0$, $N1=1 \Rightarrow T2 \text{ OFF} , T4 \text{ OFF}$
OUT can keep its value even if
 $\bar{\psi}=0$ (T3 ON)

Even Inversion




Chapter 5

(二) Clock Race Free (3/11)


★ Case1 : Precharge Racefree (2/3)

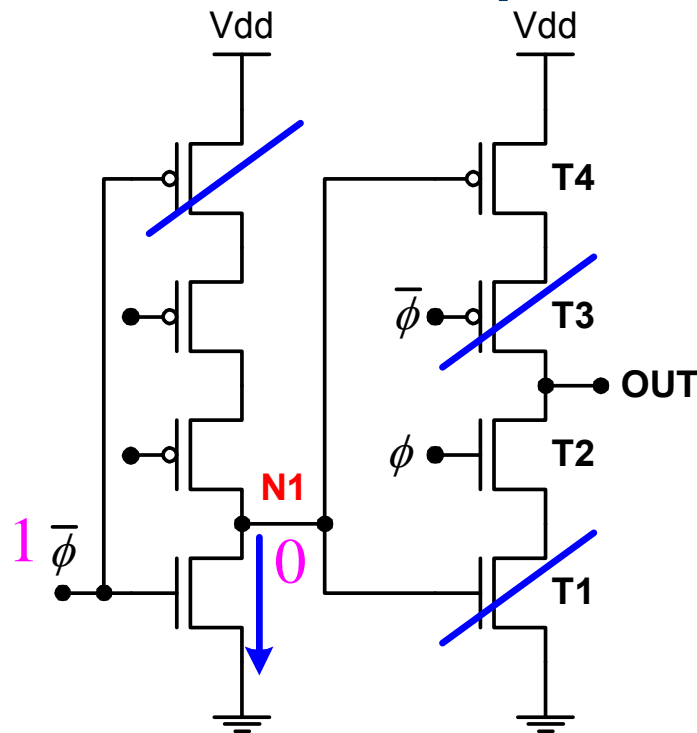(The case that the precharge signal is altered by the input)



$\bar{\psi}=1$, $N1=0 \rightarrow T3$ OFF , $T1$ OFF
OUT can keep its value even if
 $\psi=1$ ($T2$ ON)

Even Inversion

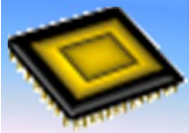

Chapter 5

(二) Clock Race Free (4/11)

✦ Case1 : Precharge Racefree (3/3)

■ Composition Rules :


- There is an even number of inversions between the last dynamic block and the C²MOS output latch
- There could be signal races for clock signals with very slow rise and fall time (10 to 20 times the gate delay) !



Chapter 5

(二) Clock Race Free (5/11)

☀ Case2 : Input Variation Racefree (1/3)

 

Even Inversion

- The case that the precharge signal is kept by inputs (ψ —section)

OUT=0 , N1=1

OUT could be changed only when N1=0 and $\psi=0$

- Precharge signal ($\psi=1$ and $\psi=0$) has no effect on the OUT signal (in the ψ — section)
- Consider the input (ψ — section) :

N3 could be changed only when N2 : 0 \rightarrow 1 and $\psi=1$

As $\psi=1$; N2 : 0 \rightarrow 1 \rightarrow Impossible !

\rightarrow Input variation Race free




Chapter 5

(二) Clock Race Free (6/11)

☀ Case2 : Input Variation Racefree (2/3)

 ■ The case that the precharge signal is kept by inputs (ψ —section)



Even Inversion

OUT=1 , N1=0

OUT could be changed only
when N1=1 and $\psi=1$

- Precharge signal ($\psi=1$ and $\bar{\psi}=0$) has no effect on the OUT signal (in the ψ — section)
- Consider the input ($\bar{\psi}$ — section) :

N3 could be changed only
when N2 : 1 \rightarrow 0 and $\psi=0$

As $\psi=0$; N2 : 1 \rightarrow 0 \rightarrow Impossible !

\rightarrow Input variation Race free



Chapter 5

(二) Clock Race Free (7/11)

✦ Case2 : Input Variation Racefree (3/3)

■ Composition Rules :

- a. There exists at least a dynamic block in every chain of the pipelined section that there is an even number of inversions between the C²MOS latch and this dynamic block
- b. The total number of inversions between the two CMOS latch stage is even



Chapter 5

(二) Clock Race Free (8/11)

Example (1/3) :


NORA Serial – Parallel Multiplier

$$A = (a_3 a_2 a_1 a_0)$$

$$B = (b_3 b_2 b_1 b_0)$$

The binary product is given by
 
$$A \times B = (p_6 p_5 p_4 p_3 p_2 p_1 p_0)$$



(a) Serial Adder



Chapter 5

(二) Clock Race Free (9/11)


Example (2/3) :

The product terms are of the form

$$P_i = \sum_{\alpha+\beta=i} (a_{\alpha} b_{\beta})$$

The 4 – bit multiplication yields


$$\begin{aligned} P_0 &= a_0 b_0 \\ P_1 &= a_0 b_1 + a_1 b_0 \\ P_2 &= a_0 b_2 + a_1 b_1 + a_2 b_0 \\ P_3 &= a_0 b_3 + a_1 b_2 + a_2 b_1 + a_3 b_0 \\ P_4 &= a_1 b_3 + a_2 b_2 + a_3 b_1 \\ P_5 &= a_2 b_3 + a_3 b_2 \\ P_6 &= a_3 b_3 \end{aligned}$$

 

Chapter 5

(二) Clock Race Free (10/11)

Example (3/3) : (Serial **b** Input)

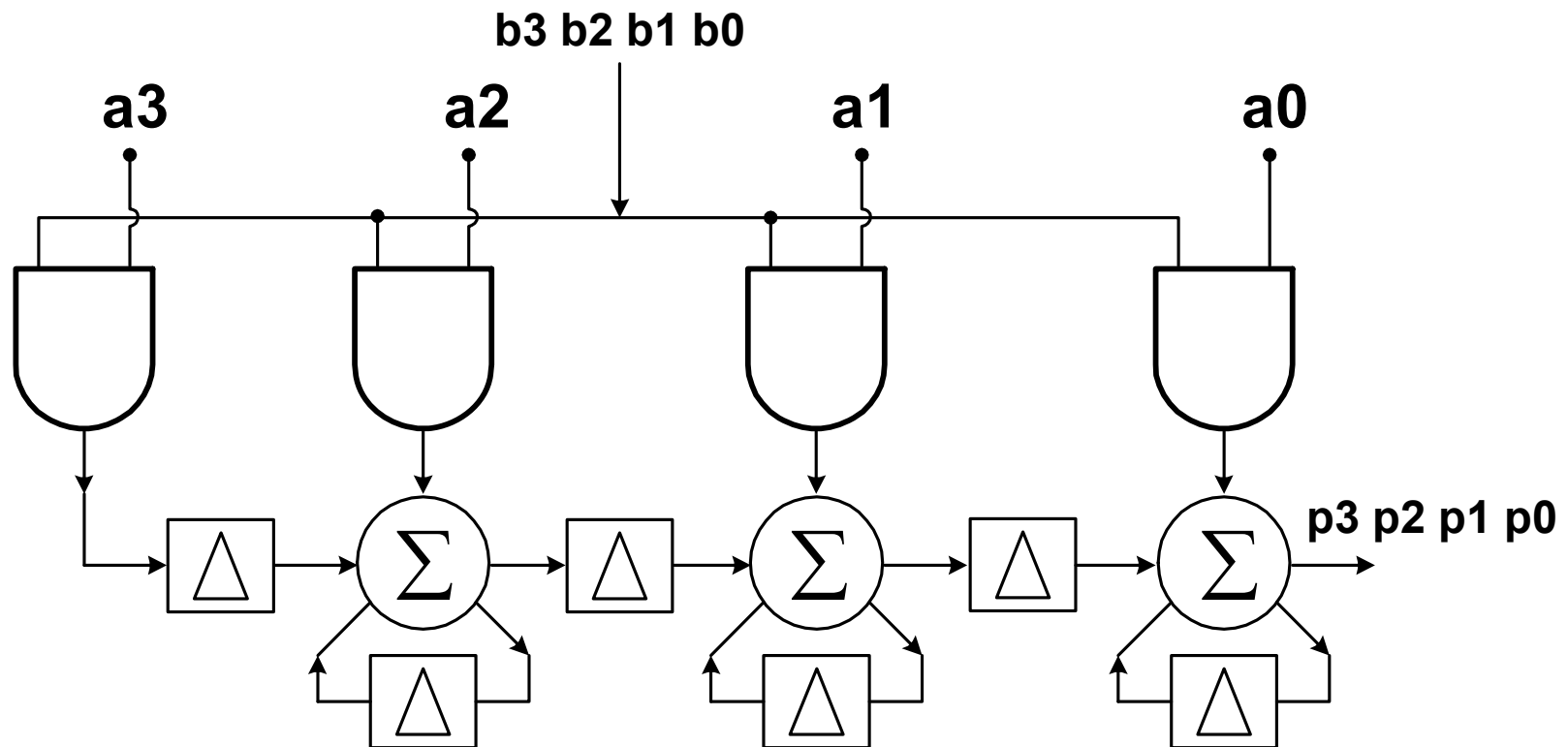

(b) Function Diagram
4-bit Serial-Parallel Multiplier



Chapter 5

(二) Clock Race Free (11/11)

■ Advantages :

- 1. Simple , small hardware
- 2. Regular
- 3. Extensive



■ Disadvantages :

- Requires long time for one multiplication



Chapter 5

- NORA serial Adder Circuit

 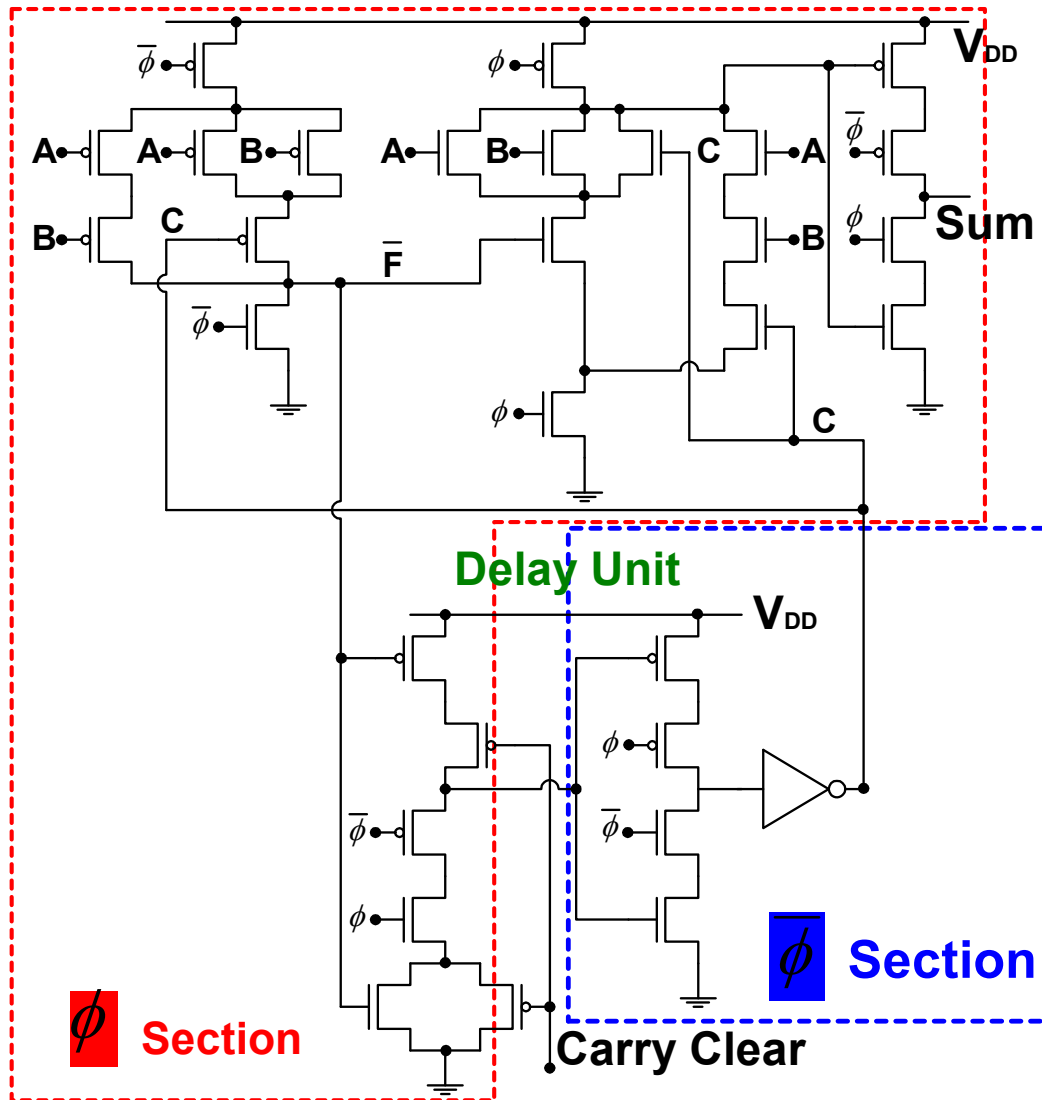

Can reduce
overlapping between
 $\bar{\phi}$ and ϕ



Chapter 5

5.2.11 True – Signal - Phase – Clock (TSPC) CMOS

Ref : [1] IEEE JSSC vol. SC-22 PP.899-901, Oct.1987

[2] IEEE JSSC vol. SC-24 PP.62-70, Feb 1989

[3] IEEE JSSC vol. 25 PP.225-233, Feb 1990

True-Single-Phase-Clock Login

The simplest clocking strategy


✧ (一) 、 Precharge (Dynamic) Logic (1/2)

- **N - Block + N - C²MOS = (ψ - section in the NORA circuit)**
- **P - Block + P - C²MOS = ($\bar{\psi}$ - section in the NORA circuit)**




Chapter 5

✧ (一) 、 Precharge (Dynamic) Logic (2/2)

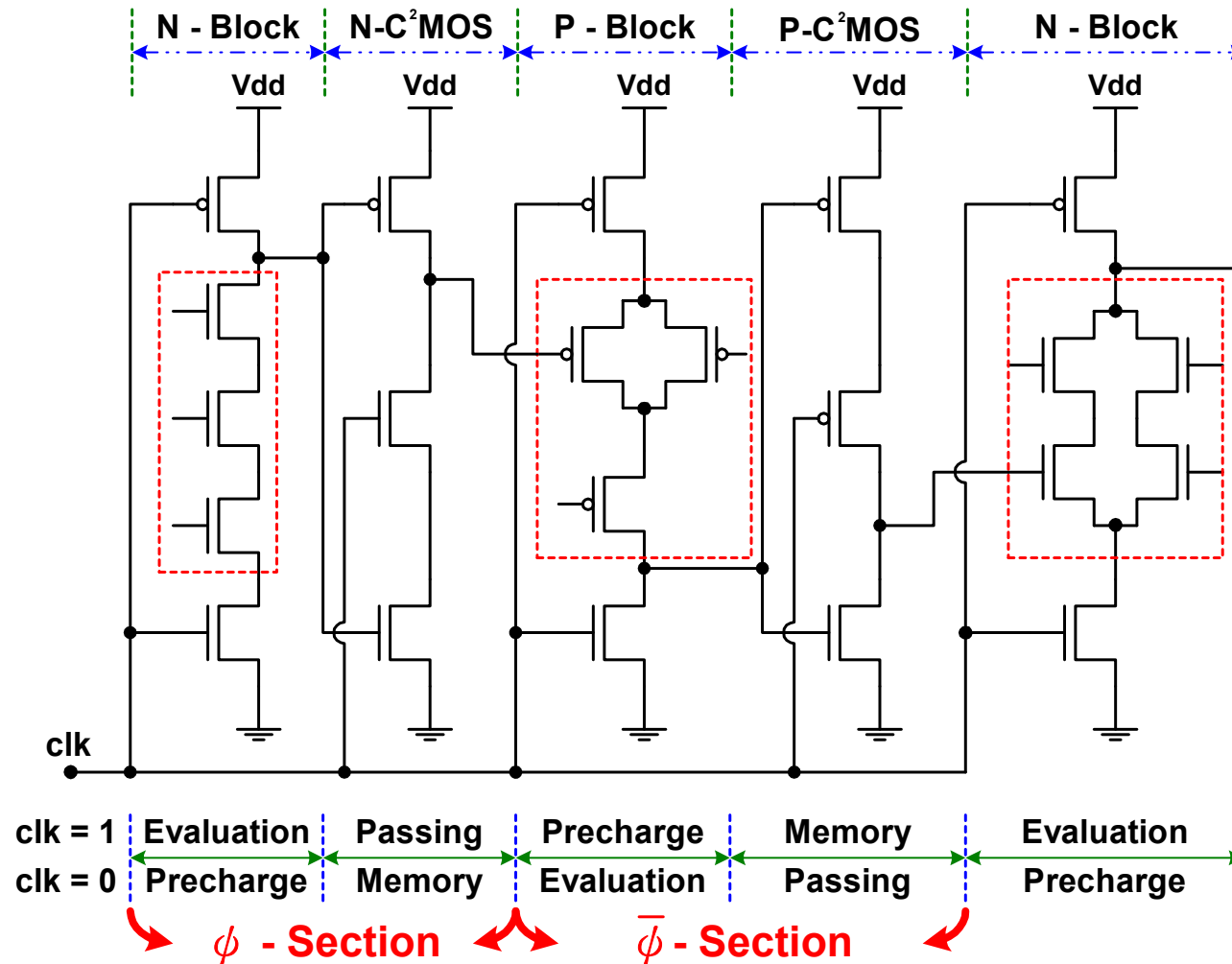

A pipeline of precharged logic circuits using the single-phase clock


 



Chapter 5

(二) 、 Storage Elements

■ D-type FF 'S (1/3)

(1) Positive edge triggered FF (ETDFF)

 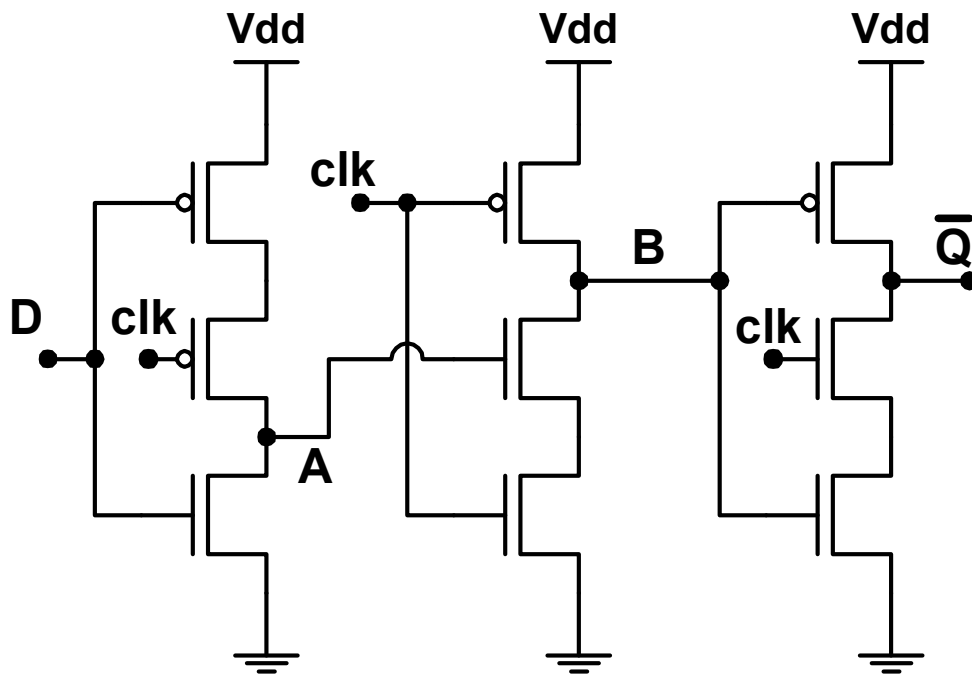

 



Chapter 5

(二) 、 Storage Elements

■ D-type FF 'S (2/3)

(2) Negative ETDFF

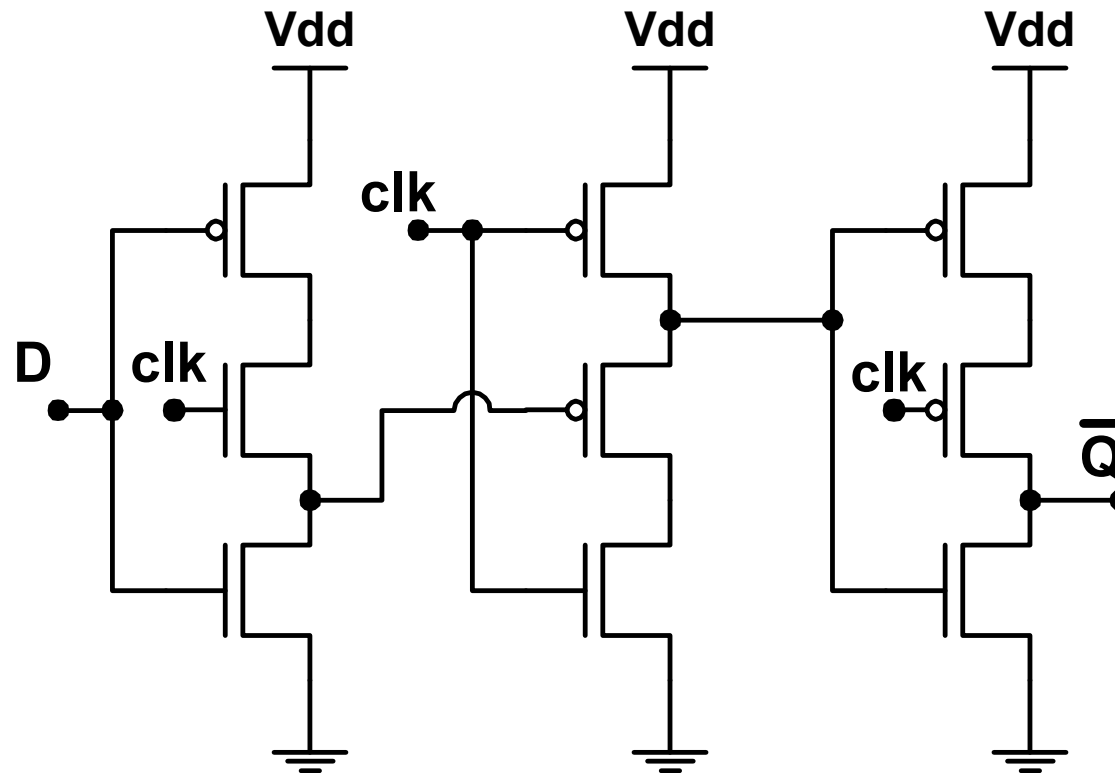

 


Chapter 5

(二) 、 Storage Elements

■ D-type FF 'S (3/3)


(3) Positive ETDFF using split – output latch stages

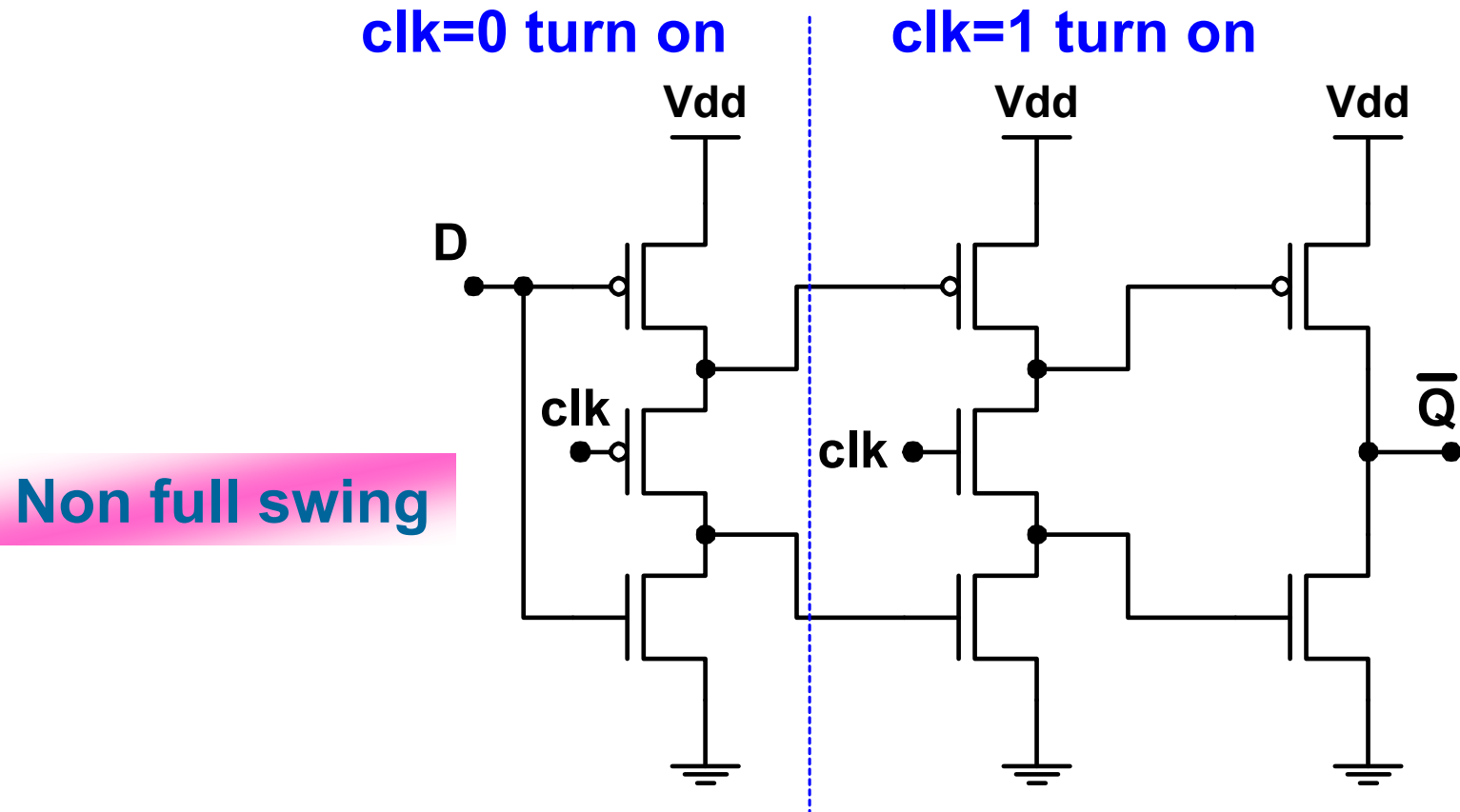



Chapter 5

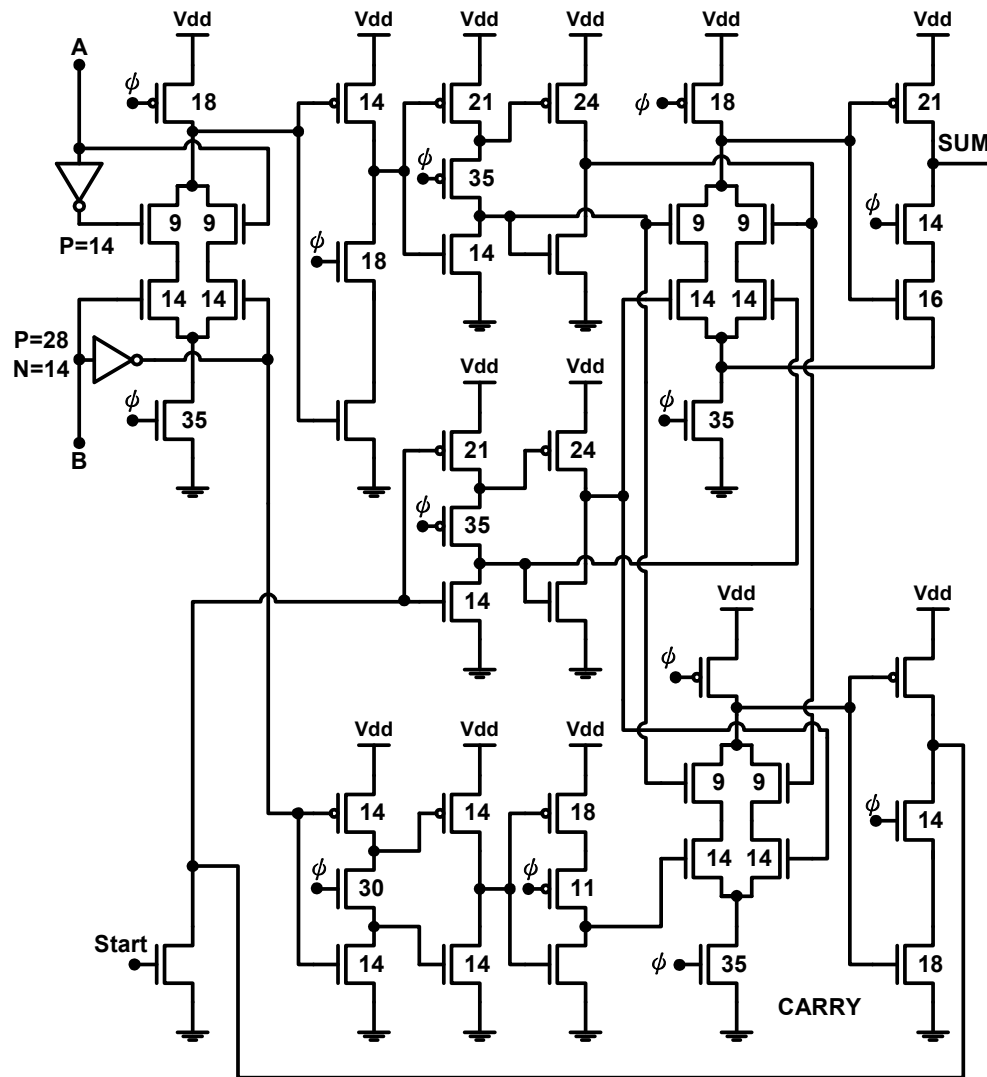(三) 、 Circuit Examples : TSPC Serial Full Adder (1/2) :




Serial full adder with
all logic in N-blocks
(TSPC adder 2).



Chapter 5

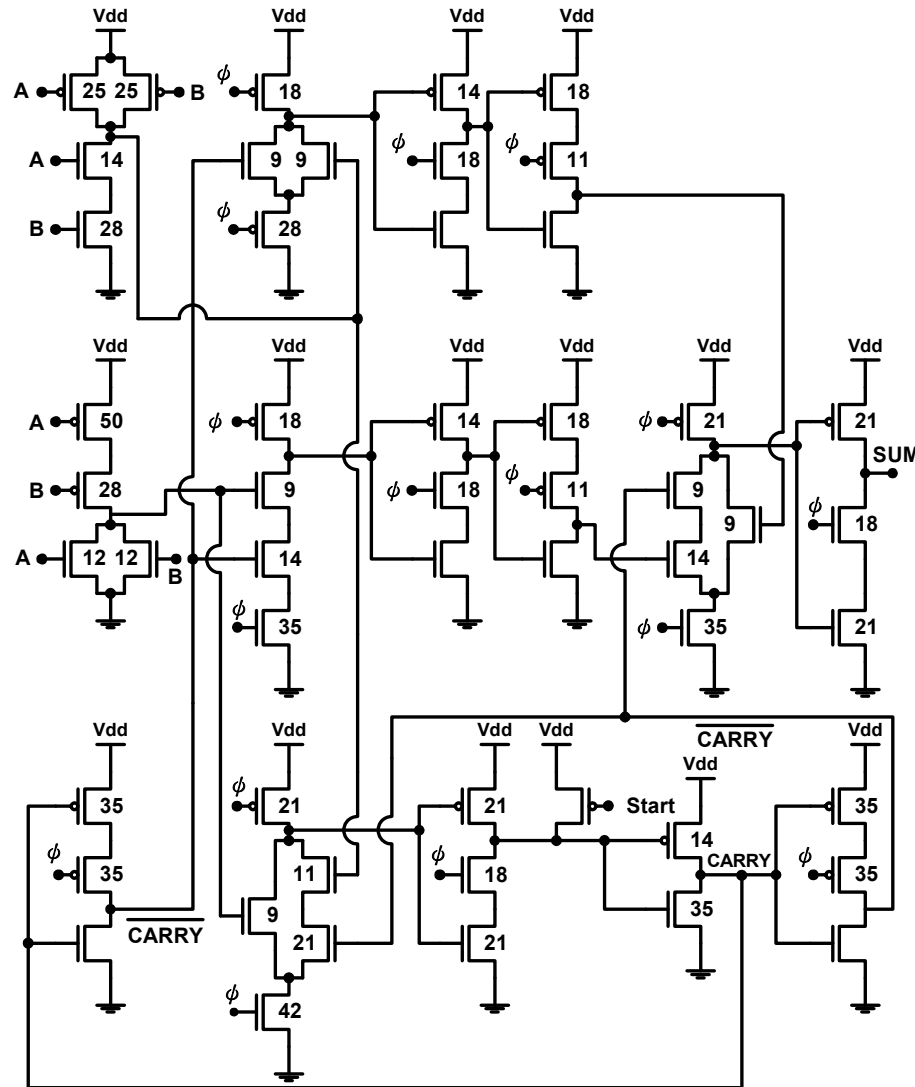(三)、Circuit Examples : TSPC Serial Full Adder (2/2) :




Fast serial full adder
(TSPC adder 3).




A. Concept :



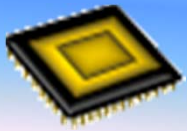


Chapter 5

B. Design Example: MODL Carry-Look-Ahead Adder (1/2)

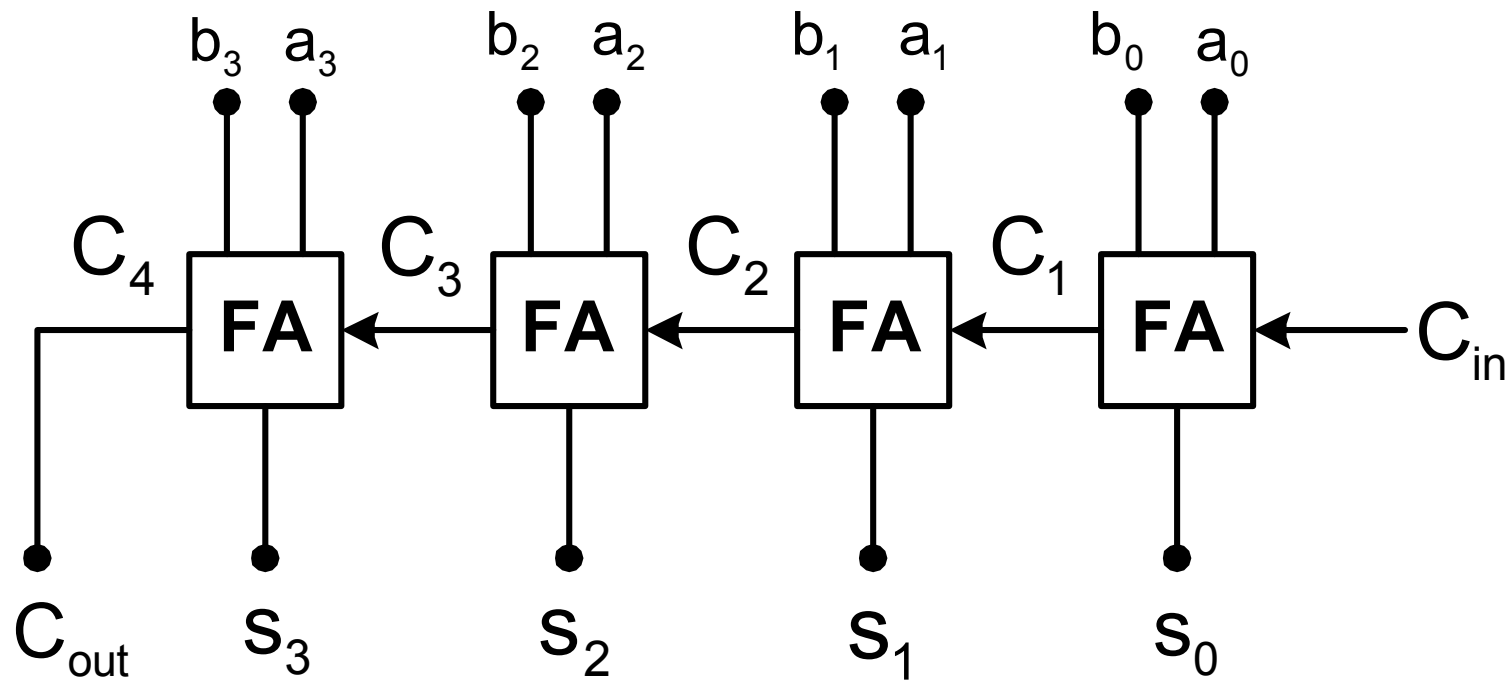

Basic 4-bit Parallel Adder

 

Chapter 5

B. Design Example: MODL Carry-Look-Ahead Adder (2/2)

■ *Basic addition algorithms*

$$S_i = a_i \oplus b_i \oplus C_i$$

$$C_{i+1} = a_i b_i + (a_i \oplus b_i) C_i$$

■ *Carry-Look-Ahead Addition algorithms*

generate function $g_i = a_i b_i$

Propagate function $P_i = (a_i \oplus b_i)$


$$C_0 = C_{in}$$

$$C_1 = g_0 + P_0 C_{in}$$


$$C_2 = g_1 + P_1 (g_0 + P_0 C_{in})$$

$$C_3 = g_2 + P_2 (g_1 + P_1 (g_0 + P_0 C_{in}))$$


$$C_4 = g_3 + P_3 (g_2 + P_2 (g_1 + P_1 (g_0 + P_0 C_{in})))$$

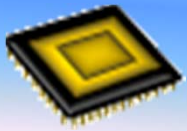

Chapter 5

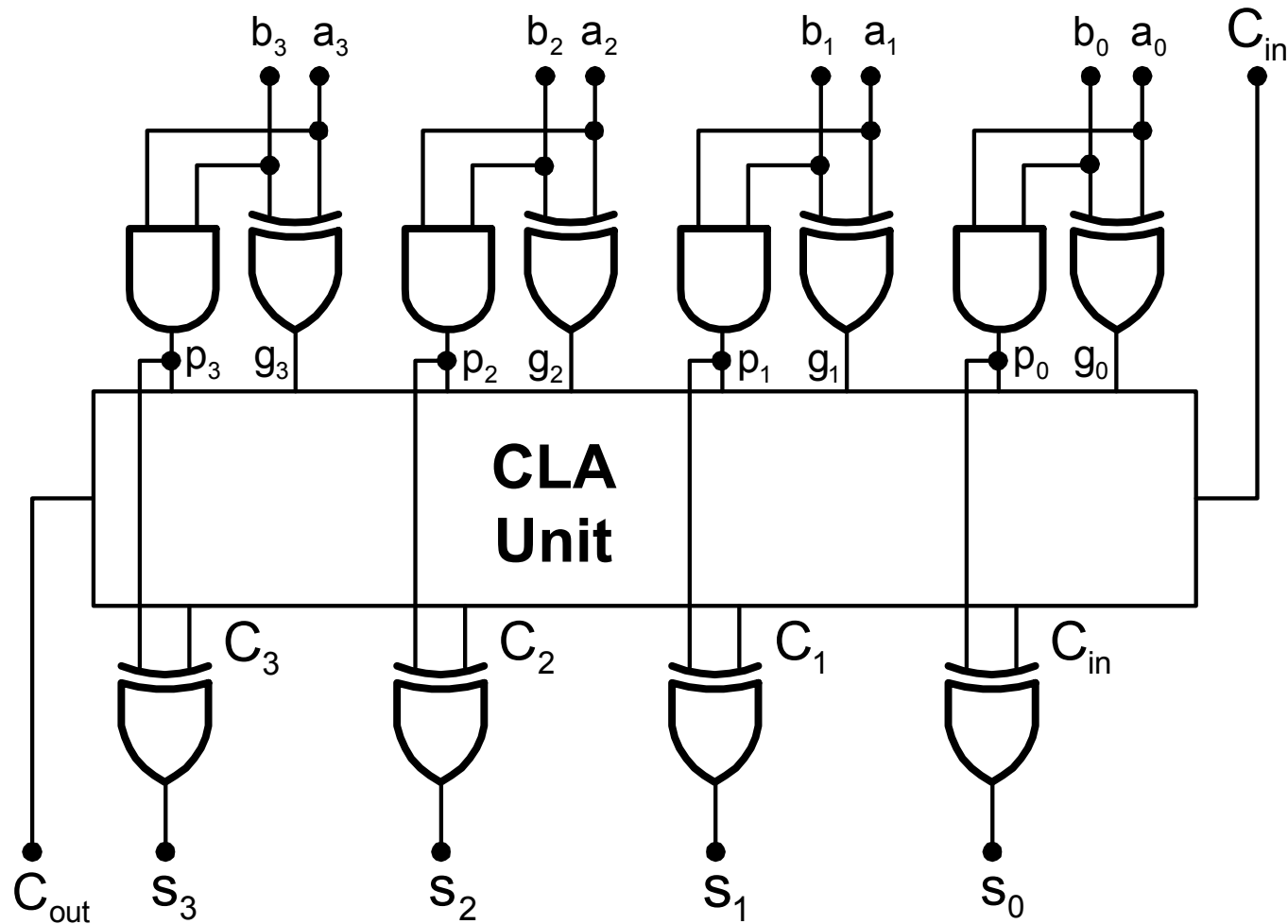

CLA 4-bit Parallel Adder

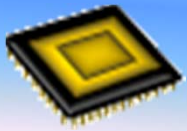

Chapter 5

5.3 CMOS Differential Logic

- Cascode Voltage Switch Logic (CVSL)
- Invented by IBM
- *Ref: VLSI Design Oct. 1984, PP.78-86*

5.3.1 Differential Cascode Voltage Switch Logic (DCVS)

Ref : [1] ISSCC Dig. Tech. Papers, Feb 1984, PP 16-17

[2] VLSI Design Oct. 1984, PP. 78-86

[3] IEEE JSSC, vol. SC-22, PP. 528-532 ,Aug ,1987


[4] IEEE JSSC, vol. SC-21, PP. 1082-1087, Dec ,1986




Chapter 5

(A) Basic Structure :

- Two cross-coupled PMOS transistors (Mp1 and Mp2) Form the latch
- The logic is performed by NMOS arrays
→ Both true and complement inputs are necessary
- Cascode transistor circuits : called TREE
- dual-rail logic → Differential Logic

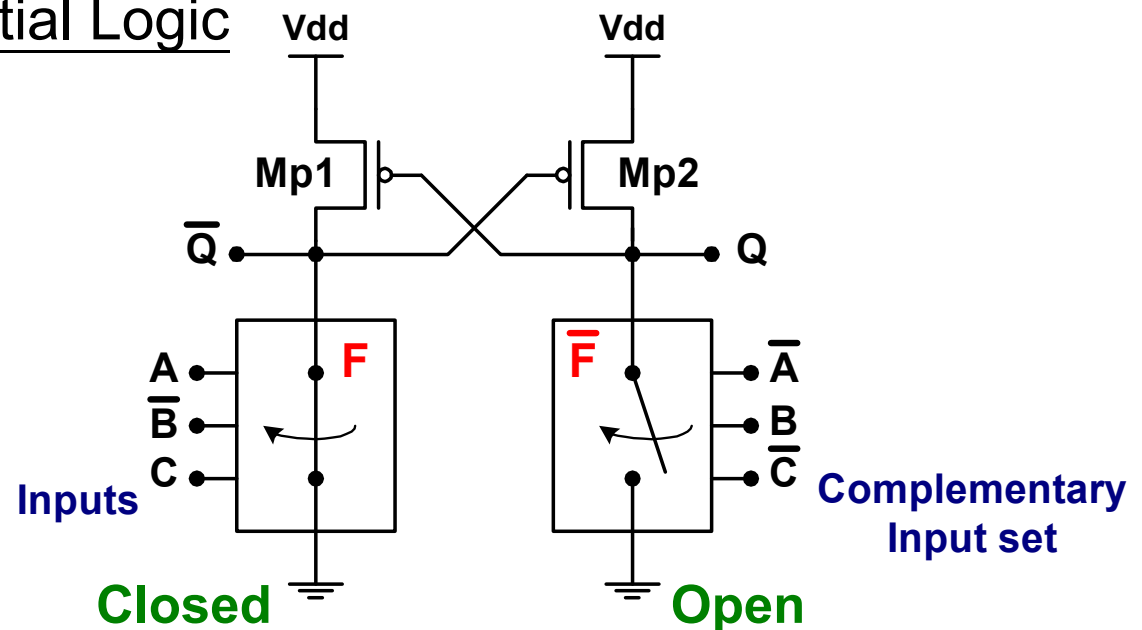

 


Chapter 5

Example - 1 :

$$F = AB + C$$

$$\bar{F} = \overline{AB + C}$$

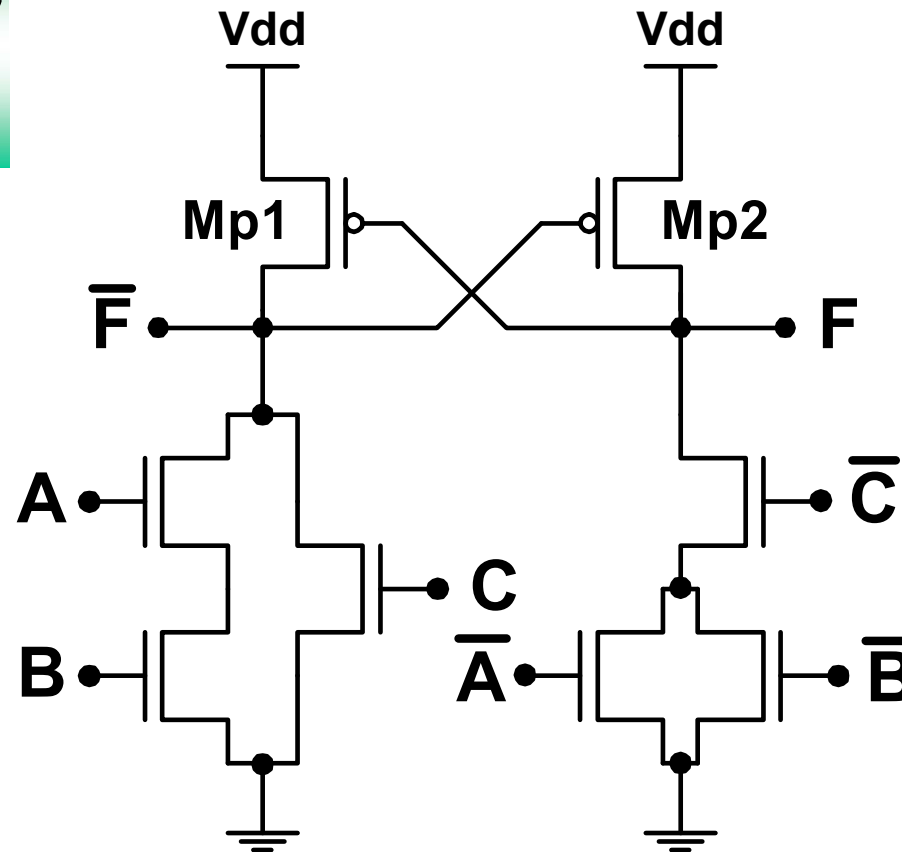




Chapter 5

Example - 2 :

DCVSL Latch

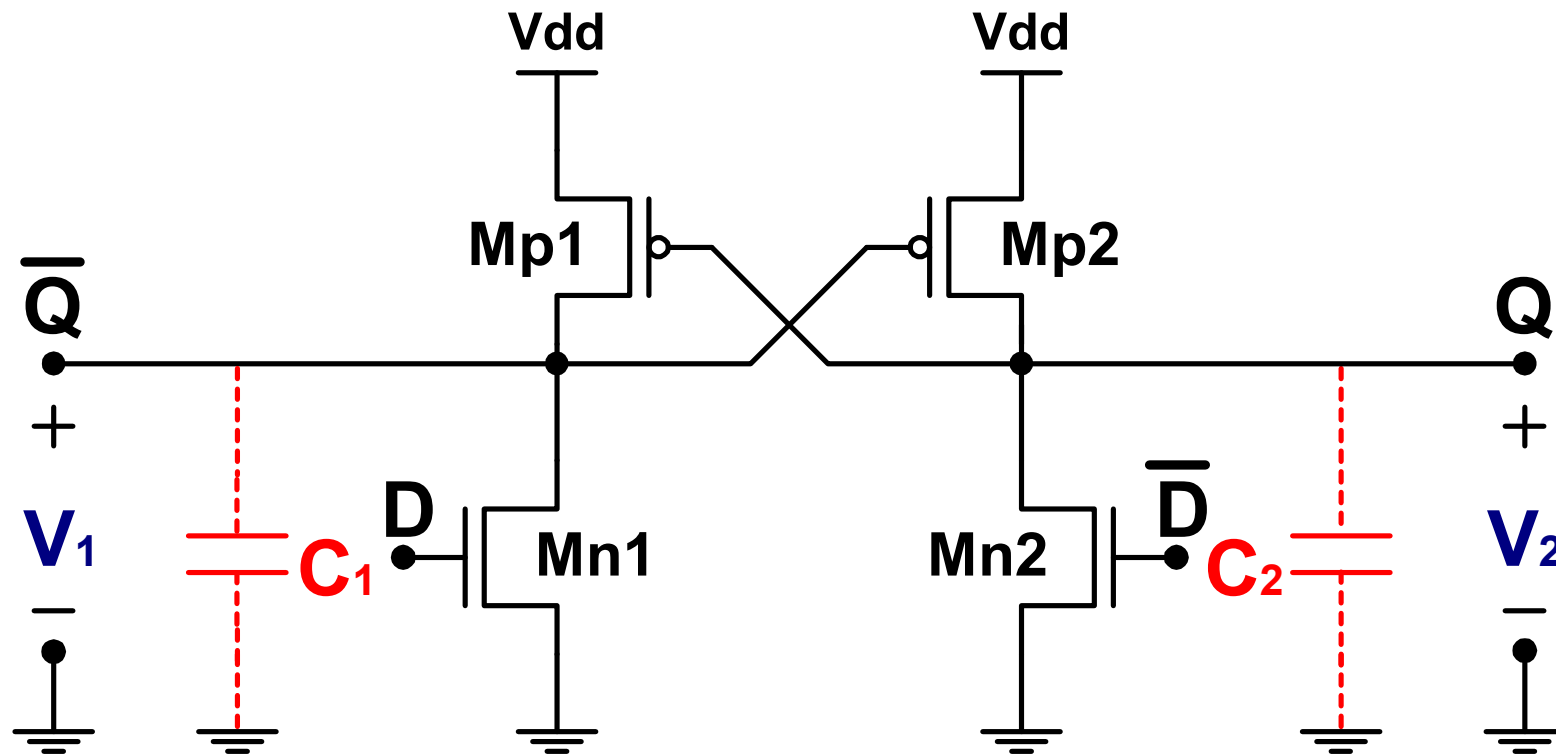






Chapter 5

Example - 3 : DCVSL Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = AB + BC + AC$$

  


 

Chapter 5

(B) Clocked DCVS (1/2) :

Weak PMOS

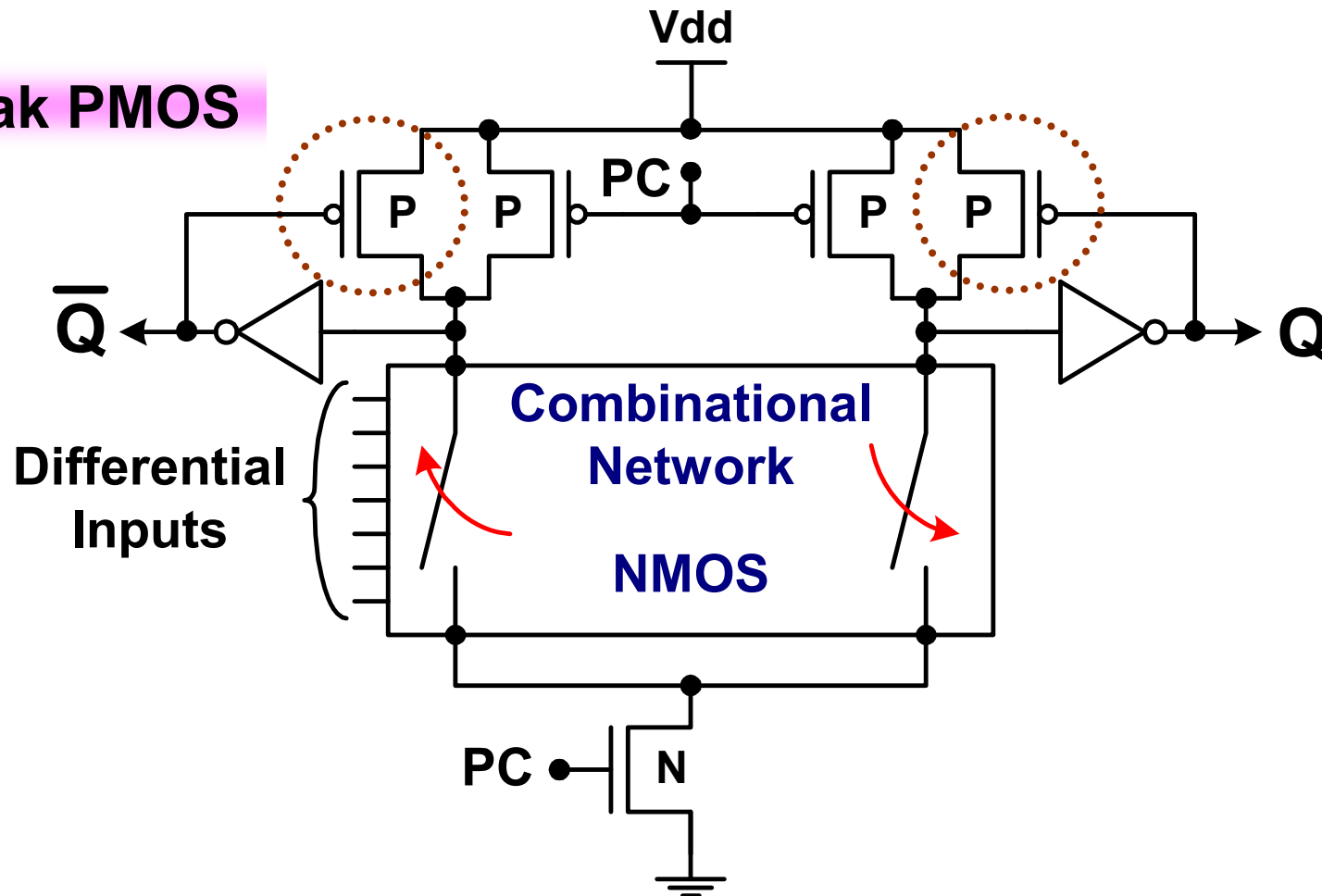



Chapter 5

(B) Clocked DCVS (2/2) :

■ Advantages :

Can implement any logic functions because of double rail logic (Differential outputs)

■ Disadvantages :

- (1) Large current spikes during switching (static logic)
- (2) Large chip area
- (3) Slow

✱ How to IMPROVE THE OPERATION SPEED OF THE DIFFERENTIAL LOGIC ?

- (1) Using SENSE AMP to improve the discharging speed .
- (2) limited the Logic Voltage Swing .




Chapter 5

5.3.2 Sample – Set Differential Logic (SSDL) (1/2)

Ref : IEEE JSSC Vol-21 PP.367-369 Feb. , 1988

- $\psi = 0$ ($\bar{\psi} = 1$) : Sample
T1, T2, and T3 are ON
N1 and N2 have a Voltage difference
(300 mV – 400 mV)
- $\psi = 1$ ($\bar{\psi} = 0$) : Set
T1, T2, and T3 are OFF
T6 : ON
- Latch operation
(N1 (or N2) is discharged quickly by sense amp.)

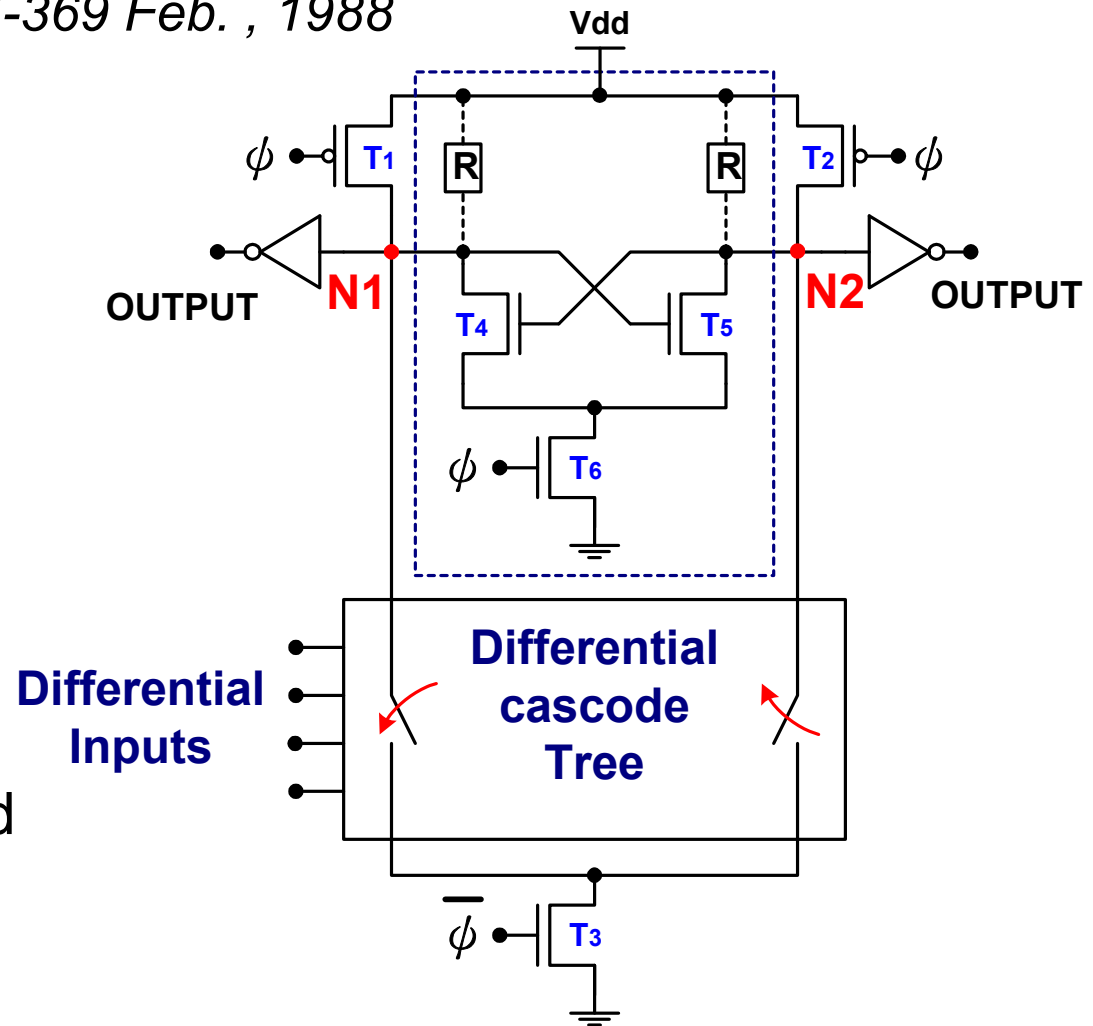



Chapter 5

5.3.2 Sample – Set Differential Logic (SSDL) (2/2)

TABLE 1

Comparison results for the static CMOS , CVSL , and SSDL circuits (*) 20 Without Resistive load elements

Circuit Type	Device Count	Active Area (um X um)	Time per Evaluatio (ns)	Power Dissipation (mW)
Static CMOS	28	420 X 3	10	1.75
CVSL	17	240 X 3	12	1.87
SSDL	22 *	250 X 3	8	3.72

TABLE 2

Speed of operation versus number of transistors in series in the NMOS tree network

Circuit Type	Transistor in Series	Relative Time to Change Buffer Output
Domino & CVSL	3	1.0
	5	1.3
	7	1.5
SSDL	3	1.0
	5	1.0
	7	1

- ❖ Allow the use of several transistors in series or parallel without significant speed degradation.
- ❖ Power dissipation↑.
- ❖ Relaxed dimension ratio and charge-redistribution design constraint .
- ❖ Stage number↓.
- ❖ true-two-phase clocking strategy.




Chapter 5

5.3.3 Differential Split – Level (DSL) circuit (1/2)


Ref : IEEE JSSC vol. SC-20 no.2 PP. 531-536, April, 1985

■ DSL Basic Structure

- ☀ Can be viewed as a modified DCVS logic circuit
- ☀ Two NMOSs **MR1** and **MR2** are added between Q (\bar{Q}) and F (\bar{F})
- ➔ this clamps the voltage on nodes F and \bar{F} to $(V_{DD} / 2)$
- ➔ higher operation speed (\because quickly discharge)

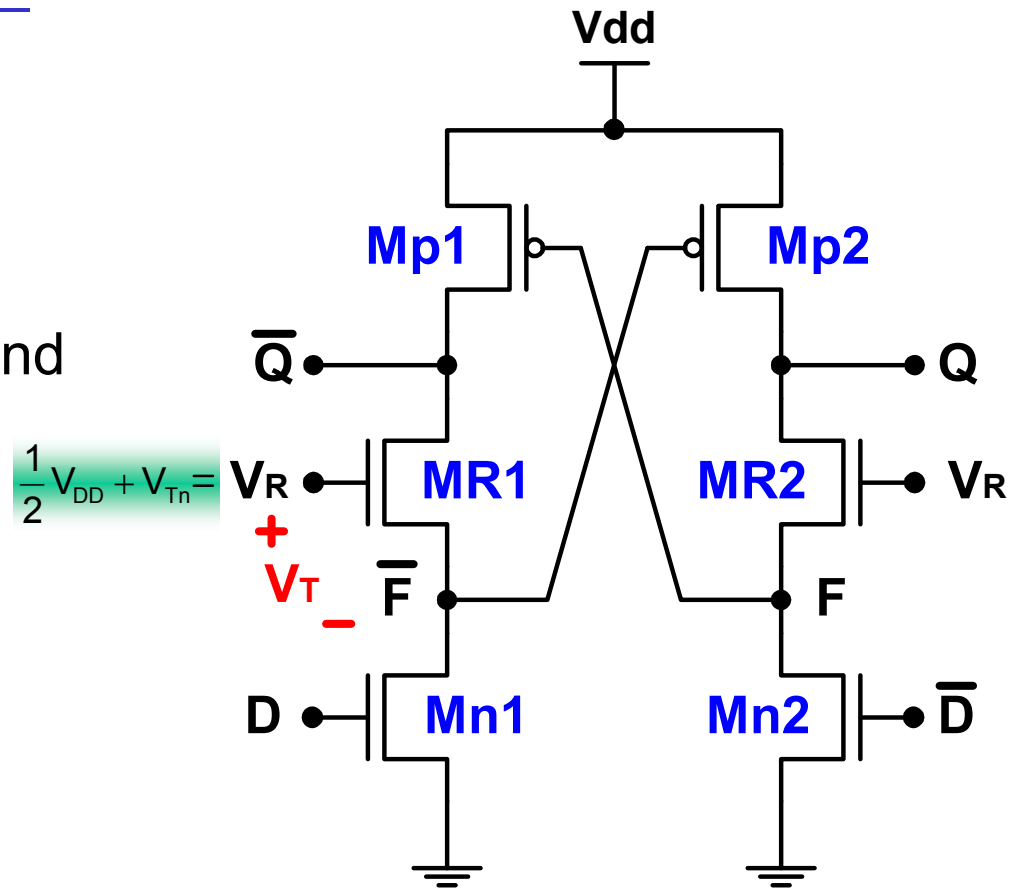

VLSI 5-103

 

Chapter 5

5.4 Pass - Transistor Logic Families


- ✦ Several pass - transistor logic families , for logic design , have been proposed for improving the speed of CMOS circuits , Such families are :
 - 1) The conventional CMOS pass - transistor logic
 - 2) The complementary pass - transistor logic (**CPL**)
 - 3) The Dual Pass - transistor Logic (**DPL**)
 - 4) The Swing Restored Pass - Transistor Logic (**SRPL**)



Chapter 5

 5.4.1 TG – Based Switch Logic Gates (1/6)

- Transmission gate logic is based on data path control



$S=1$: $B \leftarrow A$
 $S=0$: TG is OFF
(High - imp.)

Transmission - Gate Logic



Chapter 5

5.4.1 TG – Based Switch Logic Gates (2/6)

- Path Select


$$F = AS + B\bar{S}$$

This can be used as a data path selector as seen by writing.

if $S = 1 : F = A$

if $S = 0 : F = B$

 This is a special case of a multiplexer network



2 - Input TG Path Select




Chapter 5

 5.4.1 TG – Based Switch Logic Gates (3/6)

- OR Gate

$$\begin{aligned} F &= A + \overline{A}B \\ &= A + B \end{aligned}$$



TG - Logic OR Gate




Chapter 5

 
5.4.1 TG – Based Switch Logic Gates (4/6)

- XOR , XNOR Gate

$$\begin{aligned}F_1 &= A \oplus B \\&= A\bar{B} + \bar{A}B \\F_2 &= A \odot B \\&= AB + \bar{A}\bar{B}\end{aligned}$$



(a) XOR

 

(b) Equivalence

* Both A , \bar{A} , B , \bar{B} are used




Chapter 5


5.4.1 TG – Based Switch Logic Gates (5/6)

- Alternate XNOR Gate

- * Only A , B , \overline{B} are used

- * Fewer MOS transistors

 

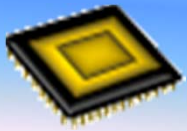

Chapter 5

5.4.1 TG – Based Switch Logic Gates (6/6)


- ✦ Compared with the traditional logic design method , pass transistor networks may achieve **high density** , **low power** , and in some case **high performances**.
- ✦ Designing pass transistor networks has been a Craft than a Science.



Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method

- Model for pass transistor logic

 



Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method

- Example : $A \odot B$ (1/3)

Modified Karnaugh Map			
		A	
		0	1
B	0	\bar{A} \bar{B} 1	\bar{A} B 0
	1	A \bar{B} 0	A B 1

Under Control of A

XNOR Truth Table			
A	B	$A \oplus B$	Pass Function
0	0	1	$\bar{A} + \bar{B}$
0	1	0	$A + \bar{B}$
1	0	0	$\bar{A} + B$
1	1	1	$A + B$


Under Control of \bar{A}




Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method


- Example : $A \odot B$ (2/3)

 

(a) complementary

 

(b) signal - polarity

 

(c) cross - coupled

Two - input XNOR gate implemented in pass - transistor logic



Chapter 5


5.4.2 TG – Based Switch Logic Gates Design Method

- Example : $A \odot B$ (3/3)

Modified Karnaugh Map			
		A	
		0	1
B	0	\bar{A} 1 \bar{B}	\bar{A} 0 B
	1	A 0 \bar{B}	A 1 B

Under Control of \bar{B}

Under Control of B

 



Chapter 5


5.4.2 TG – Based Switch Logic Gates Design Method

- Example : OR Gate

		A	
		0	1
B	0	A 0 B	A 1 \bar{B}
	1	\bar{A} 1 B	A 1 B

Under Control of \bar{A}

Under Control of A

 

Can be eliminated
(Why ?)



Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method

- Alternate XNOR Gate : $A \odot B = AB + \bar{A}\bar{B}$ (1/2)

Modified Karnaugh Map			
		A	
		0	1
B	0	\bar{A} \bar{B} 1	\bar{A} B 0
	1	A \bar{B} 0	A B 1

\bar{B} \bar{B}

Under Control of \bar{A}
(pass 1)

B B

Under Control of A
(pass 0)

Why ?

A A


Under Control of B
(pass logic value 1 and 0)



Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method

- Alternate XNOR Gate : $A \odot B = AB + \bar{A}\bar{B}$ (2/2)

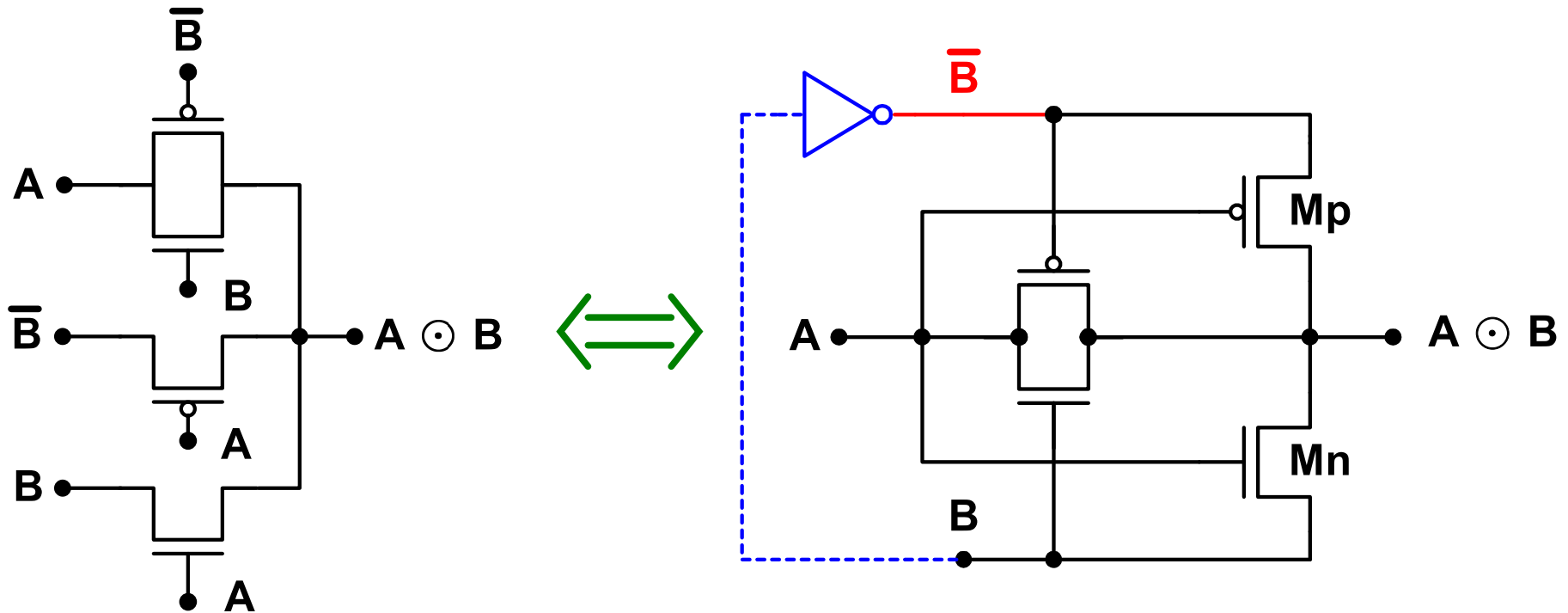




Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method


• Full Adder (1/2) :

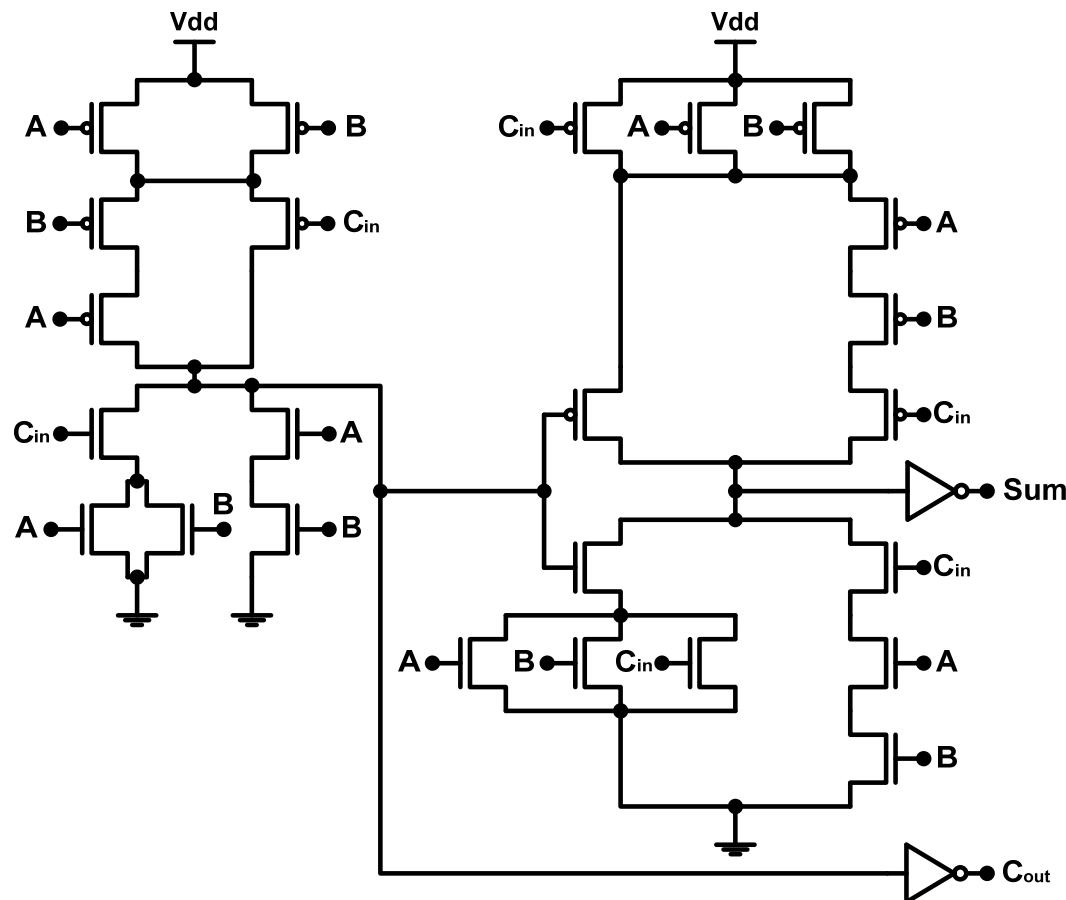

Adder Turth Table

A	B	Cin	Sout	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1


CMOS static full adders using complementary style

 

Chapter 5

5.4.2 TG – Based Switch Logic Gates Design Method

- Full Adder (2/2) :

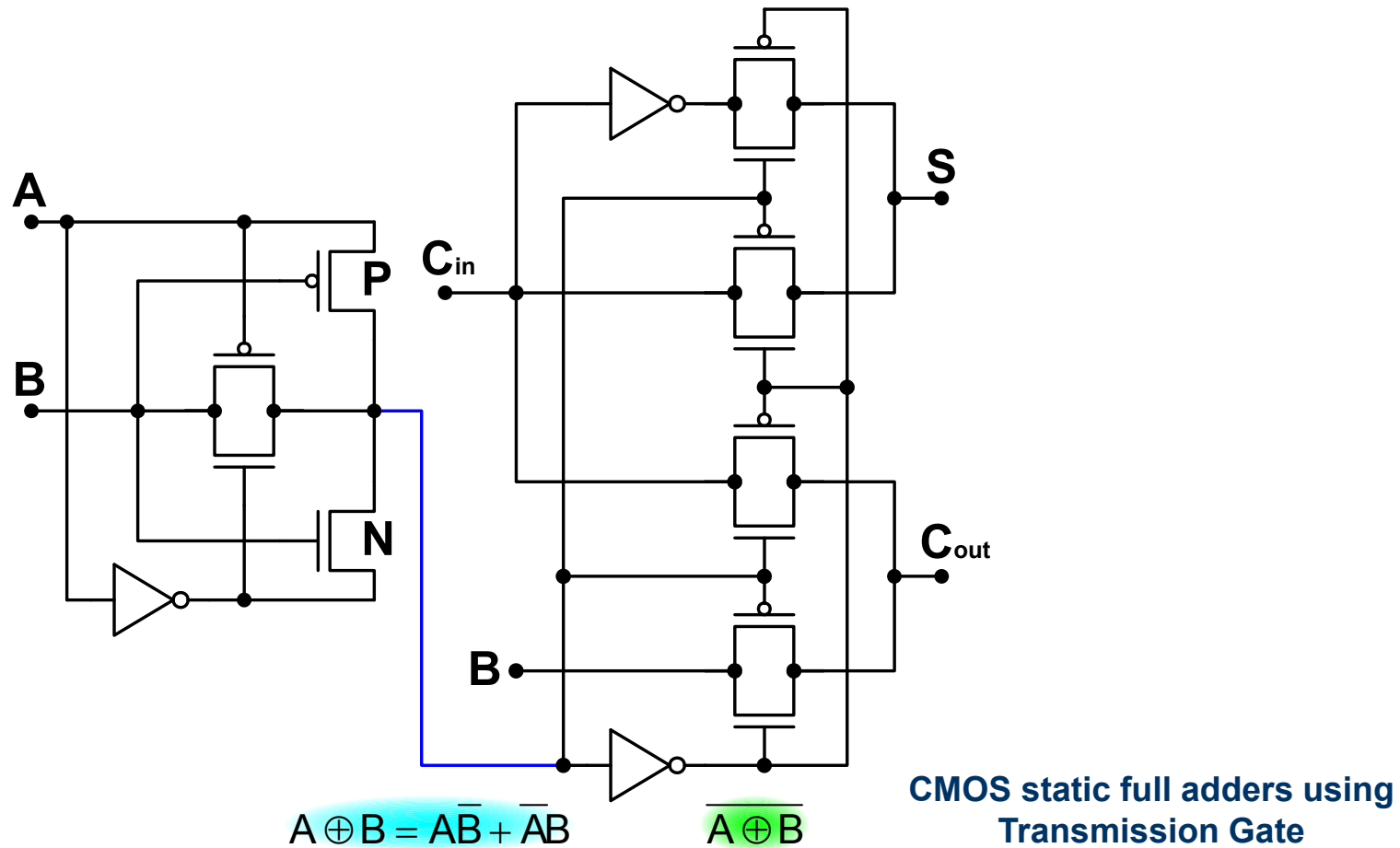





Chapter 5

5.4.3 Pass – Transistor Array Logic (1/7)

- Multiplexer and Demultiplexer can be directly implemented using PG arrays

 

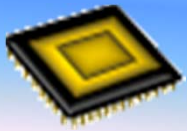


Chapter 5

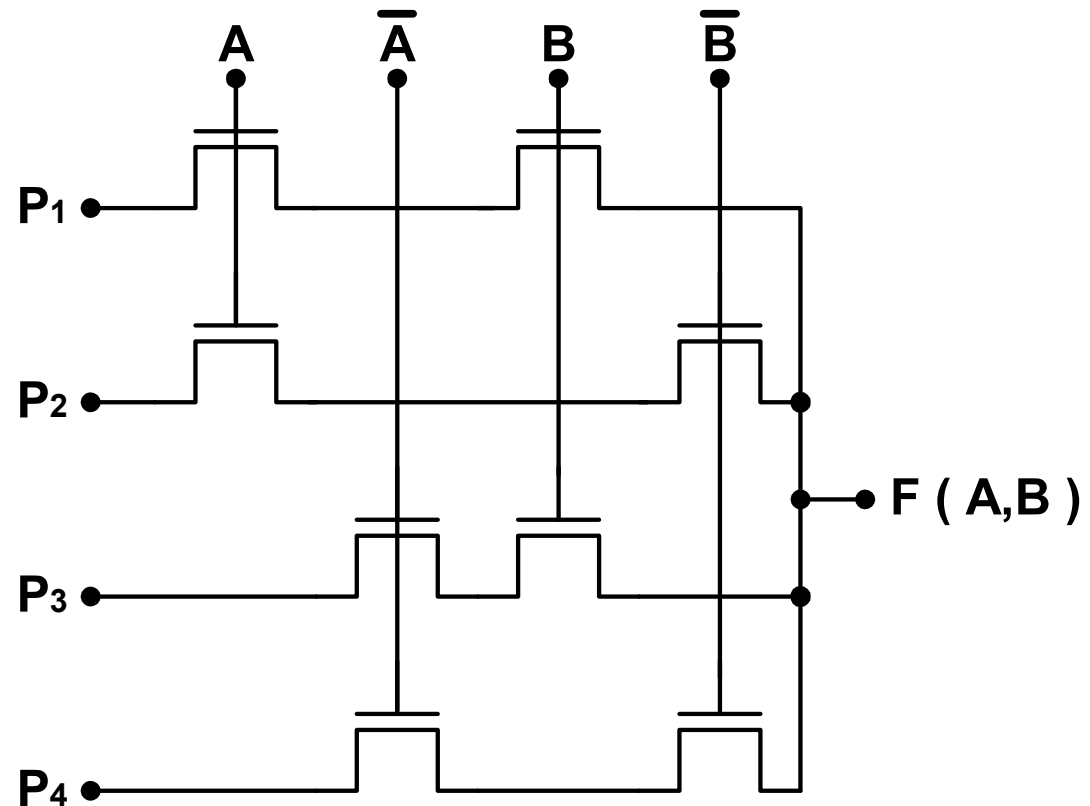
5.4.3 Pass – Transistor Array Logic (2/7)

■ (a) NMOS PTL

- $V_o \doteq V_{DD} - V_{TN}$
- Multiplexer



$$F = P_1 AB + P_2 A\bar{B} + P_3 \bar{A}B + P_4 \bar{A}\bar{B}$$

 


Chapter 5

5.4.3 Pass – Transistor Array Logic (3/7)

■ (b) CMOS PTL (I)

- $V_o = V_{DD}$
- Chip area \uparrow
- Faster than NMOS PTL

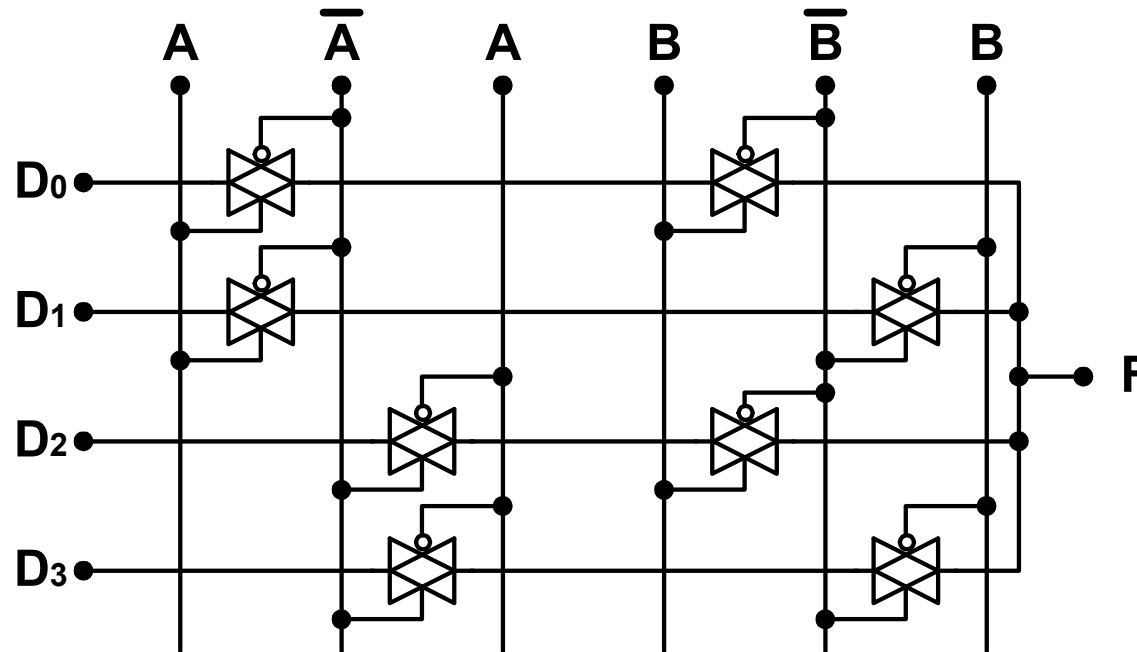





Chapter 5

5.4.3 Pass – Transistor Array Logic (4/7)

■ (c) Split CMOS PTL (II)

- Chip area is smaller than that of (b) CMOS PTL (I)
∴ $n^+ - p^+$ contacts ↓
- $V_o = V_{DD}$

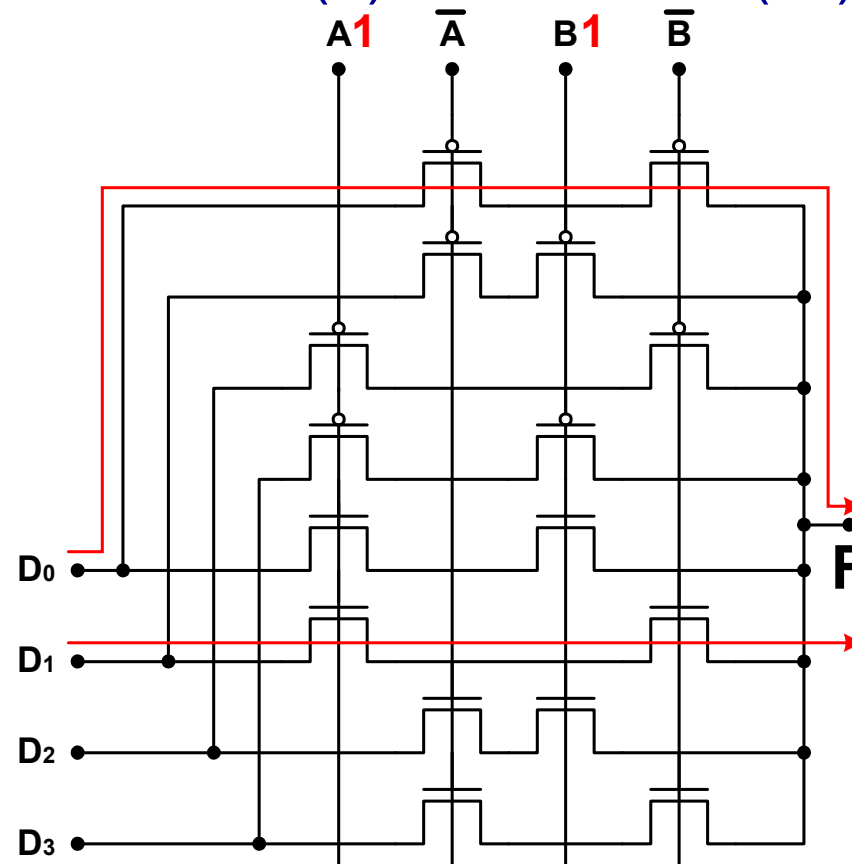

 


Chapter 5

5.4.3 Pass – Transistor Array Logic (5/7)

■ (d) CMOS PTL (Ⅲ)

- V_o restoring circuit $\rightarrow V_o \doteq V_{DD}$
- Speed can be improved

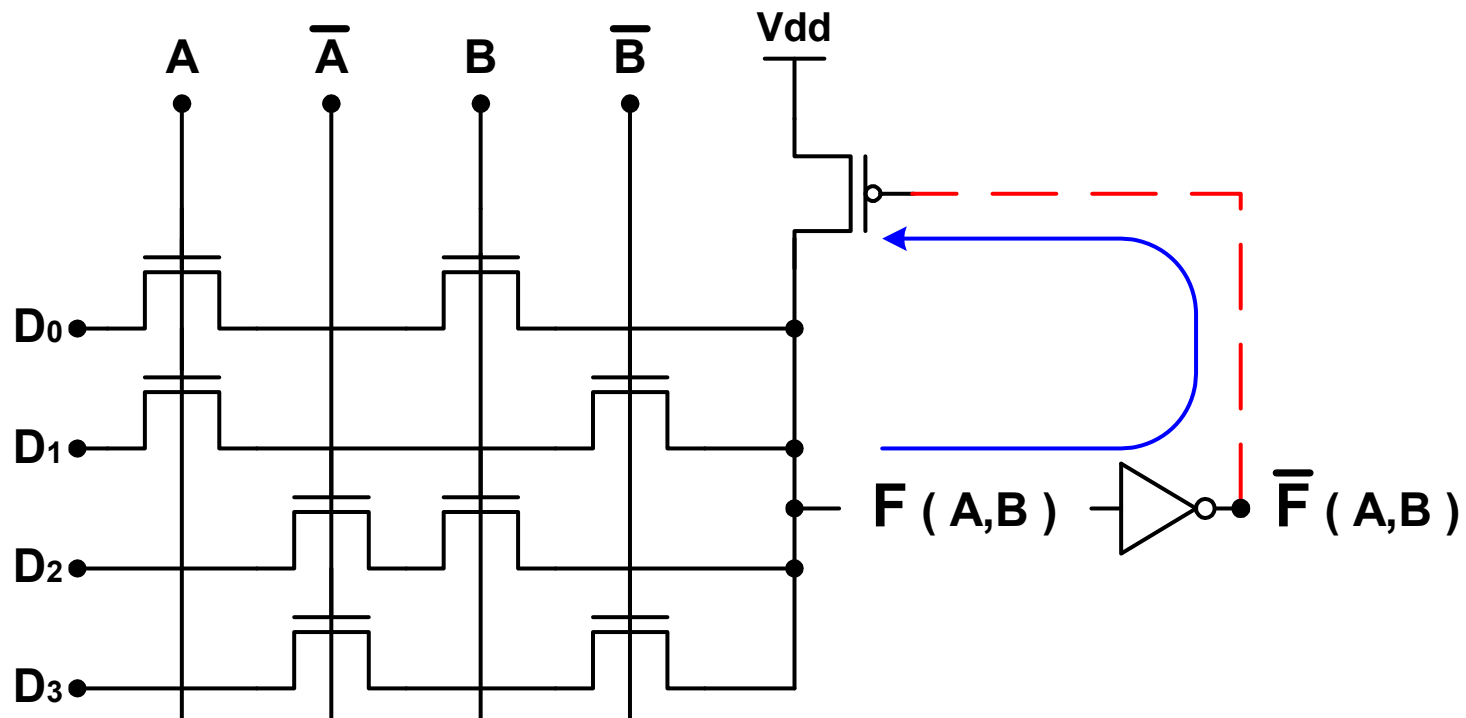




Chapter 5

 5.4.3 Pass – Transistor Array Logic (6/7)

- ✱ However , the Pass – Transistor (TG) logic circuit does not provide a restoration of the logic level , i.e. the logic gates are passive with no gain elements .
- ✱ The driving capability of the circuit is limited and delay increases with long TG chains .




An inverter stage is added every 4 TG stages



Chapter 5

5.4.3 Pass – Transistor Array Logic (7/7)

 




Chapter 5

5.4.4 Complementary Pass – Transistor Logic (CPL) (1/7)

Ref : IEEE JSSC , Vol. sc-25 , No.2 P.P.388 ~ 394 , April 1990 (Hitachi VLSI Eng. Corp.)

- ✦ CPL consists of NMOS pass transistor logic network driven by two sets of complementary inputs and two CMOS inverters used as buffers.
- ✦ For 1.2 V applications

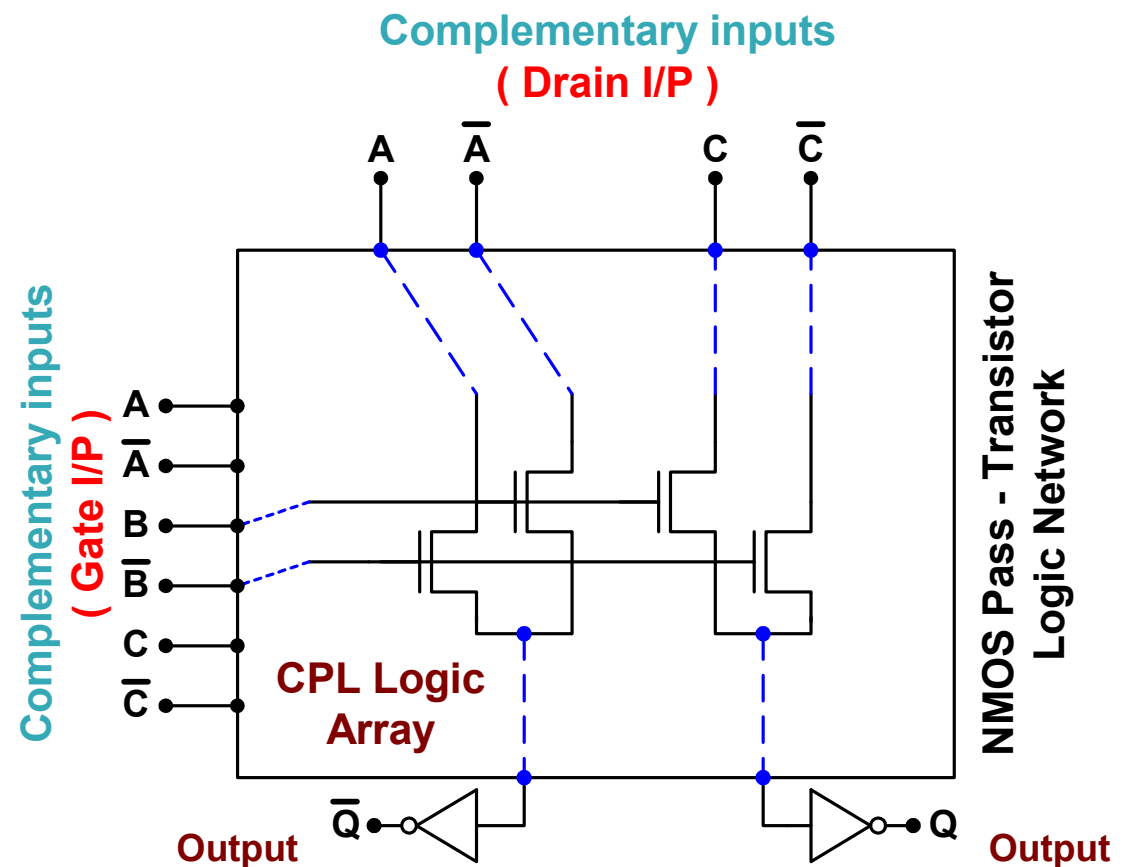



Chapter 5

5.4.4 Complementary Pass – Transistor Logic (CPL) (2/7)

✱ 2-input NAND gate (1/2)

- The NMOS network from pull - up and pull - down function



→ the voltage of the node Q is

$$V_Q = V_{DD} - V_{TN} \quad (V_Q)$$

- Sol : The logic threshold of the inverter buffer should be shifted to lower voltage than $\frac{1}{2} V_{DD}$

→ β ratio of Inv. =
$$\frac{\mu_n \frac{W_n}{L_n}}{\mu_p \frac{W_p}{L_p}} > 1$$

→ Inv. output quickly to pull - down

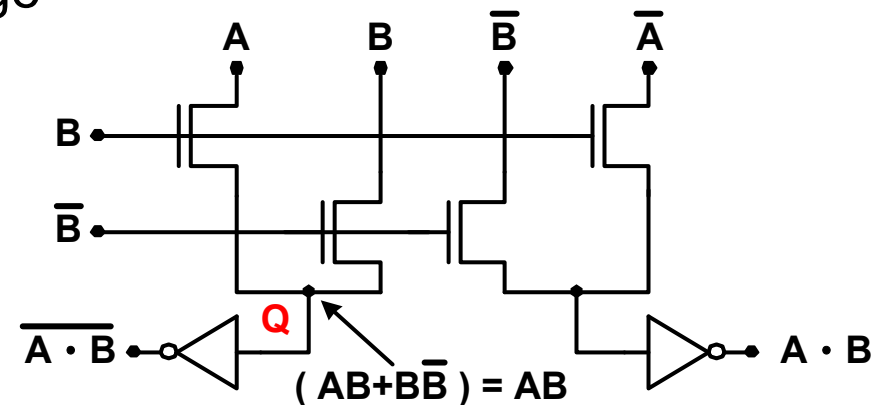 



Chapter 5

5.4.4 Complementary Pass – Transistor Logic (CPL) (3/7)

✱ 2-input NAND gate (2/2)

■ $\therefore V_Q (\text{High}) = V_{DD} - V_{TN}$

➔ the V_{GS} of the PMOS is $-V_{TN}$ as shown

in Fig (1)

➔ the PMOS is not completely OFF

➔ DC power dissipation

■ Sol :

(1) ✱ Can design MOS threshold such that

$$V_{TN} < |V_{TP}|$$

(2) ✱ Using PMOS latch to restore the high – level voltage of the node Q .

✱ Careful design should be considered , otherwise the high – level stored in the latch can not be discharged .



 


Fig (1) High level degradation in CPL .




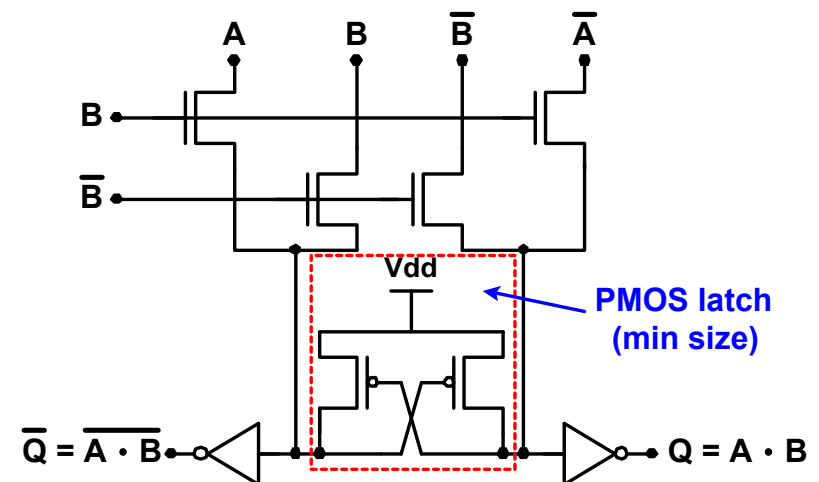


 

Chapter 5

5.4.4 Complementary Pass – Transistor Logic (CPL) (4/7)

✱ 2-input OR , XOR gate

 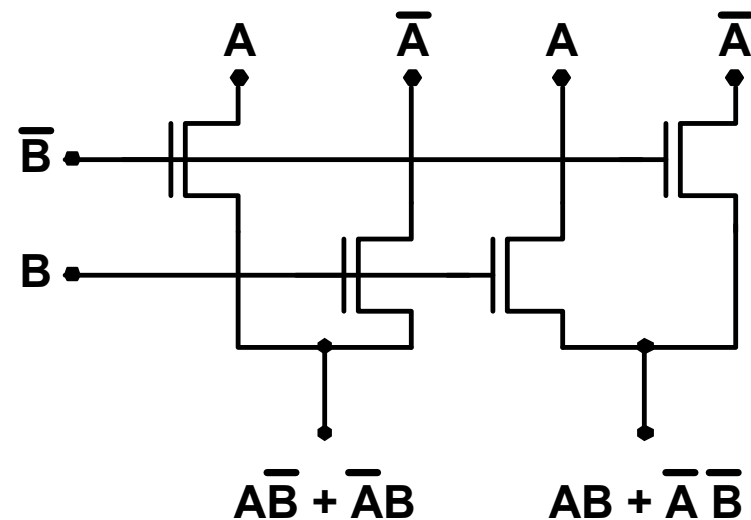  




Chapter 5

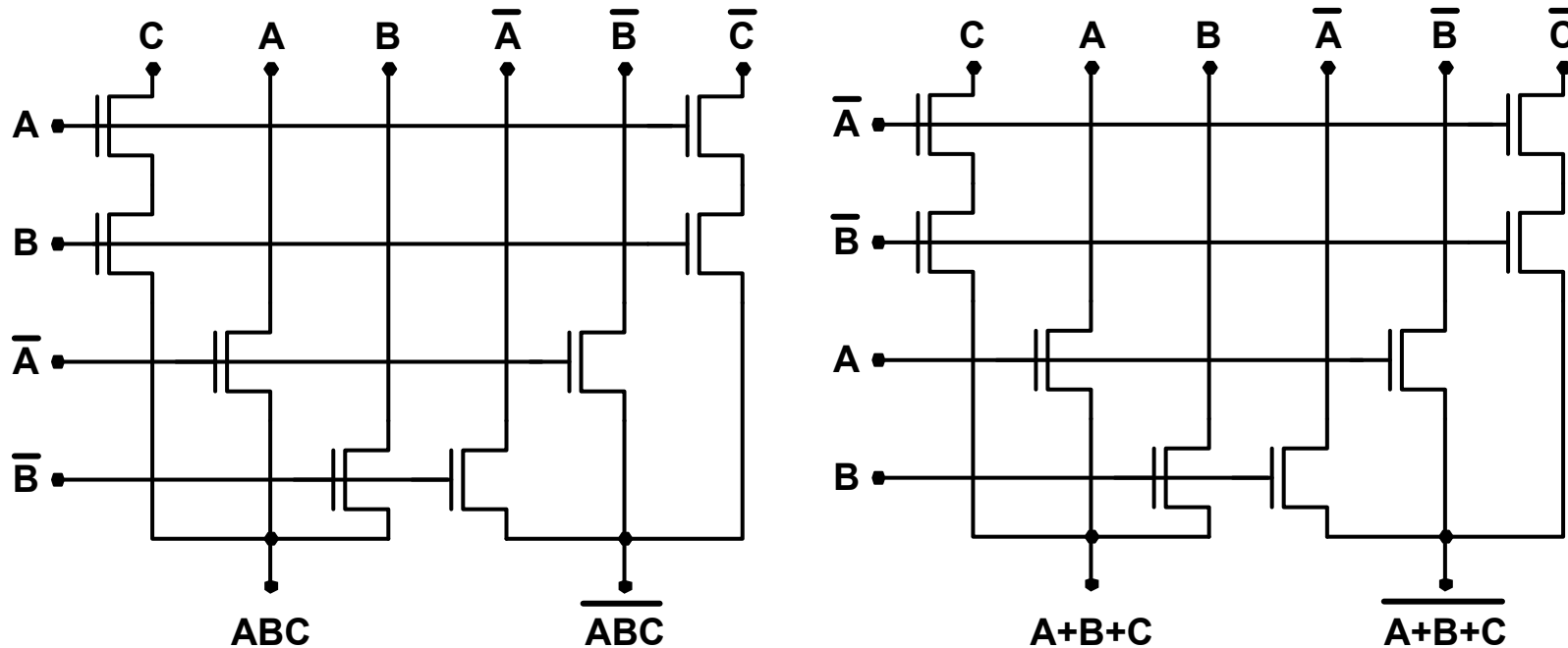5.4.4 Complementary Pass – Transistor Logic (CPL) (5/7)

✦ 3-input AND / NAND , OR / NOR logic array



- Any complex logic function can be constructed easily using this principle of the NMOS network transistors .




Chapter 5


5.4.4 Complementary Pass – Transistor Logic (CPL) (6/7)

✦ CPL Full Adder (1/2)

(a) Sum block

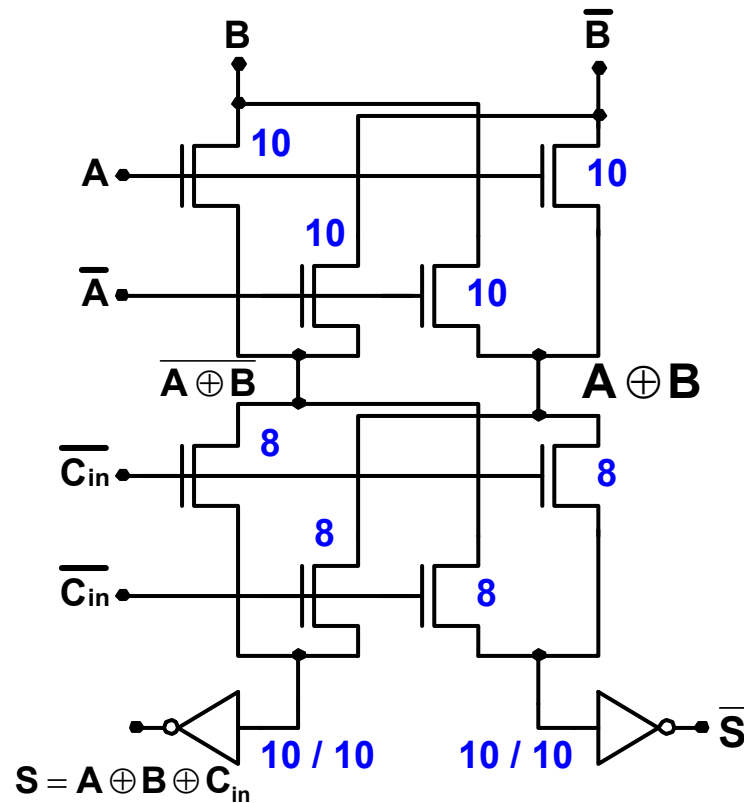

(b) Carry block

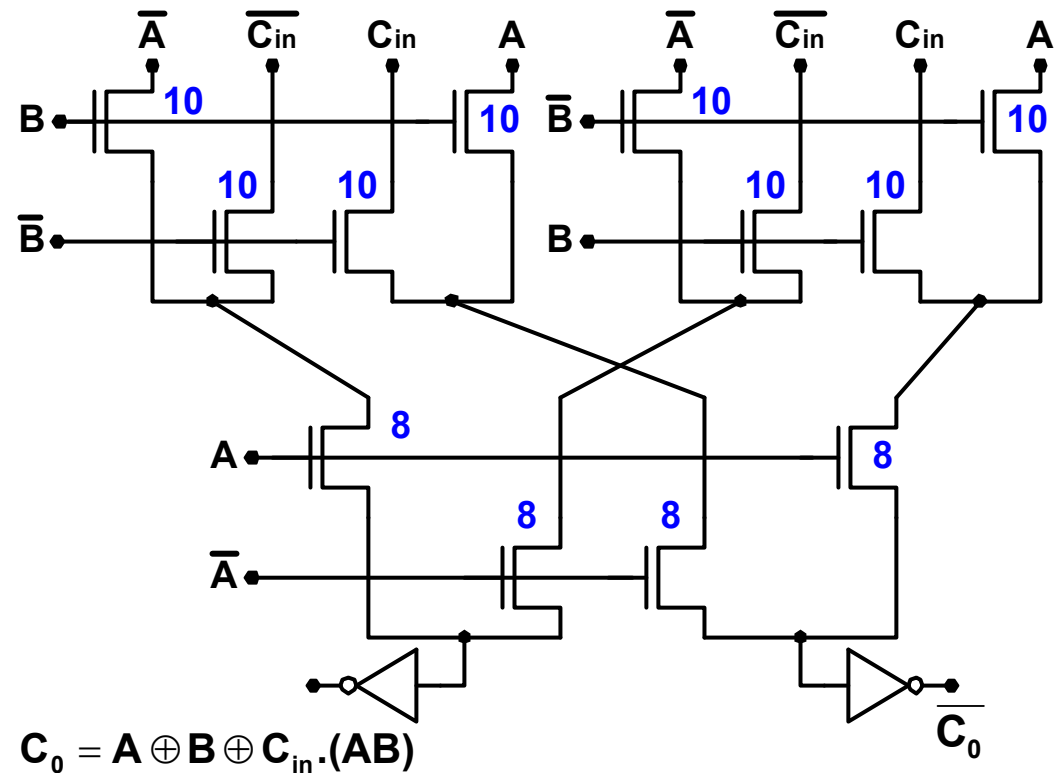



Chapter 5

5.4.4 Complementary Pass – Transistor Logic (CPL) (7/7)

CPL Full Adder (2/2)

- For fast operation , the transistors of the NMOS network , far from the output , have large size than those closer to the output .
(This is because the NMOS devices , closer to the output , pass a reduced swing .)




Chapter 5

5.4.5 Dual Pass – Transistor Logic (DPL) (1/5)

- Ref : IEEE JSSC , vol. sc-28 , no.11 , PP.1145~1151 , Nov. 1993.
- ✦ The DPL is a modified version of CPL suitable for low – voltage applications.

■ DPL NAND / AND gate

 - Consists of NMOS and PMOS pass transistors .
- Output is full rail – to – rail swing



DPL AND / NAND gate



Chapter 5

5.4.5 Dual Pass – Transistor Logic (DPL) (2/5)

■ Features of DPL

- The DPL has a balanced input capacitance .
(reduces the delay dependence of the input data)
- In DPL , for any input combination , these are always two current paths driving the output .



Chapter 5

5.4.5 Dual Pass – Transistor Logic (DPL) (3/5)

■ Comparison of CPL , conventional CMOS TG and DPL

- In the true tables , the column labeled “ pass ” shows which signals are passed and perform the XOR function .

	CPL	CMOS	DPL																																																												
circuit																																																															
Turth Table & Operation	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr> <td>0</td><td>1</td><td>1</td><td>B</td></tr> <tr> <td>1</td><td>0</td><td>1</td><td>B-bar</td></tr> <tr> <td>1</td><td>1</td><td>0</td><td>B-bar</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1	B	1	0	1	B-bar	1	1	0	B-bar	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr> <td>0</td><td>1</td><td>1</td><td>B</td></tr> <tr> <td>1</td><td>0</td><td>1</td><td>B-bar</td></tr> <tr> <td>1</td><td>1</td><td>0</td><td>B-bar</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1	B	1	0	1	B-bar	1	1	0	B-bar	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr> <td>0</td><td>1</td><td>1</td><td>B</td></tr> <tr> <td>1</td><td>0</td><td>1</td><td>B-bar</td></tr> <tr> <td>1</td><td>1</td><td>0</td><td>B-bar</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1	B	1	0	1	B-bar	1	1	0	B-bar
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1	B																																																												
1	0	1	B-bar																																																												
1	1	0	B-bar																																																												
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1	B																																																												
1	0	1	B-bar																																																												
1	1	0	B-bar																																																												
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1	B																																																												
1	0	1	B-bar																																																												
1	1	0	B-bar																																																												
Swing	$0 \leftrightarrow V_{DD} - V_{Tn}$	$0 \leftrightarrow V_{DD}$	$0 \leftrightarrow V_{DD}$																																																												




Chapter 5

5.4.5 Dual Pass – Transistor Logic (DPL) (4/5)

■ CPL Full – Adder (1/2)

$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ &= (A \oplus B) \oplus C_{in} \\ &= (A \oplus B) \overline{C_{in}} + \overline{(A \oplus B)} C_{in} \end{aligned}$$

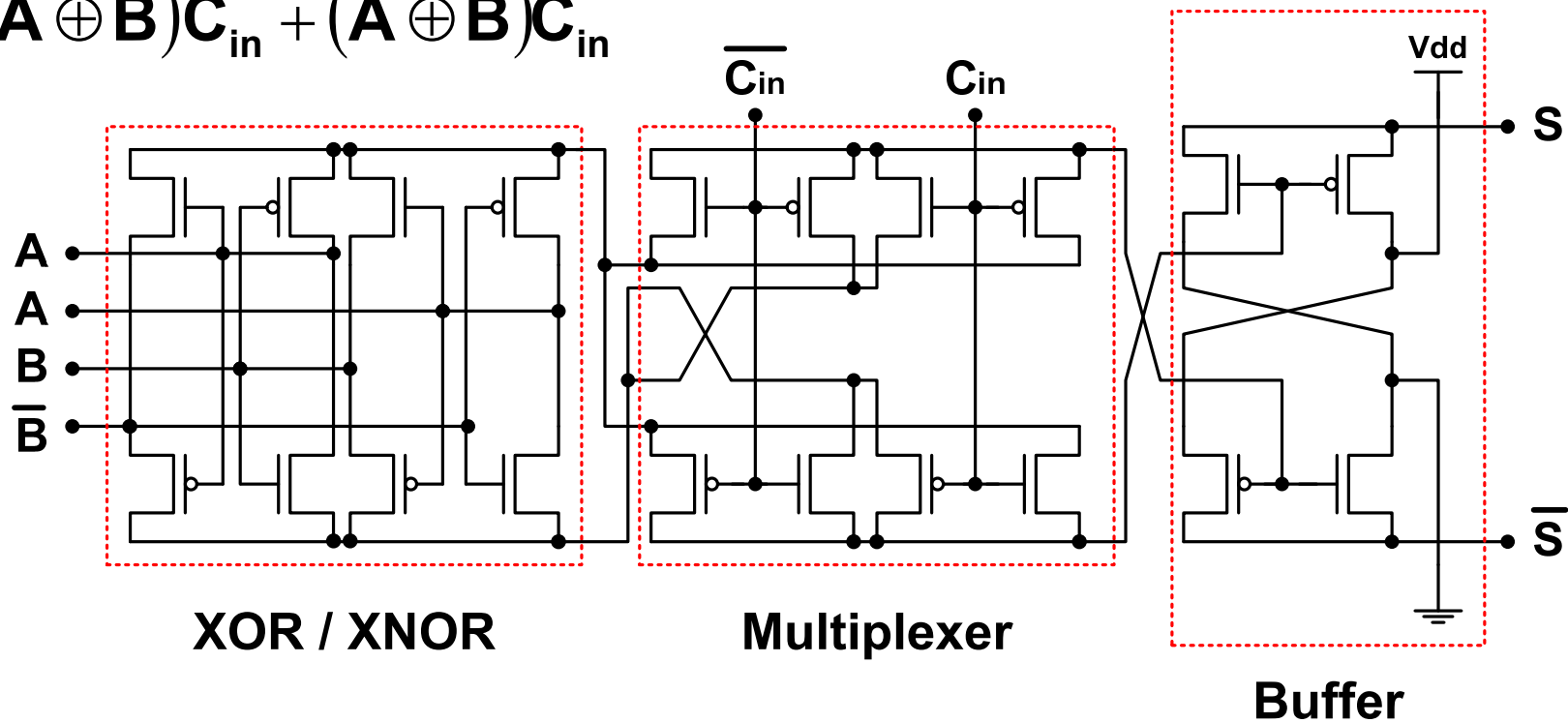




Chapter 5

5.4.5 Dual Pass – Transistor Logic (DPL) (5/5)

■ CPL Full – Adder (2/2)

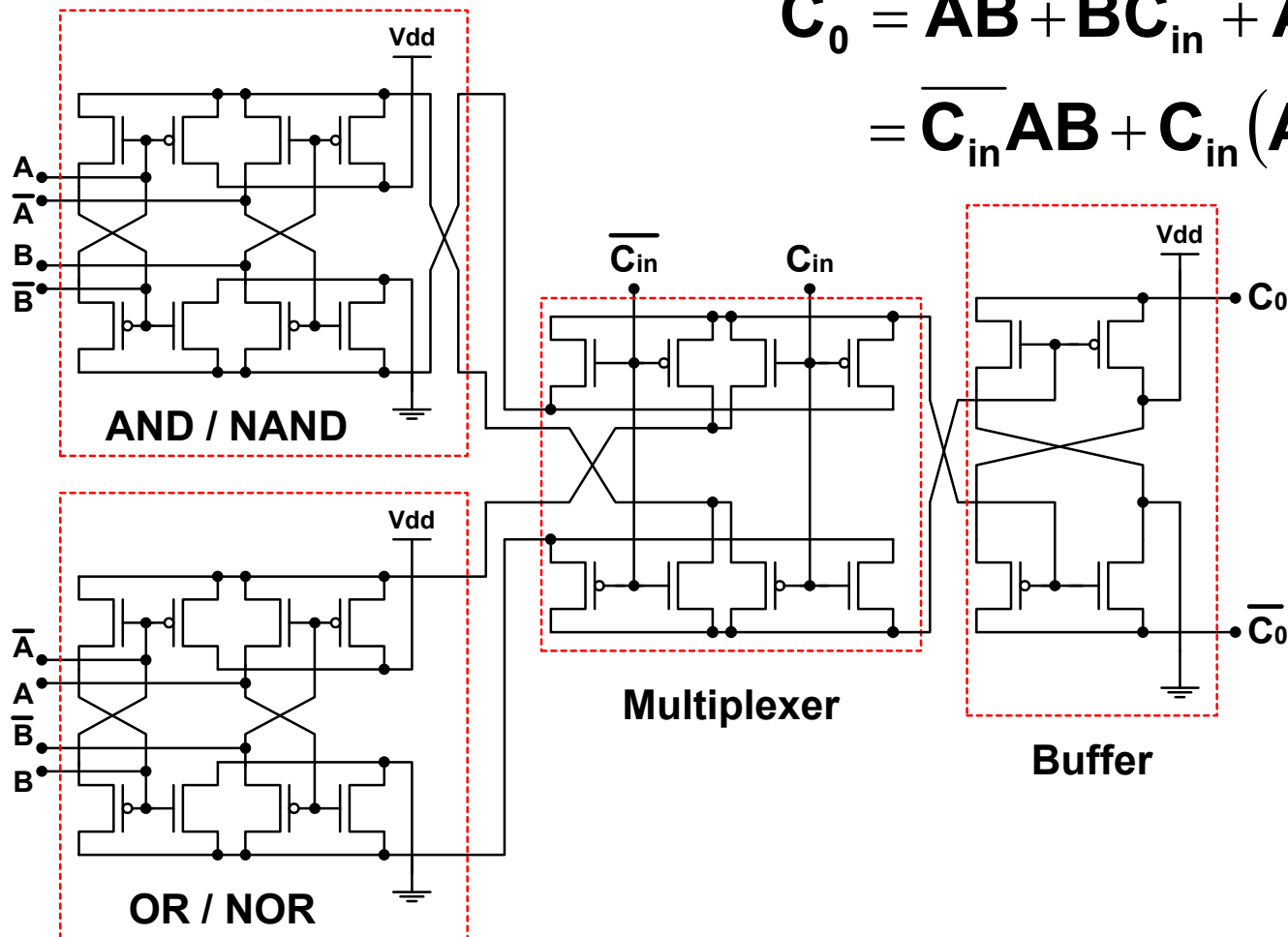


$$C_0 = AB + BC_{in} + AC_{in}$$
$$= \overline{C_{in}}AB + C_{in}(A + B)$$



Chapter 5

5.4.6 Swing Restored Pass - Transistor Logic (SRPL) (1/2)

- Ref : *IEEE Custom Integrated Circuits Conference Tech Dig. PP.278~281 , May. 1994.*
- ✱ CPL like style suitable for low – power / low – voltage application .
- The cross – coupled CMOS inverters (latch) permit to restore the logic levels .
- The size of the latch should be minimum


 




Chapter 5

 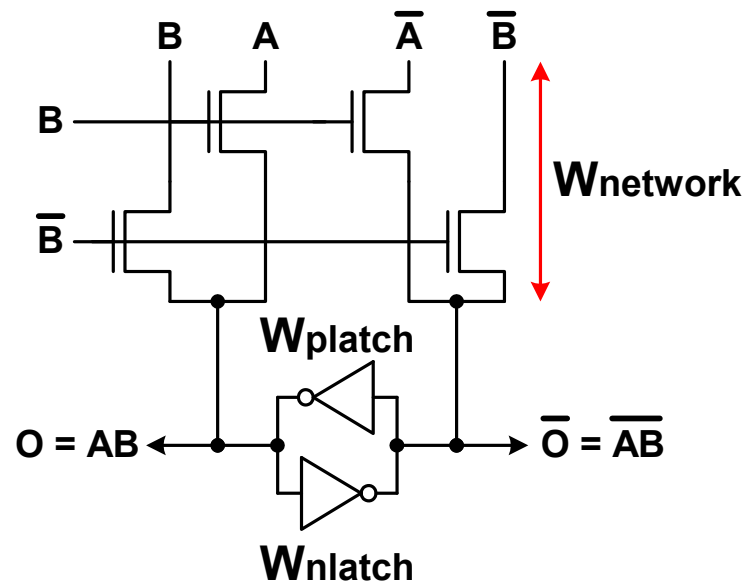5.4.6 Swing Restored Pass - Transistor Logic (SRPL) (2/2)

- The size of such a logic is critical for speed and power dissipation .



Delay of AND / NAND gate versus NMOS size


- If the size of the NMOS transistors in the network is small , the output of the SRPL gate fail to swing to ground , because the equivalent impedance of the network is lower than the one seen by the output to V_{DD} .*



Chapter 5

5.4.7 Pass - Transistor Logic Comparison

- ✱ The speed and power dissipation of the different pass – logic styles , so far presented , **depend on the circuit type and the application of the circuit** (cascaded gates , driving a fixed load , etc .) . For the case of a full – adder , used in a multiplier array , a comparison is given . In general , **SRPL has the lowest power dissipation** but careful design is needed when **small device sizes** are used . The **DPL** consumes more power than SRPL and PMOS latch CPL , because of the **higher transistor count** . Both CPL and SRPL circuits have the smallest area and the fastest speed . In summary , CPL – like styles are promising , for low – power and high – speed applications .

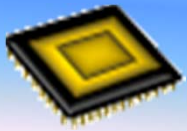

Chapter 5

5.5 Input / Output Circuits


- I/O circuits connect the on – chip logic circuitry to the external world .
- Play an important role in the limitation of speed and power dissipation of the whole chip



Chapter 5

5.5.1 Overall Organization (1/2)

- Pad structure

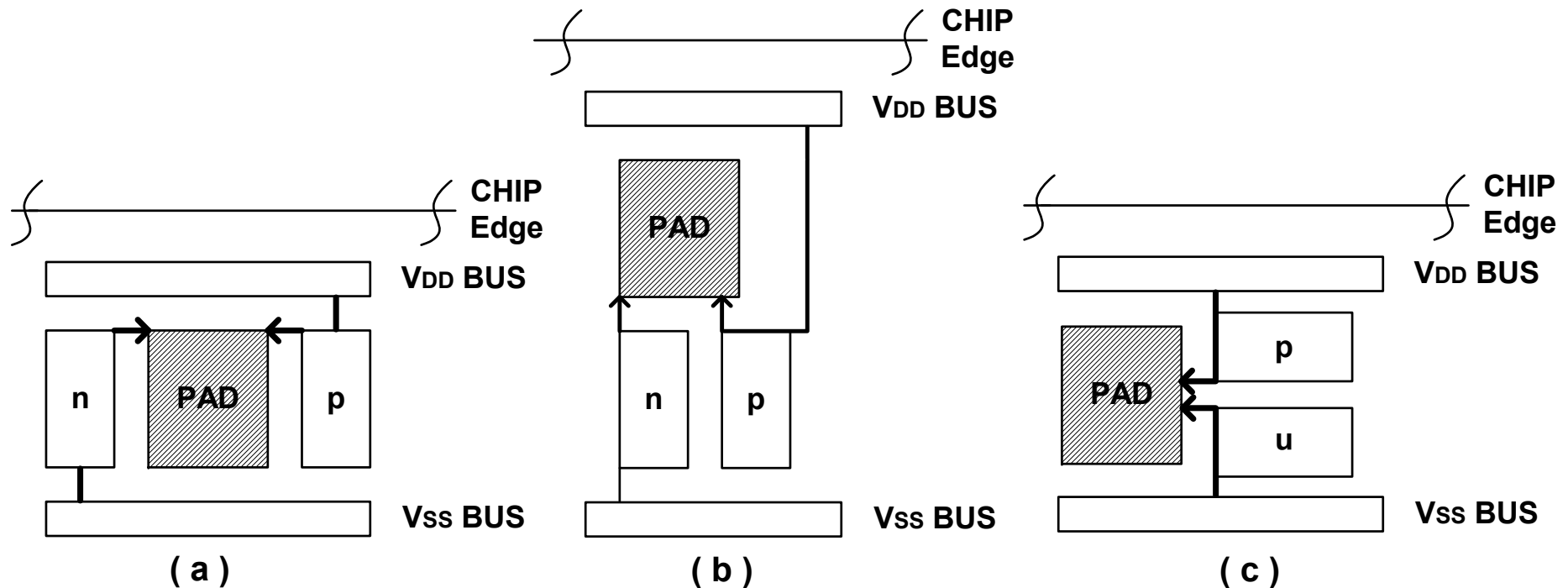





Chapter 5

5.5.1 Overall Organization (2/2)

- I/O Frame

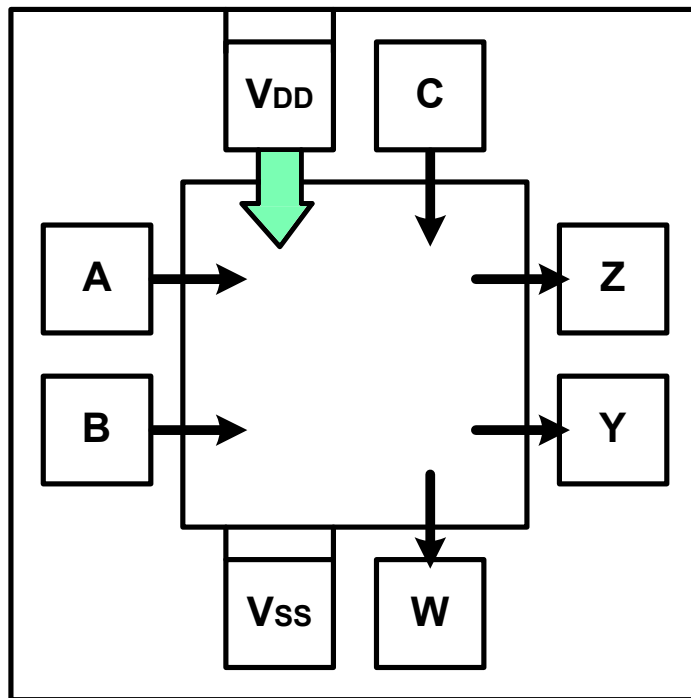

(a) I/O frame generation

 


(b) V_{DD} pad design



Chapter 5

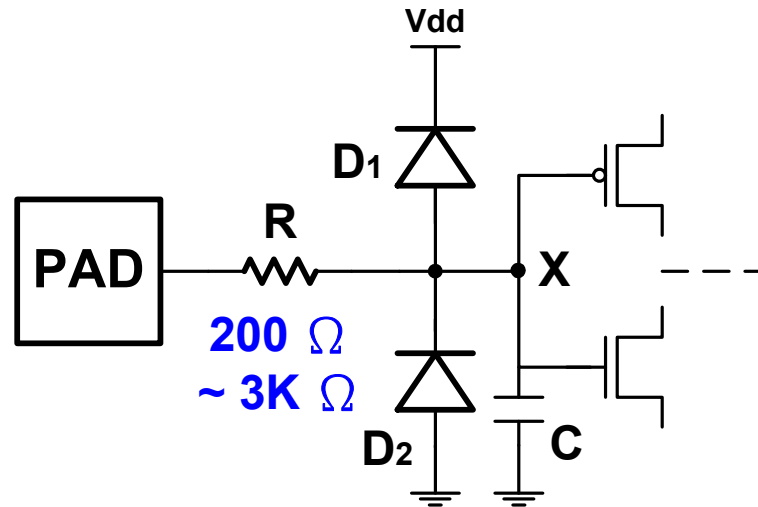5.5.2 Input – pad Protection Circuit (1/2)






- D1 and D2 protection diode : limit the voltage excursion of the node N within $(-V_{BE})$ and $(V_{DD} + V_{BE})$
- Input protection circuit has a parasitic RC limits the high speed operation .



Chapter 5

5.5.2 Input – pad Protection Circuit (2/2)

  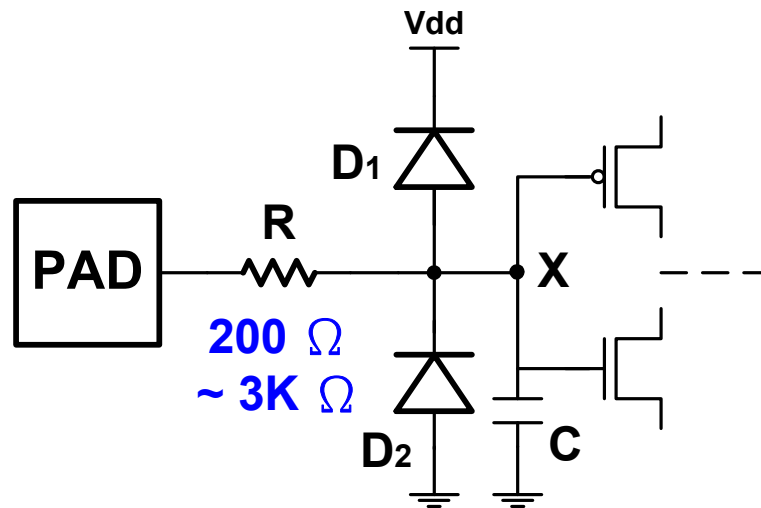




Chapter 5

5.5.3 Tri – state Output Buffer (1/2)


- Non – inverting tri – state buffer
- ※ For large output cap.

Truth table

En	A	Output
0	X	Z (High Impedance)
1	0	0
1	1	1

 


(a) symbol

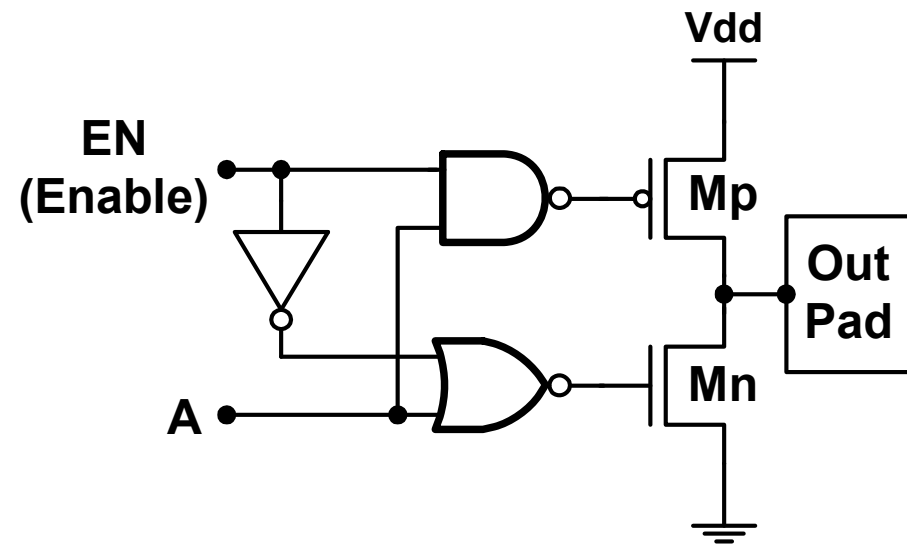

(b) Circuit



※ C²MOS is not suitable in this case (Why ?)

 


Chapter 5

5.5.3 Tri – state Output Buffer (2/2)


- Inverting tri – state buffer

  

 

Chapter 5

5.5.4 Bi – Directional Pad

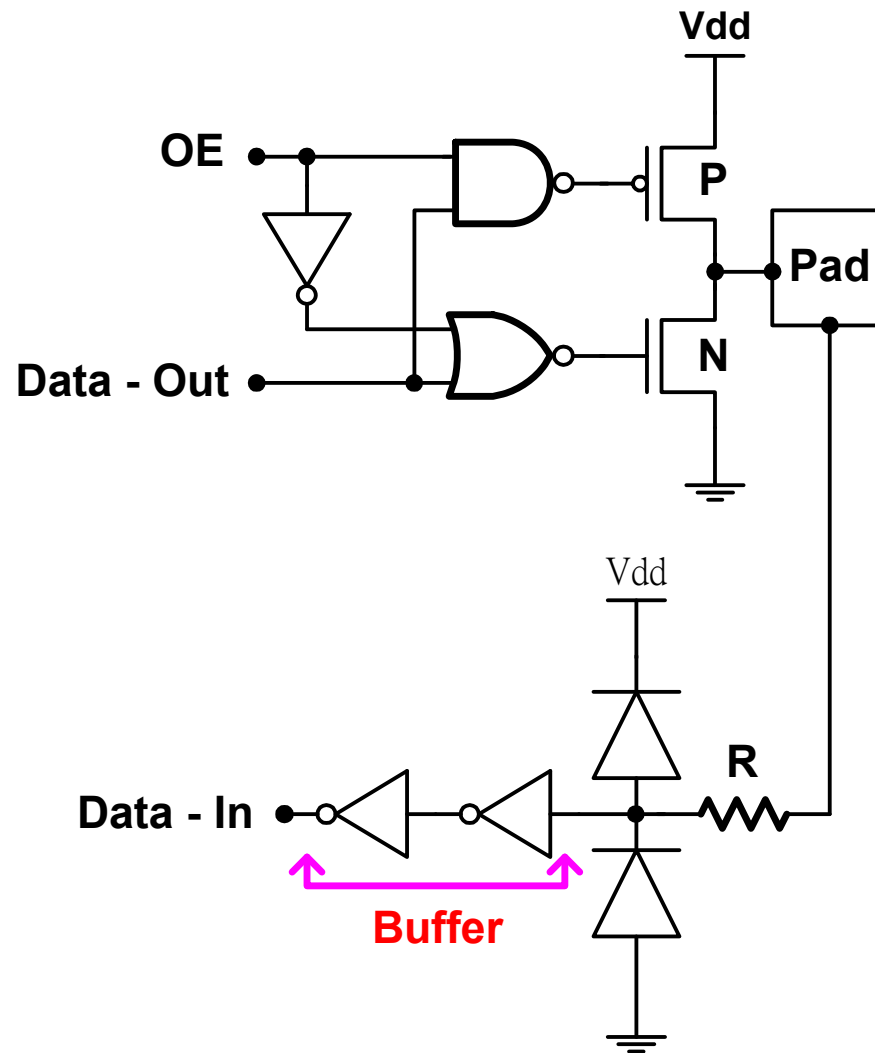





Chapter 5

5.5.5 CMOS To TTL Output Buffer


- If the CMOS Output buffer is intended to drive bipolar TTL inputs , then important current is **SUNK** .
→ A CMOS output buffer must sink this current .
- For 3.3V supply , this current can be 1mA to 12mA (depending on driver)

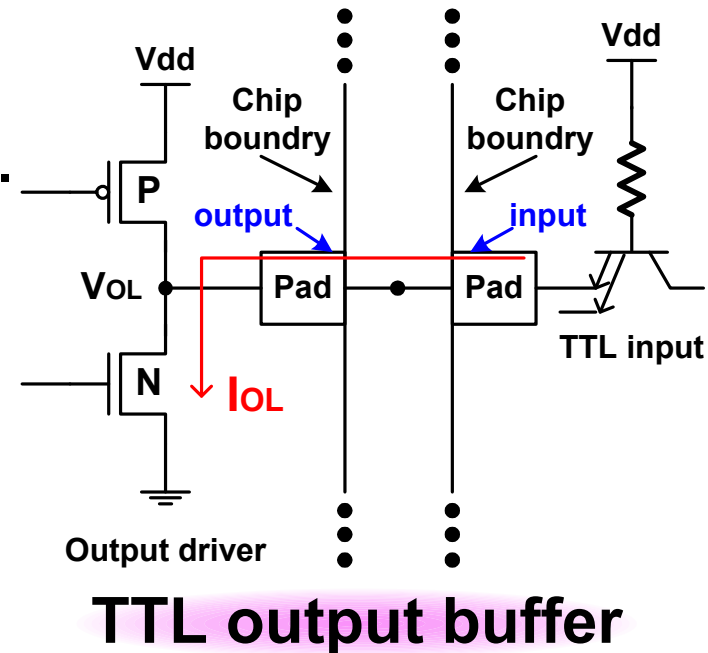

 


Chapter 5

5.5.6 Schmitt Trigger (1/4)

 

 Transfer characteristic of Schmitt trigger



Voltage waveforms for slow input



Chapter 5

5.5.6 Schmitt Trigger (2/4)

- When $V_{in} = V_{T+}$, N_2 enters in conduction mode which means $V_{GS2} = V_{Tn}$ then

$$V_{FN} = V_{T+} - V_{Tn}$$
- We neglect the body effect of N_2
- The voltage V_{FN} is controlled by N_1 and N_3 . These transistors operate in saturation because


$$V_{GS1} = V_{T+}$$

$$V_{DS1} = V_{FN} = V_{FN} = V_{T+} - V_{Tn}$$

And

$$V_{GS3} = V_{DD} - V_{FN}$$

$$V_{DS3} = V_{DD} - V_{FN}$$

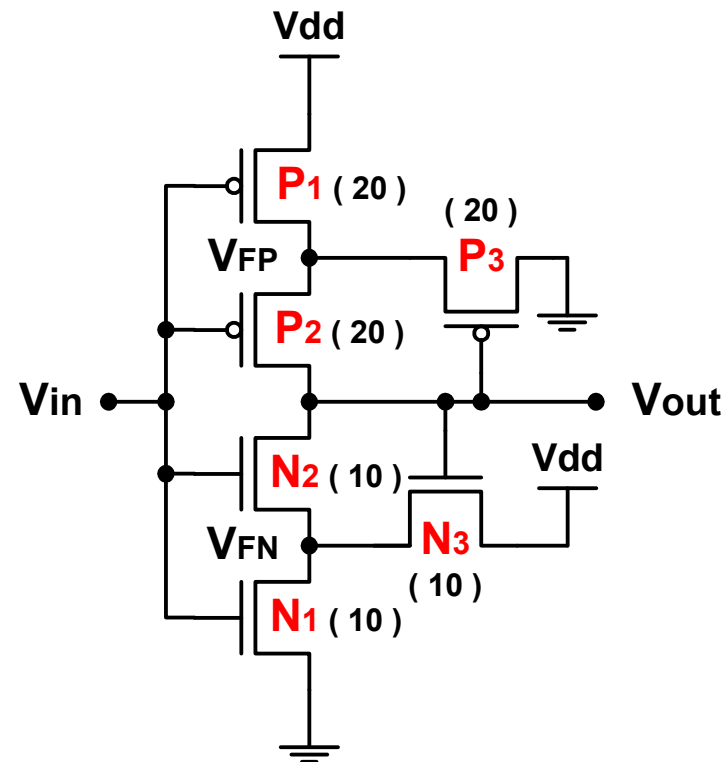

The CMOS Schmitt trigger schematic



Chapter 5

5.5.6 Schmitt Trigger (3/4)

The drain currents flowing in N_1 and N_3 are equal . Then using a simple MOS model we have

$$\frac{\beta_{n1}}{2}(V_{T+} - V_{Tn})^2 = \frac{\beta_{n3}}{2}(V_{DD} - V_{T+})^2$$

We have
$$V_{T+} = \frac{V_{DD} + \sqrt{\beta_n} V_{Tn}}{1 + \sqrt{\beta_n}}$$

Where
$$\beta_n = \frac{\beta_{n1}}{\beta_{n3}} = \left\{ \frac{W_{n1}/L_{n1}}{W_{n3}/L_{n3}} \right\}_{\text{eff}}$$

This equation shows that the trigger point is independent of the process parameters except for V_{Tn} . By symmetry , the trigger point for falling transition , can be deduced from the pull – up section .

We have
$$V_{T-} = \frac{\sqrt{\beta_p}(V_{DD} + V_{Tp})}{1 + \sqrt{\beta_p}}$$

Where
$$\beta_p = \frac{\beta_{p1}}{\beta_{p3}} = \left\{ \frac{W_{p1}/L_{p1}}{W_{p3}/L_{p3}} \right\}_{\text{eff}}$$





Chapter 5

5.5.6 Schmitt Trigger (4/4)

If $n=p$ and $V_{Tn} = -V_{Tp} = V_T$, then

$$V_{T+} = \frac{V_{DD}}{2} + \frac{V_T}{2} ; V_{T-} = \frac{V_{DD}}{2} - \frac{V_T}{2} ; V_H = V_{T+} - V_{T-} = V_T$$

In this case the hysteresis voltage can be made equal to V_T .
The short – circuit power dissipation of the Schmitt trigger can be very important since the rise / fall times of the input signal is very long .

  




Chapter 5

5.6 Clock Drivers and Clock Distribution

5.6.1 Clock Skew Problem (1/2)

- The clock skew problem is due mainly to two issues :
- ☀ (1) 、 **The difference in RC interconnect time constants :**
- Example : node A and node B have different branch lengths to node C → at node A and node B are different

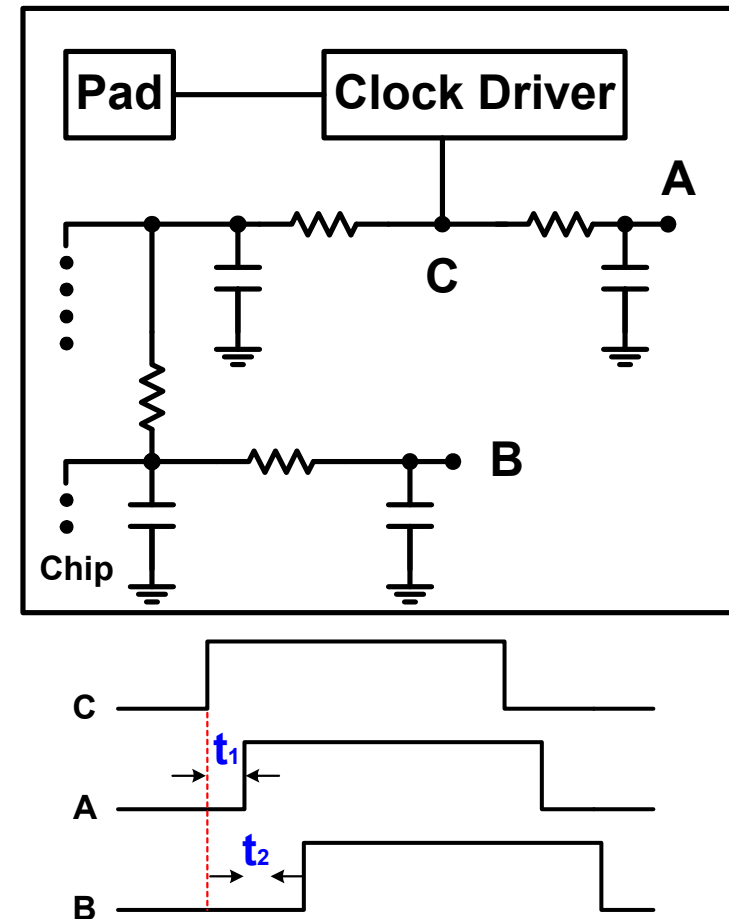




Chapter 5

5.6.1 Clock Skew Problem (2/2)

✱ (2) 、 Unbalanced loads at different nodes :


- Example : load at node A and B (C_A , C_B) are different → clock skew .

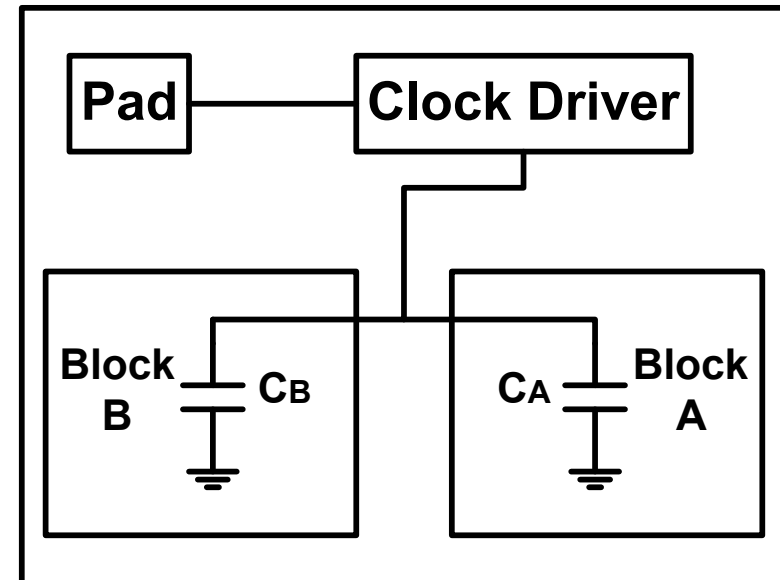




Chapter 5


5.6.2 Clock Driver Options (1/3)

 

(a) Single driver

 

(b) Four side approach

 

(c) " down the center "
" approach




Chapter 5

5.6.2 Clock Driver Options (2/3)

■ Clock distribution

- Cascaded inverters for global clock distribution

 



Chapter 5

5.6.2 Clock Driver Options (3/3)

■ Tree distribution

